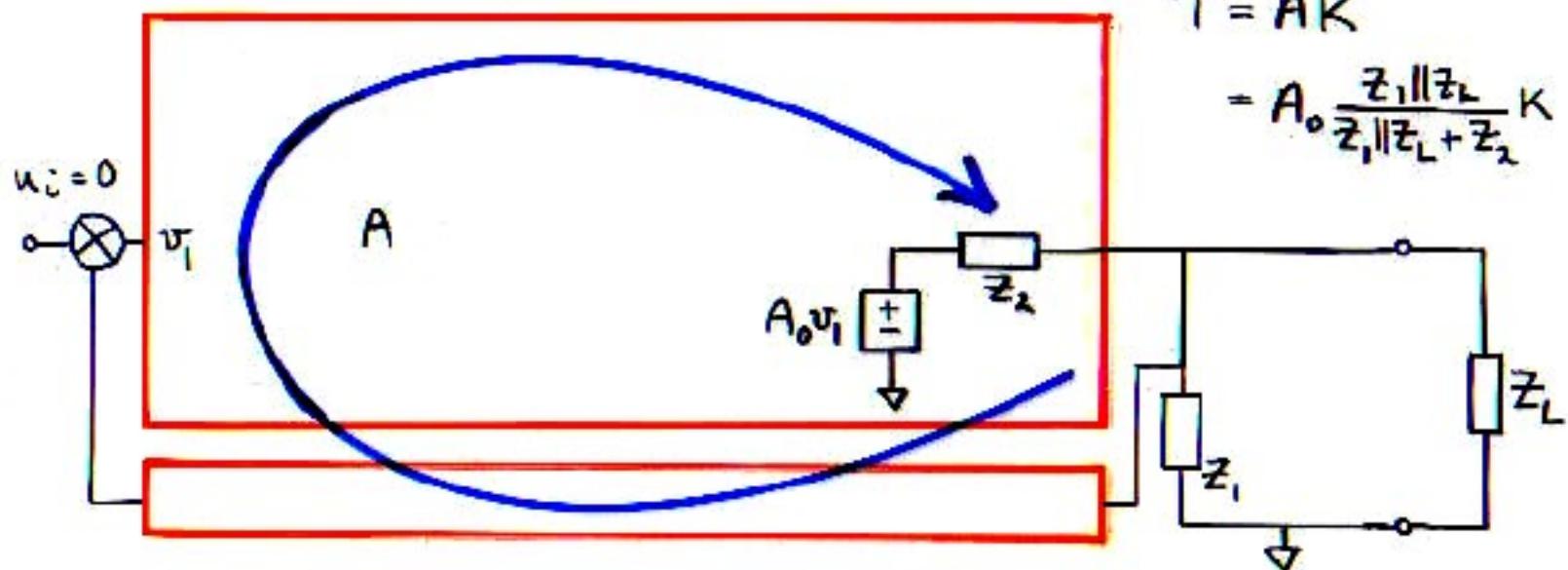



9


ALL ABOUT T



$$T = AK$$

$$= A_0 \cdot \frac{z_1 \| z_L}{z_1 \| z_L + z_2} K$$

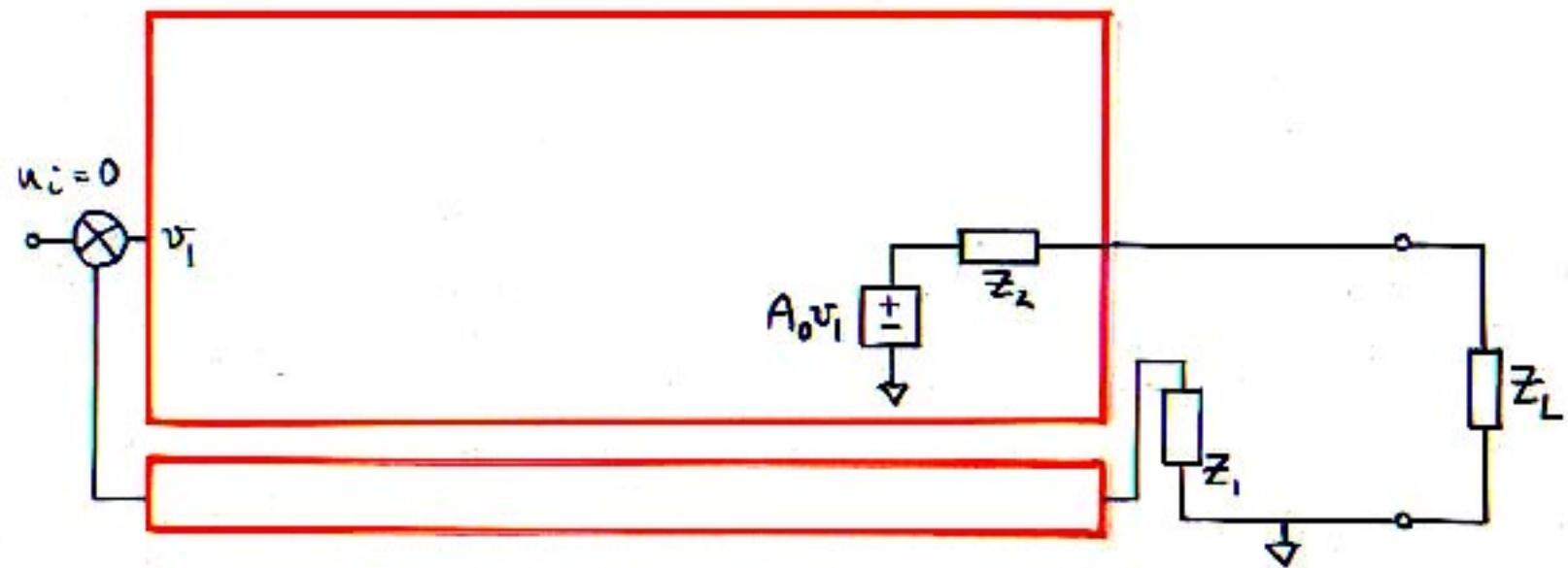


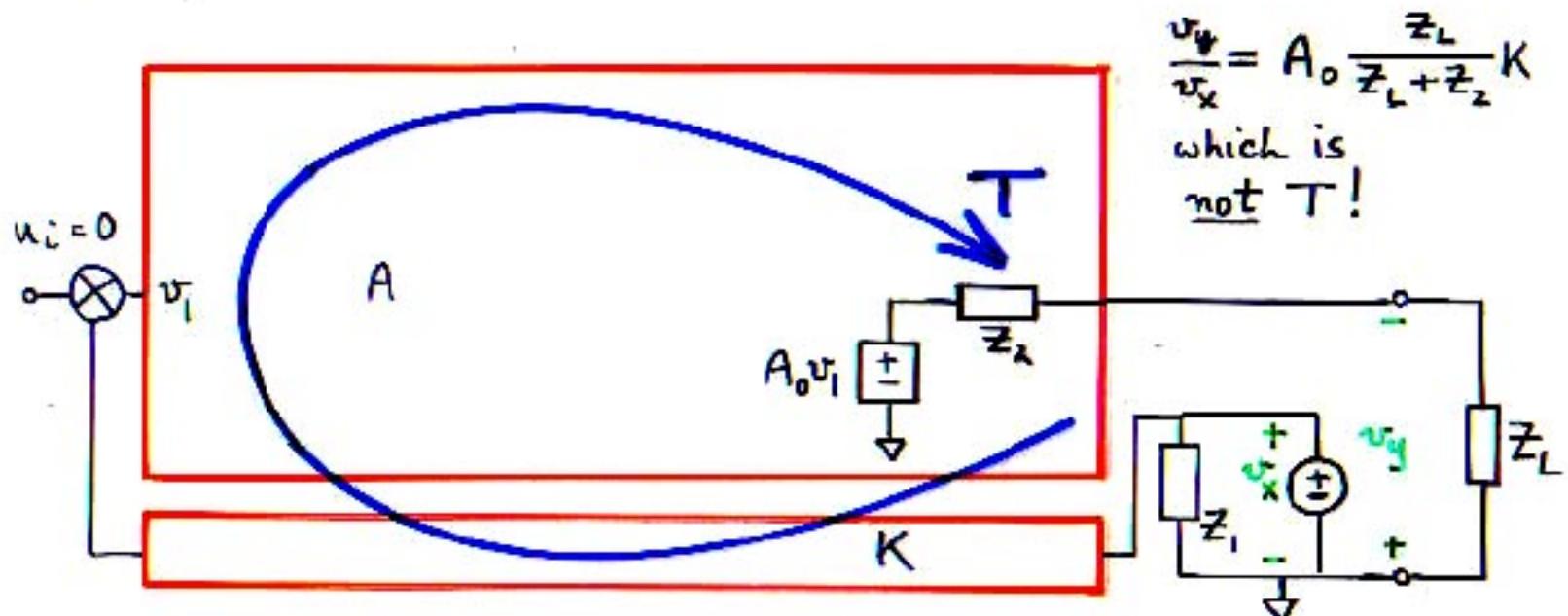

Conventional procedure: break the loop at the output (or input) of the forward path, and find $T = \frac{u_y}{u_x} = AK$.


However, often the feedback path loads the forward path at the output (or input), so the value found for A and/or K is not the same as when the loop is closed, and so the wrong answer is obtained for T.

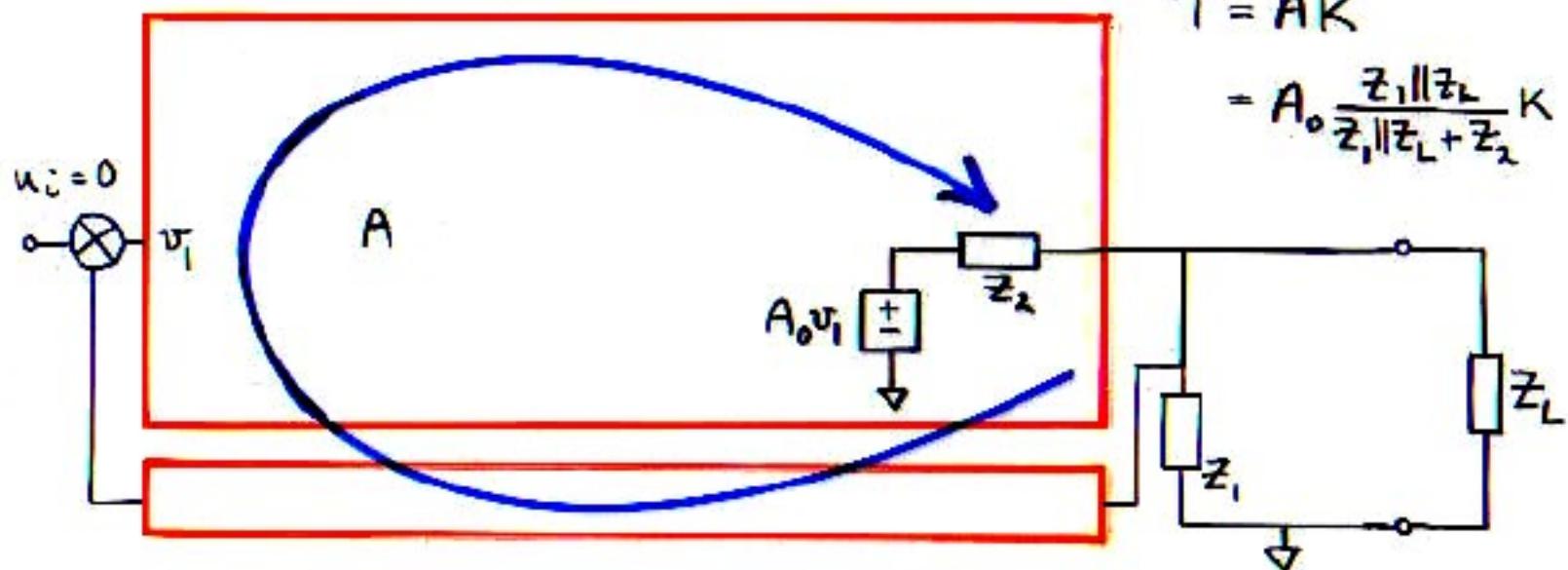In some cases the loading may be simulated, but involves guesswork.



$$T = AK$$

$$= A_0 \frac{z_1 || z_L}{z_1 || z_L + z_2} K$$

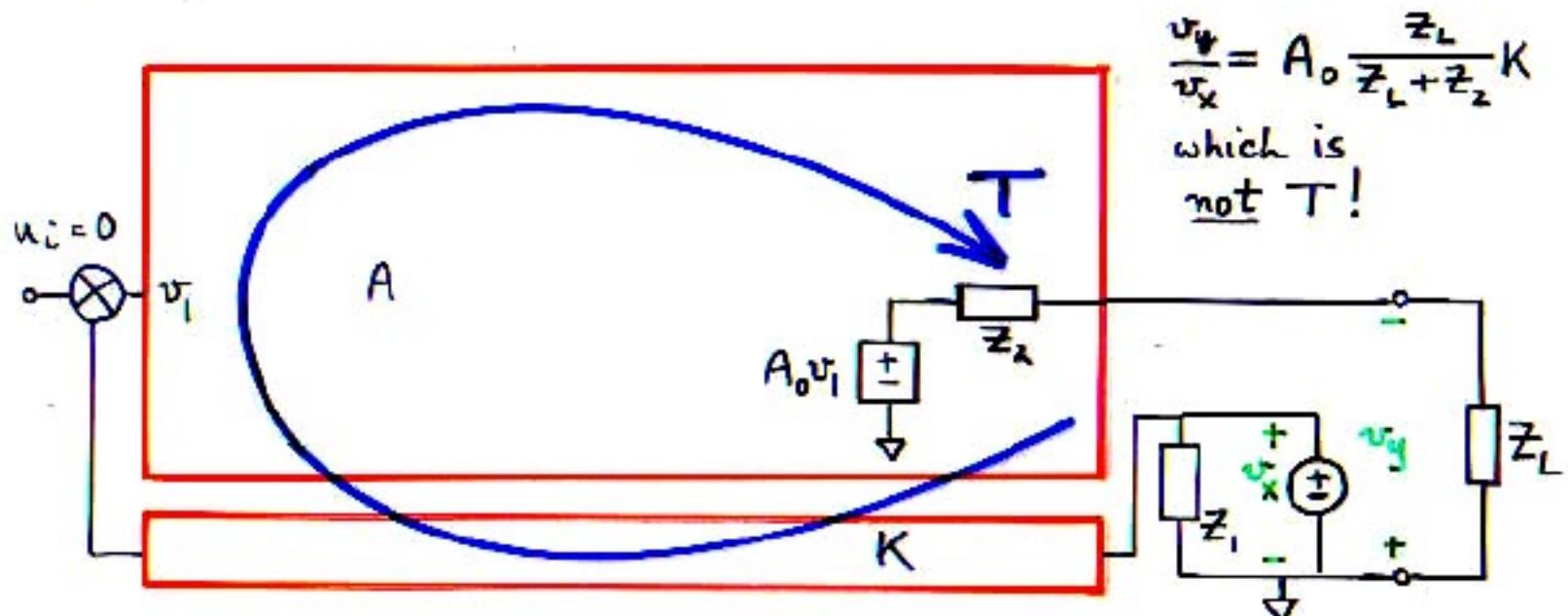

Conventional procedure: break the loop at the output (or input) of the forward path, and find $T = \frac{v_y}{v_x} = AK$.

However, often the feedback path loads the forward path at the output (or input), so the value found for A and/or K is not the same as when the loop is closed, and so the wrong answer is obtained for T.

In some cases the loading may be simulated, but involves guesswork.


Instead, since A need not be known separately, break the loop at a point where the loading is not disturbed (usually somewhere in the forward path).


Loop Gain by Signal Injection into the Closed Loop


One of the most valuable benefits of the improved feedback formula is that, since A does not have to be known separately, the loop need not be broken at either the input or the output.


Instead, the break can be made anywhere in the loop, so that a test point can be chosen where the loading is not upset by the break.

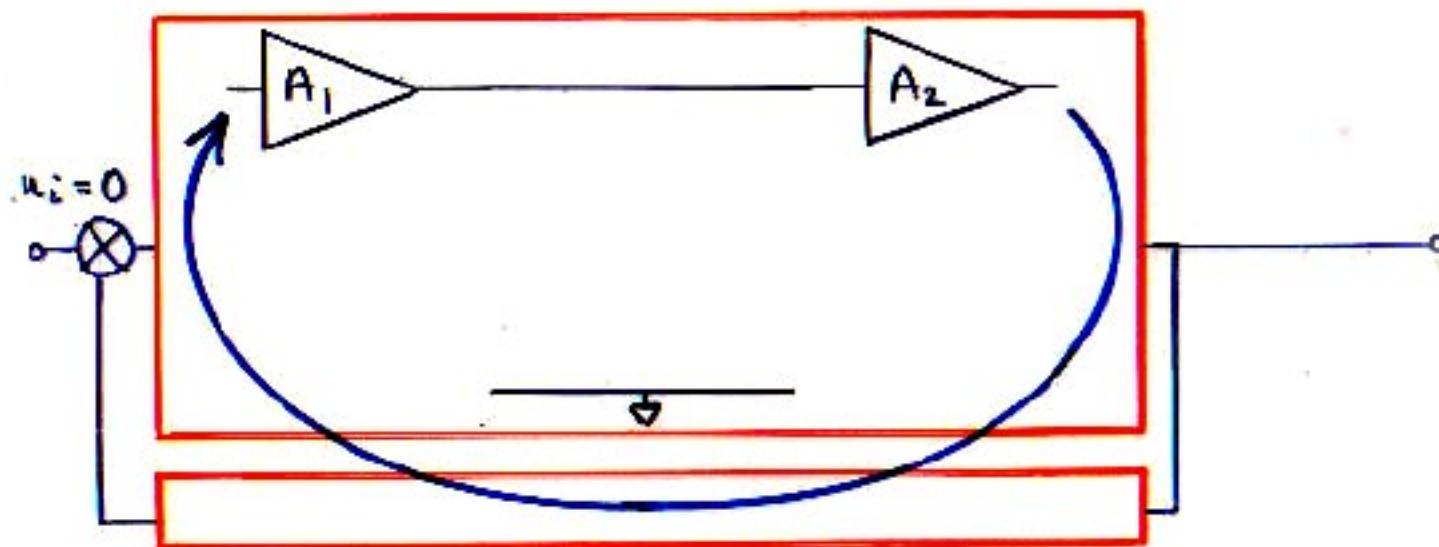A convenient test point is at a dependent generator in the model.



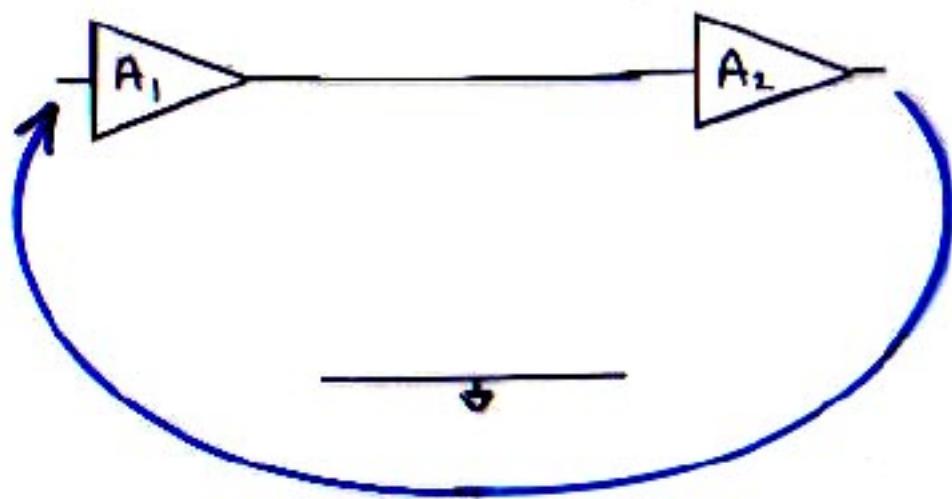


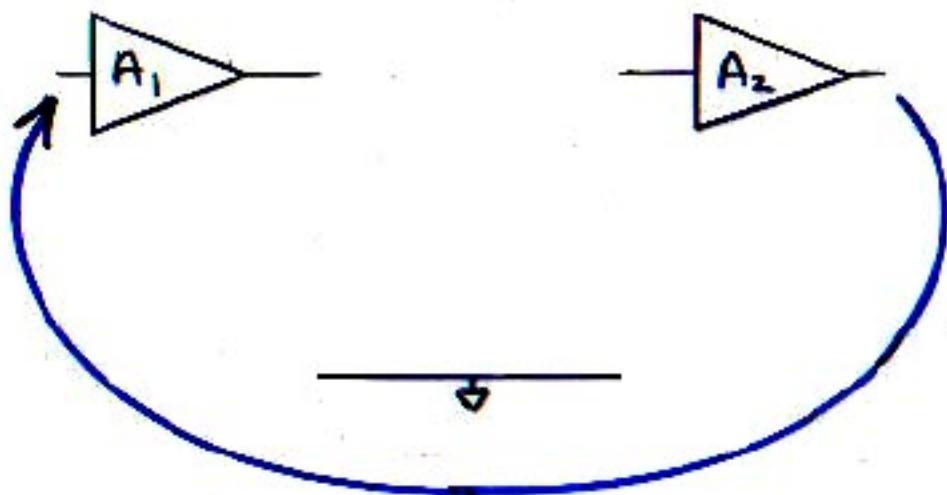

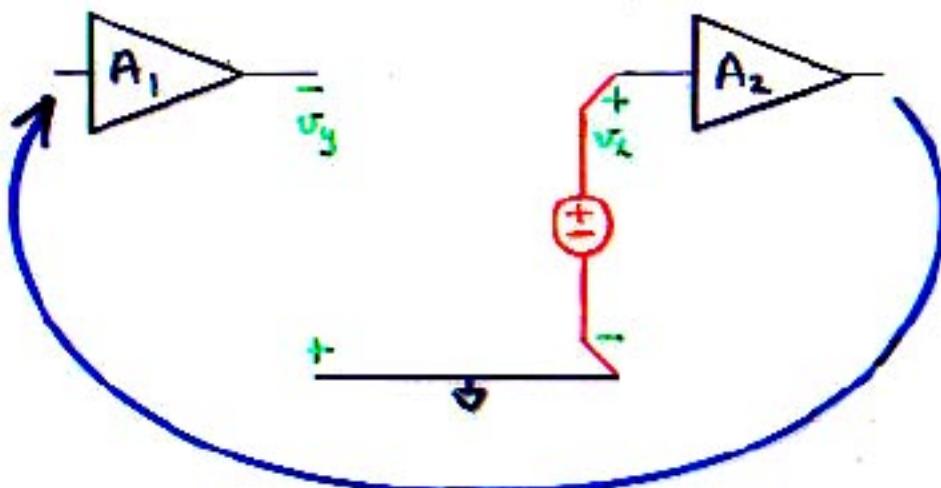

If A_1 and A_2 are unaffected by breaking the loop between A_1 and A_2 , a test signal v_x may be applied at the input of A_2 , and the resulting signal v_y at the output of A_1 gives the correct value of the loop gain T as


$$T = \frac{v_y}{v_x}$$

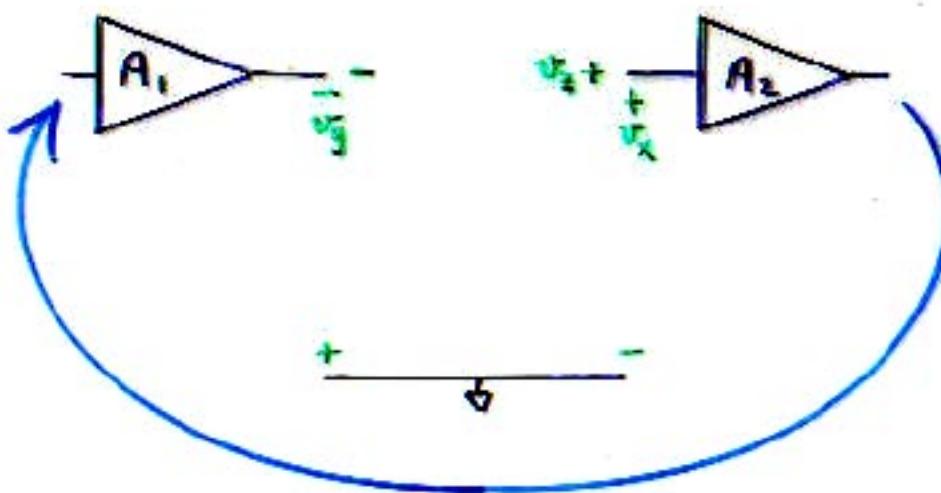

Under such conditions, a voltage $v_z = v_x + v_y$ exists across the break.

It makes no difference to the ratio v_y/v_x whether the driving signal is v_x or v_z .

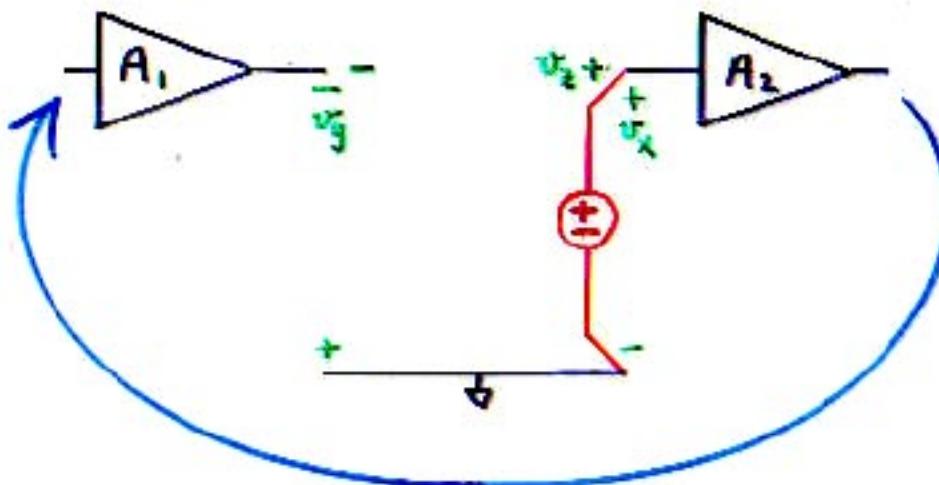
Hence $T = \frac{v_x}{v_x}$, regardless of whether the system is driven by v_x or v_z .



Under such conditions, a voltage $v_z = v_x + v_y$ exists across the break.

It makes no difference to the ratio v_y/v_x whether the driving signal is v_x or v_z .

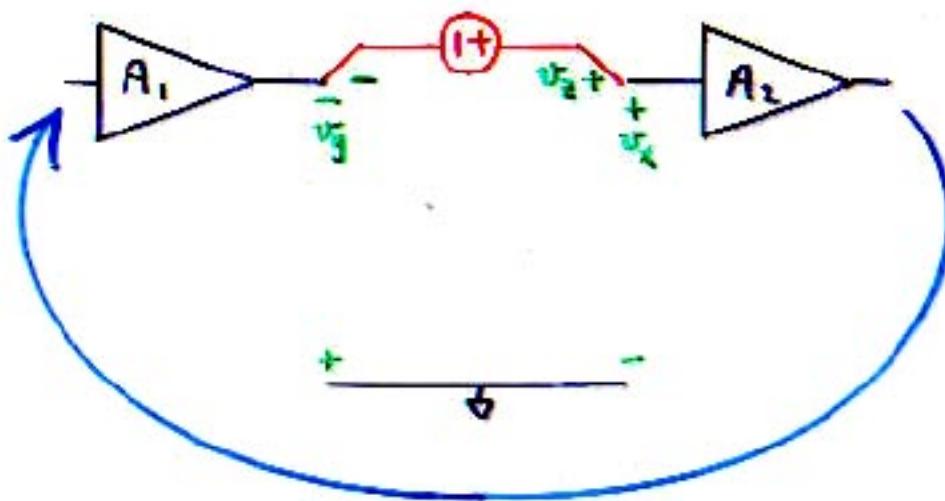
Hence $T = \frac{v_z}{v_x}$, regardless of whether the system is driven by v_x or v_z .



Under such conditions, a voltage $v_z = v_x + v_y$ exists across the break.

It makes no difference to the ratio v_y/v_x whether the driving signal is v_x or v_z .

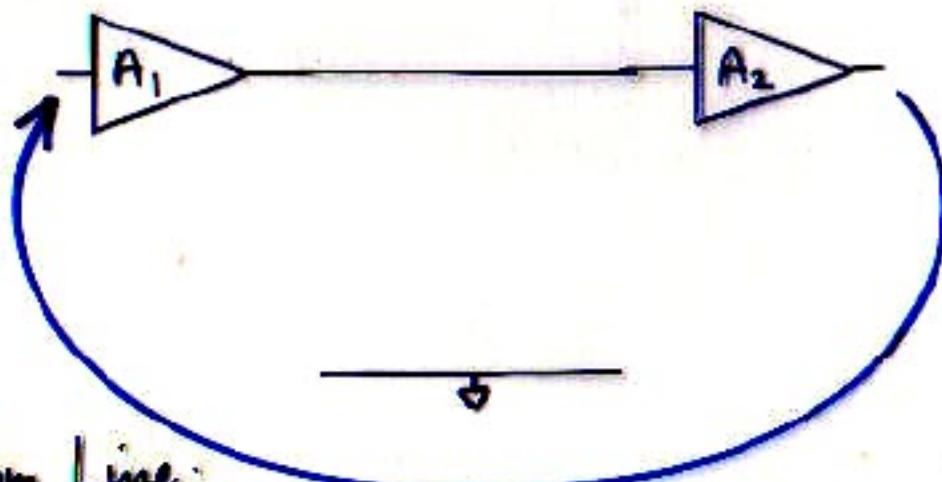
Hence $T = \frac{v_y}{v_x}$, regardless of whether the system is driven by v_x or v_z .



Bottom Line:

There are great advantages, especially for experimental application, in use of an injected test signal into the closed loop:

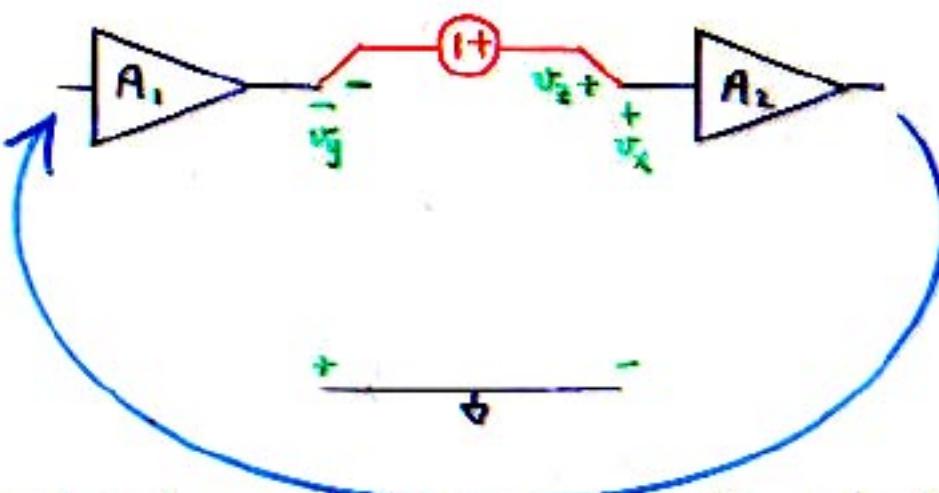1. The loop does not have to be broken, with consequent difficulties in maintaining the proper operating point.
2. The circuit remains in the same configuration (loop remains closed).




Physical interpretation of how the signals adjust to injection of a test signal into the closed loop

$$v_x + v_y = v_z \text{ phasor sum, fixed by the drive } v_z$$


$$\frac{v_y}{v_x} = T \text{ phasor ratio, fixed by the circuit}$$

Hence, the values of v_x and v_y adjust themselves to satisfy simultaneously these two conditions:

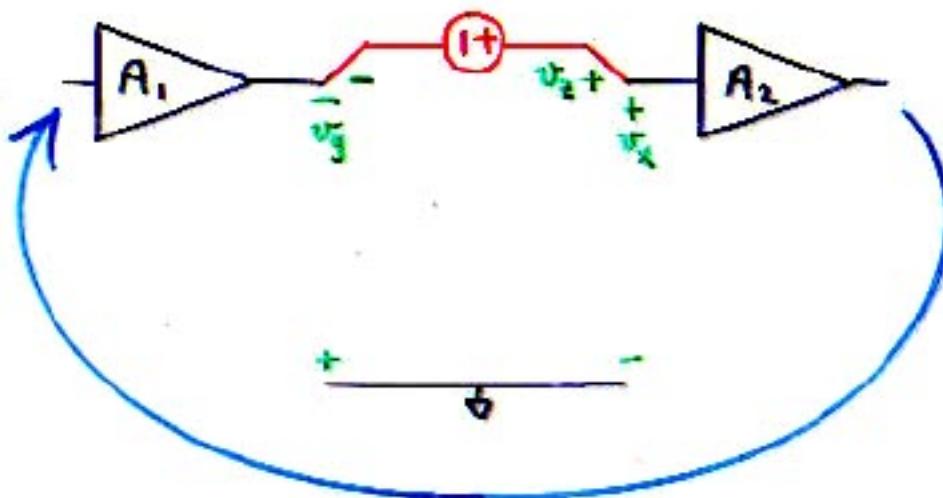
$$v_x = \frac{1}{1+T} v_z \qquad v_y = \frac{T}{1+T} v_z$$



Phasor diagrams for given $|v_z|$ at increasing frequencies:

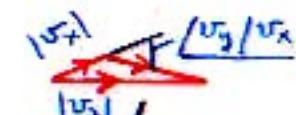

Below crossover frequency, $f \ll f_c$: $\left| \frac{v_y}{v_x} \right| \gg 1$

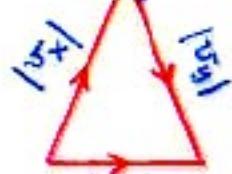

At crossover frequency, $f = f_c$: $\left| \frac{v_y}{v_x} \right| = 1$



Above crossover frequency, $f \gg f_c$: $\left| \frac{v_y}{v_x} \right| \ll 1$

Generalization: Determination of Loop Gain by Injection of a Test Signal into the Closed Loop

Preferable to application of a test signal to a broken loop, because:

1. The loop remains closed, avoiding disturbances of operating point.
2. The circuit remains in the same configuration.

However, injection must be done at a point where, if the loop were broken, there would be negligible change in the loading effects.

Determination of Feedback System Parameters – General

The method of Loop Gain T determination T by injection of a test signal into the closed loop can be generalized and, by inclusion of the Null Double Injection technique, also leads to determination of the Ideal Closed-Loop Gain G_{oo} .


Basic relations:

$$G = \frac{A}{1+AK} = \frac{A}{1+T}$$

$$= \frac{L}{K} \frac{T}{1+T}$$


$$= G_{oo} D$$

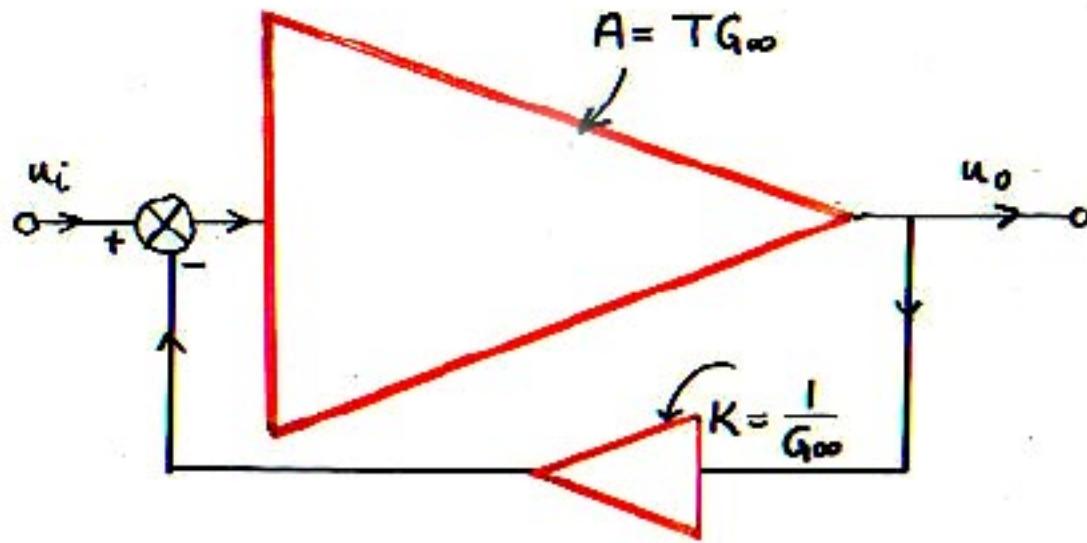Note that $A = TG_{\infty}$ and $K = 1/G_{\infty}$:




Note that $A = TG_{\infty}$ and $K = 1/G_{\infty}$:

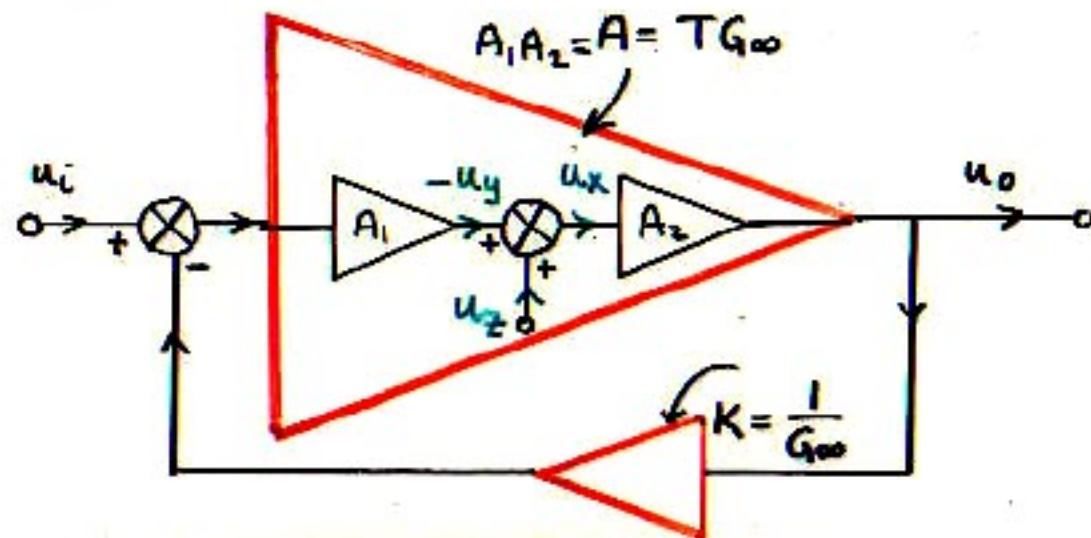Consider a second driving signal u_z injected into the forward path:



Note that $A = TG_{\infty}$ and $K = 1/G_{\infty}$:

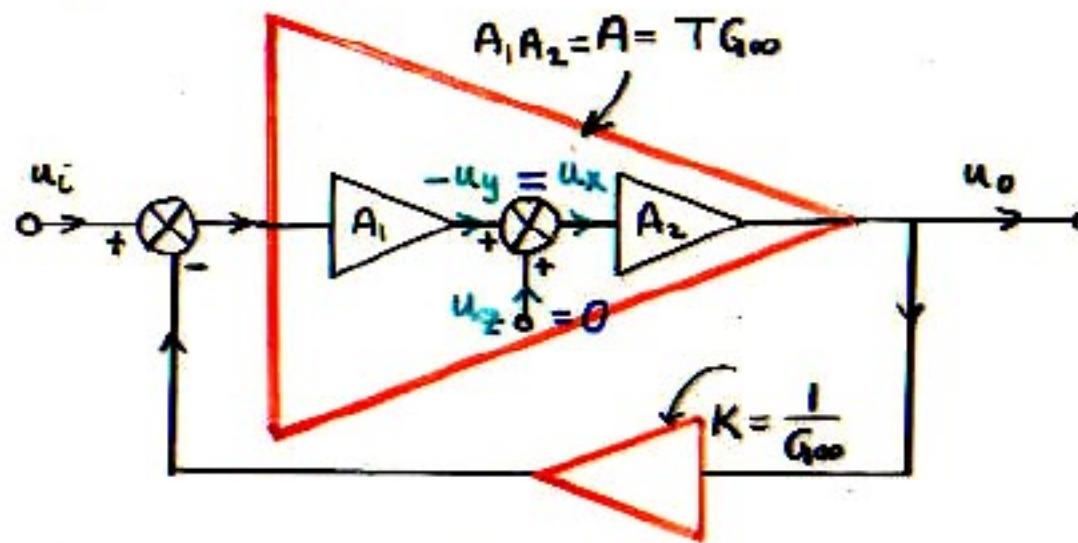Consider a second driving signal u_2 injected into the forward path:




For single injection, u_i only (normal operation):

$$\left. \frac{u_o}{u_i} \right|_{u_2=0} = G = G_{\infty} \frac{T}{1+T} \quad \text{closed-loop gain}$$

Note that $A = TG_{\infty}$ and $K = 1/G_{\infty}$:

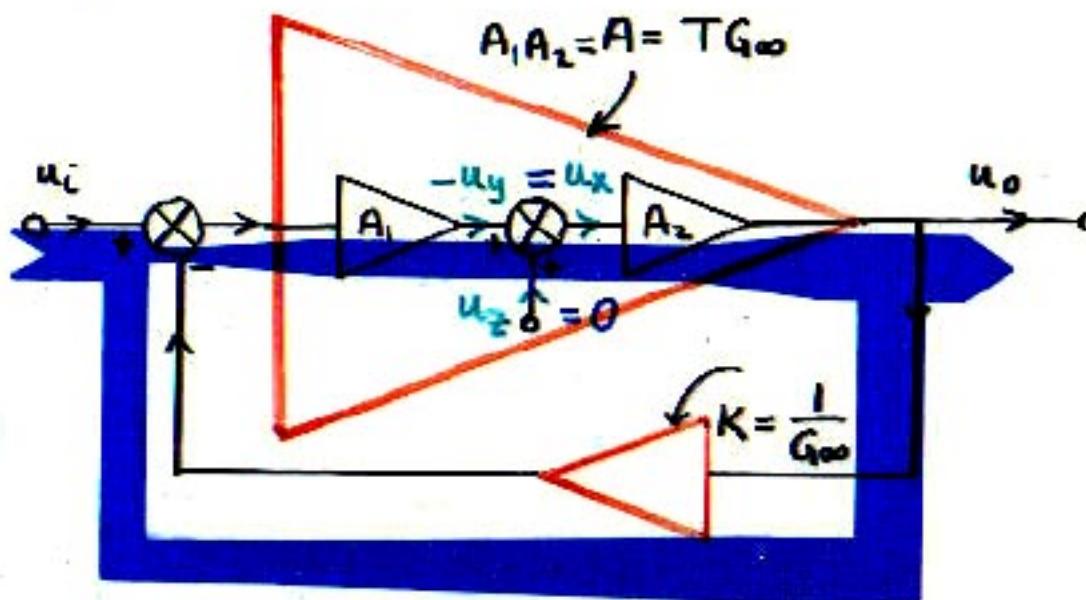Consider a second driving signal u_2 injected into the forward path:




For single injection, u_i only (normal operation):

$$\left. \frac{u_o}{u_i} \right|_{u_2=0} \equiv G = G_{\infty} \frac{T}{1+T} \quad \text{closed-loop gain}$$


Note that $A = TG_{oo}$ and $K = 1/G_{oo}$:

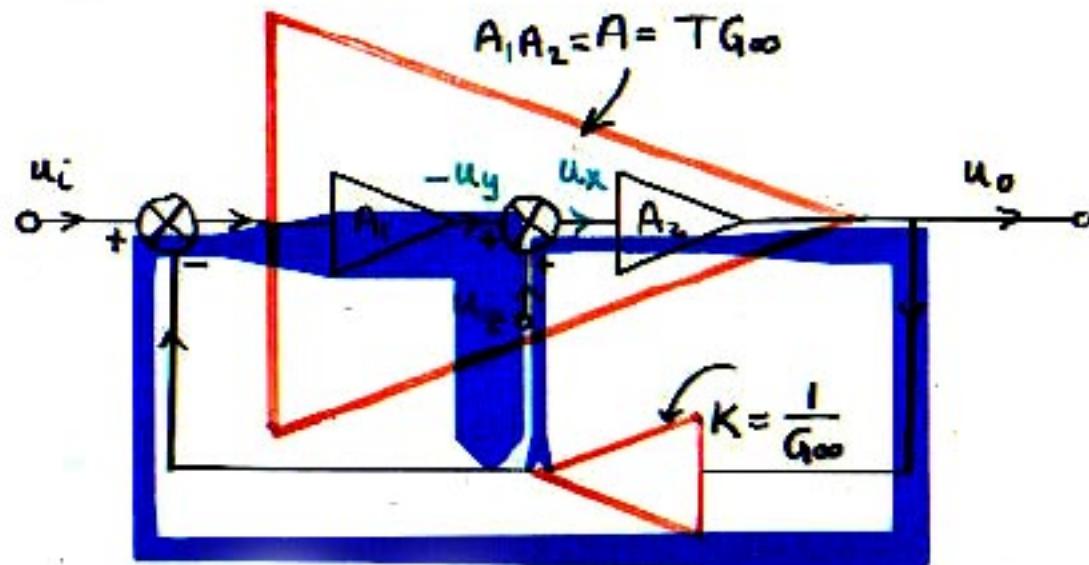Consider a second driving signal u_2 injected into the forward path:



Note that $A = TG_{oo}$ and $K = 1/G_{oo}$:

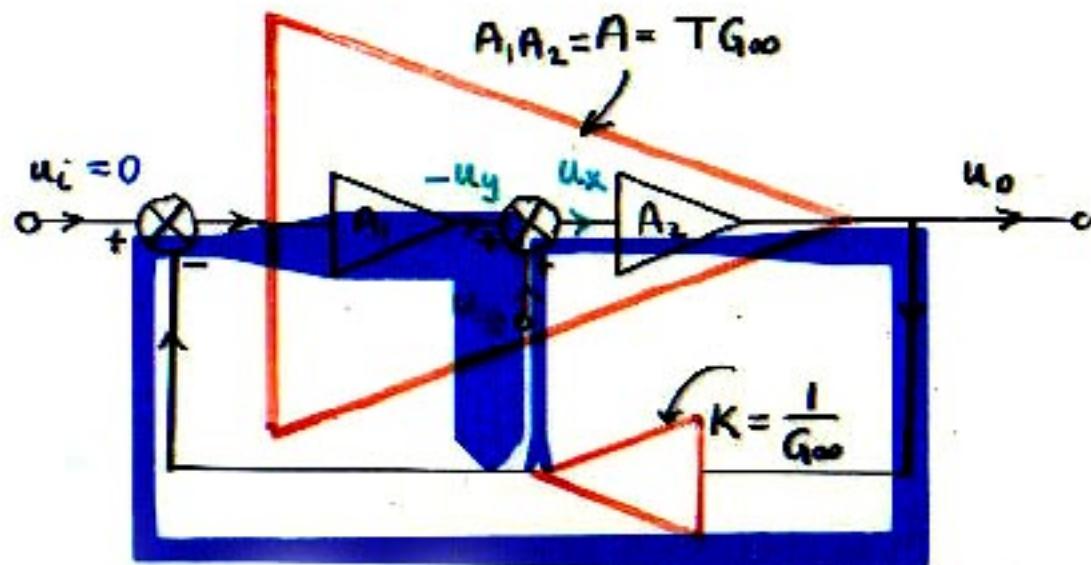Consider a second driving signal u_x injected into the forward path:




For single injection, u_x only,

$$\left. \frac{u_y}{u_x} \right|_{u_i=0} = A_2 K A_1 = A K \equiv T \quad \text{loop gain}$$


Note that $A = TG_{oo}$ and $K = 1/G_{oo}$:

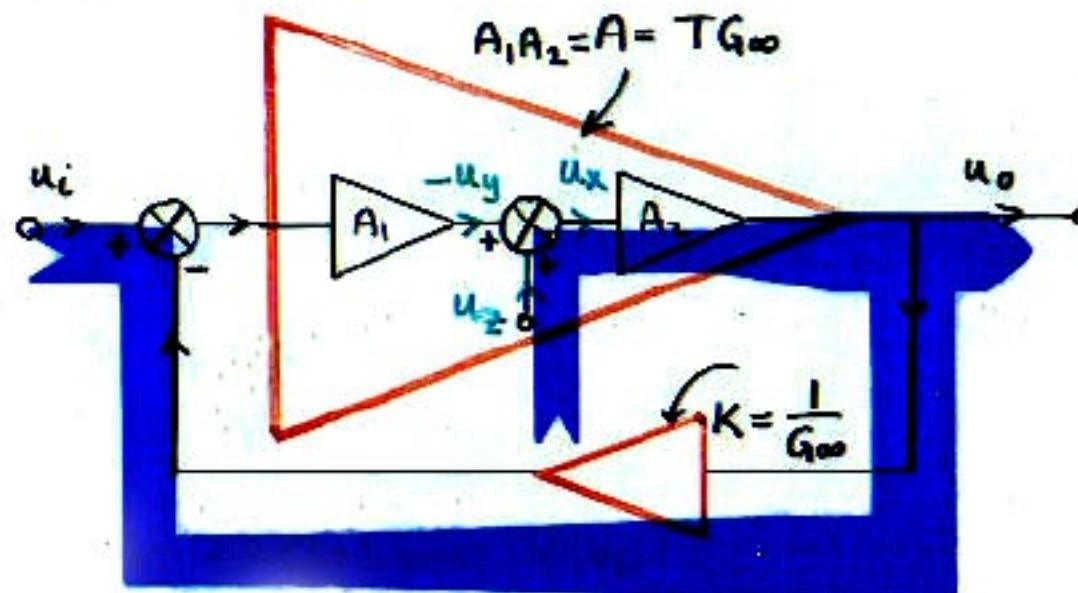Consider a second driving signal u_2 injected into the forward path:



Note that $A = TG_{\infty}$ and $K = 1/G_{\infty}$:

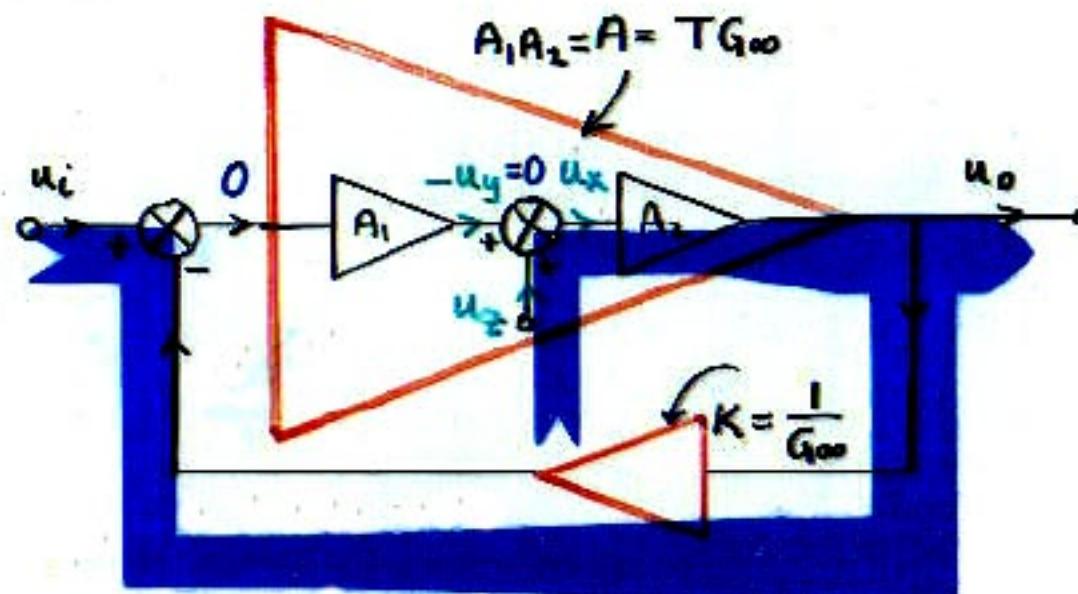Consider a second driving signal u_z injected into the forward path:



For double injection, u_i and u_z , adjusted to null u_y :

$$\left. \frac{u_o}{u_i} \right|_{u_y=0} = \frac{1}{K} = G_{\infty} \quad \text{ideal closed-loop gain}$$

Generalization: The Feedback Theorem

The feedback path does several things:

1. Provides the feedback signal — ideal (desired)
 2. Loads the output
 3. Loads the input
- } nonideal (undesired)

Conventional form of the theorem:

$$G_f = \frac{A}{1+T} \quad \text{where } T = AK$$

Disadvantages:

Breaking the feedback path at the input or the output
disturbs the loading effects.

Recommended form of the theorem:

$$G = G_{\infty} D \quad \text{where } G_{\infty} = \frac{1}{K} \quad D = \frac{T}{1+T}$$

Advantages:


1. G_{∞} and D are directly related to the important properties of the system:

G_{∞} , the Ideal Loop Gain, is the design Specification;
 D , the Discrepancy Factor, must be designed to be close to unity over the specified frequency range.

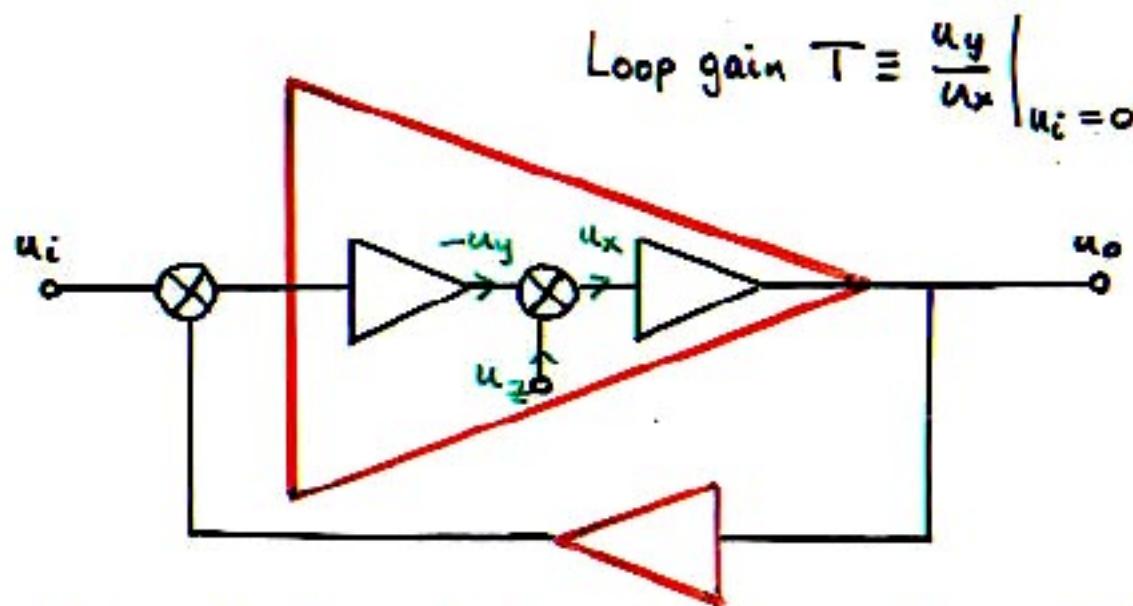2. T can be found by injection of a test signal into the closed loop, without disturbance of the feedback path loading effects, and G_{∞} can be found by Null Double Injection of both the input and a test signal.

NOTE: It is never necessary to know A , the open-loop forward gain: A is always embedded in T , which is why the nonideal loading effects of the feedback path are automatically accounted for.

Implementation of injection of second signal for loop gain determination




Conditions to be satisfied by injection point:

1. Must be inside the feedback loop
2. Injected signal must add to the forward signal without affecting the impedance loading

Two points satisfy these conditions

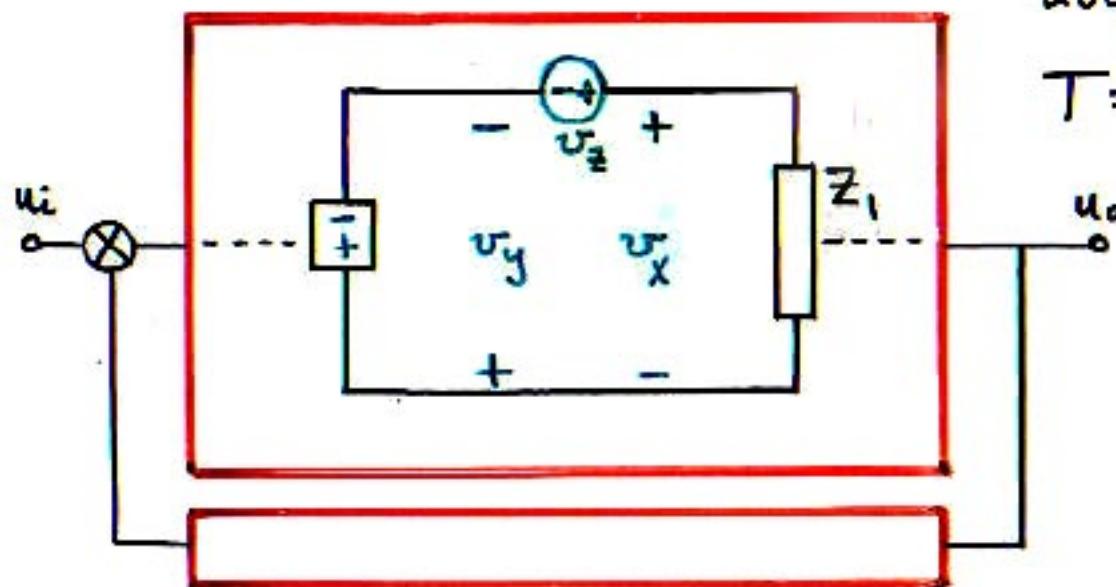1. Inject a voltage in series with a controlled voltage generator:




$$v_z = v_x + v_y$$

Loop gain:

$$T = \frac{v_y}{v_x} \Big|_{u_i=0}$$

Two points satisfy these conditions

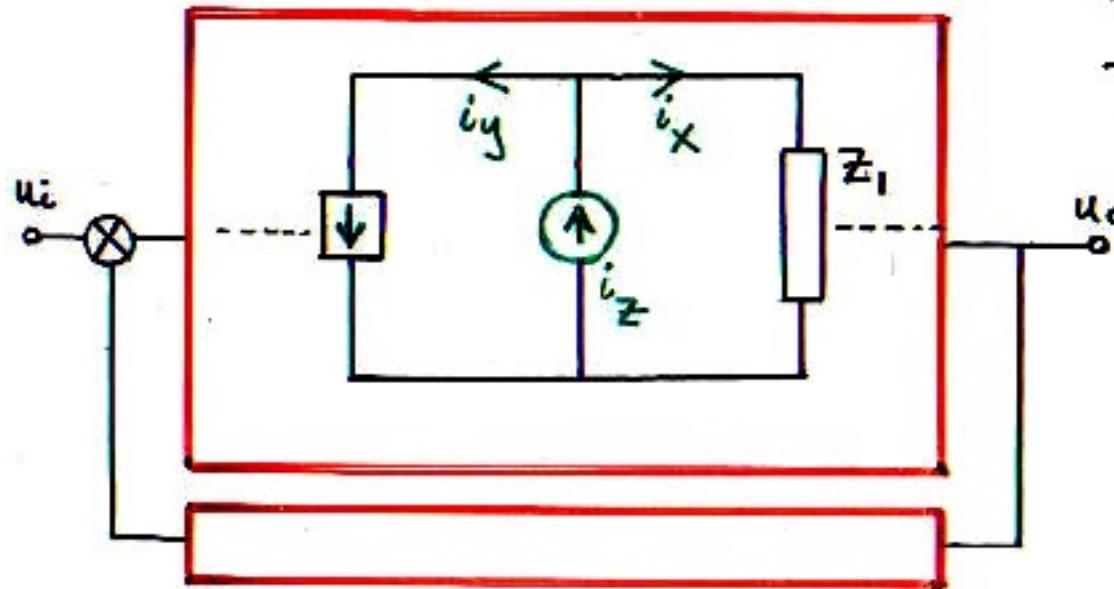2. Inject a current in shunt with a controlled current generator:




$$i_z = i_x + i_y$$

Loop gain:


$$T = \frac{i_y}{i_x} \Big|_{u_i=0}$$

Determination of Feedback System Parameters - Example

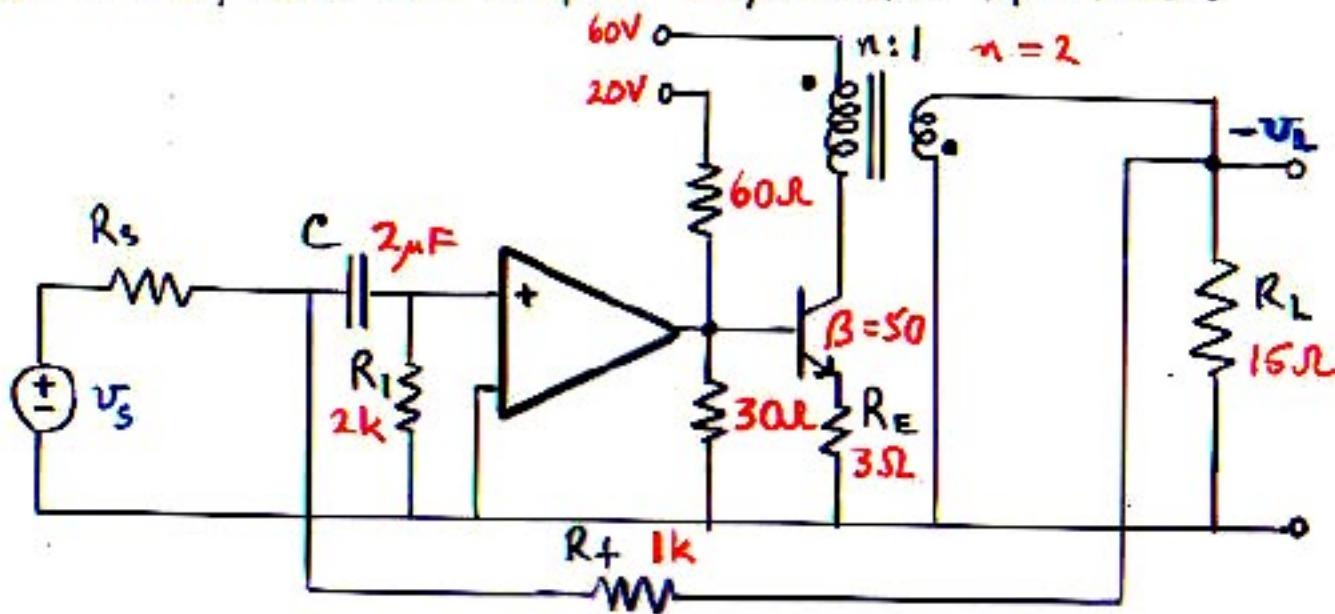Single-ended Class A audio feedback amplifier. The driver opamp has a gain $A_1 = A_{10} / (1 + s/\omega_A)$, where $A_{10} = 8 \text{ dB}$ and $\omega_A = 2 \text{ kHz}$, and an output impedance of 4.5Ω .




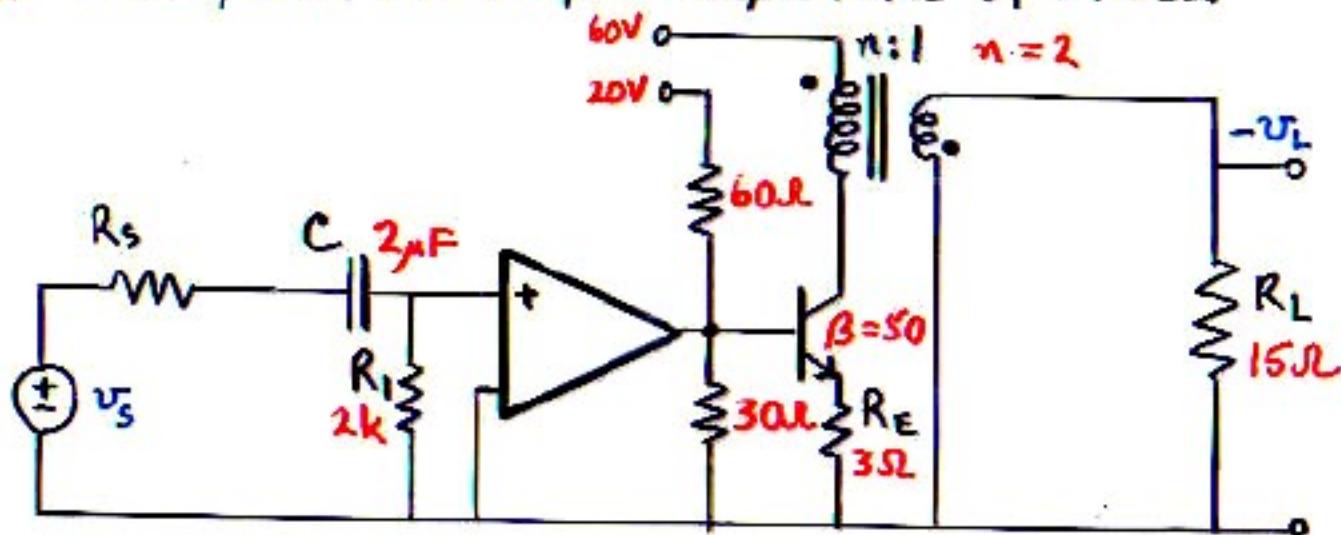Single-ended Class A audio feedback amplifier. The driver opamp has a gain $A_1 = A_{10} / (1 + s/\omega_A)$, where $A_{10} = 8 \text{ dB}$ and $\omega_A = 2 \text{ kHz}$, and an output impedance of 4.5Ω .



The conventional analysis method is to break the loop by opening the feedback path, then calculate A and K separately to get $T = AK$ and $G_f = A/(1+T)$.

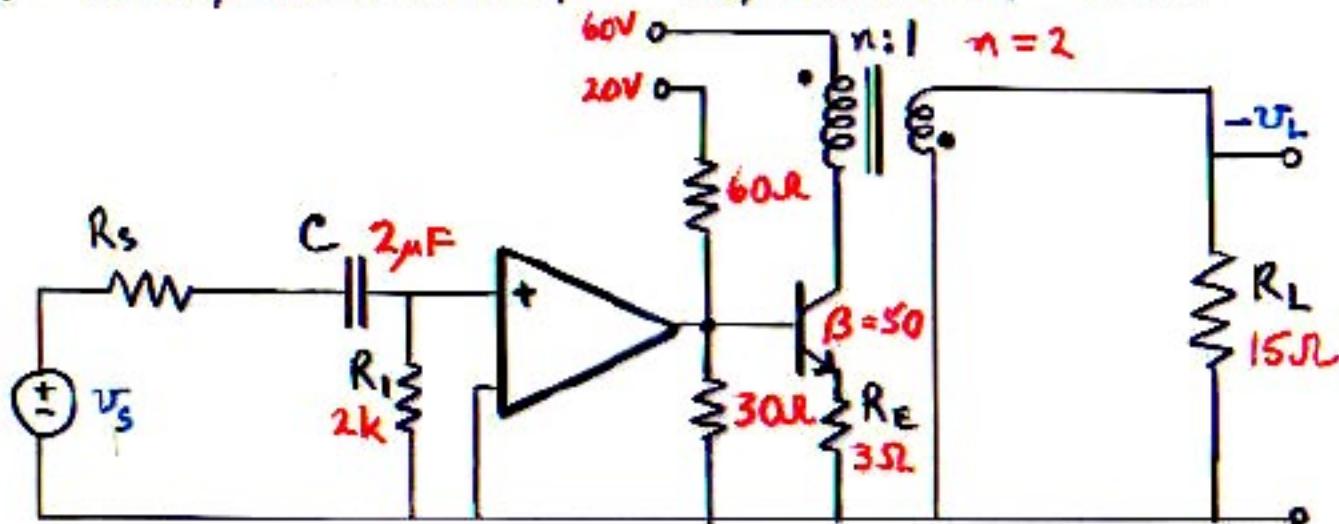
Single-ended Class A audio feedback amplifier. The driver opamp has a gain $A_1 = A_{10} / (1 + s/\omega_A)$, where $A_{10} = 8 \text{ dB}$ and $\omega_A = 2\text{kHz}$, and an output impedance of 4.5Ω .



This is wrong, because loading by the feedback network at output and input is ignored.



The loading could be simulated, but involves guesswork.

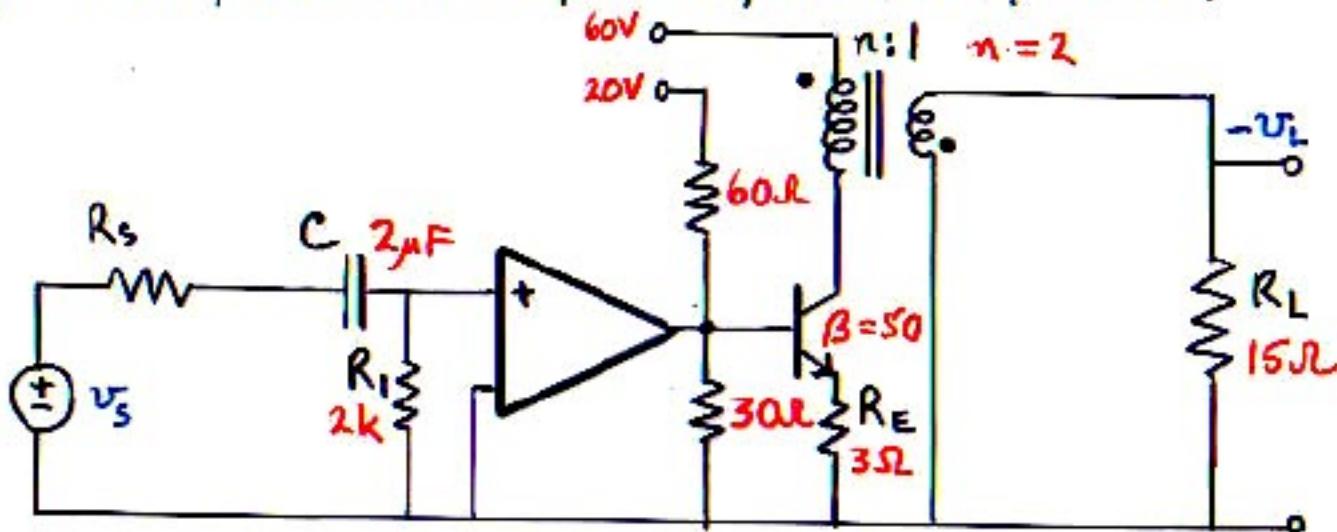
Single-ended Class A audio feedback amplifier. The driver opamp has a gain $A_1 = A_{10} / (1 + s/\omega_A)$, where $A_{10} = 8 \text{ dB}$ and $\omega_A = 2 \text{ kHz}$, and an output impedance of 4.5Ω .



Instead, break the loop in the forward path and find T directly.

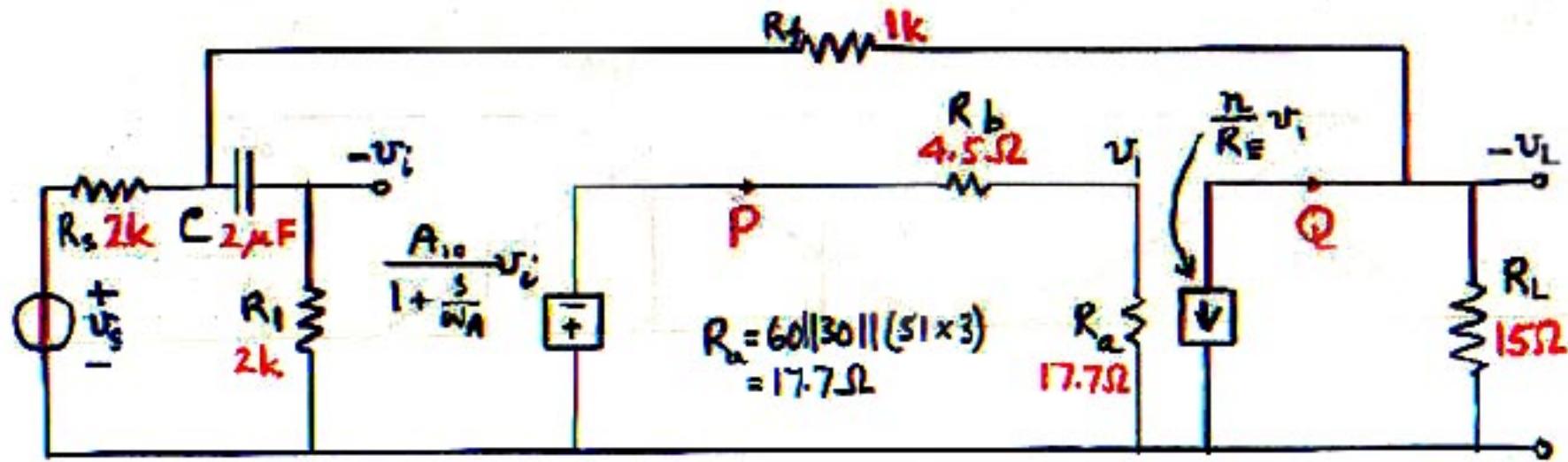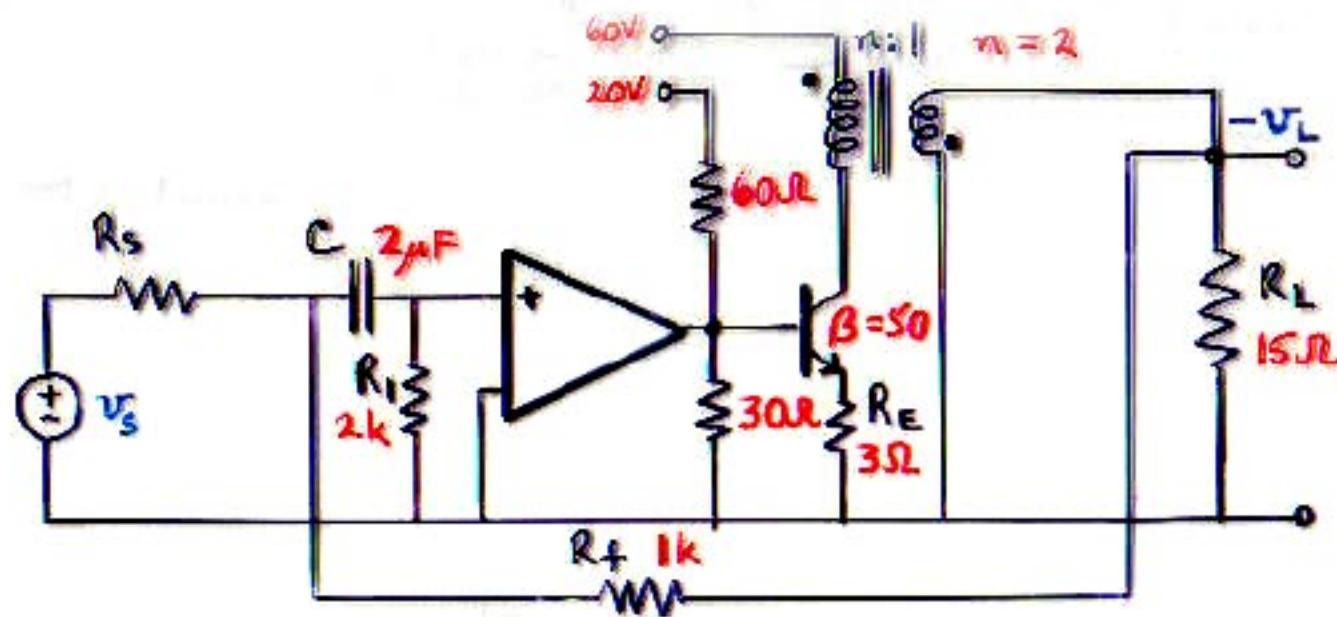First, make an equivalent circuit model of the closed loop.



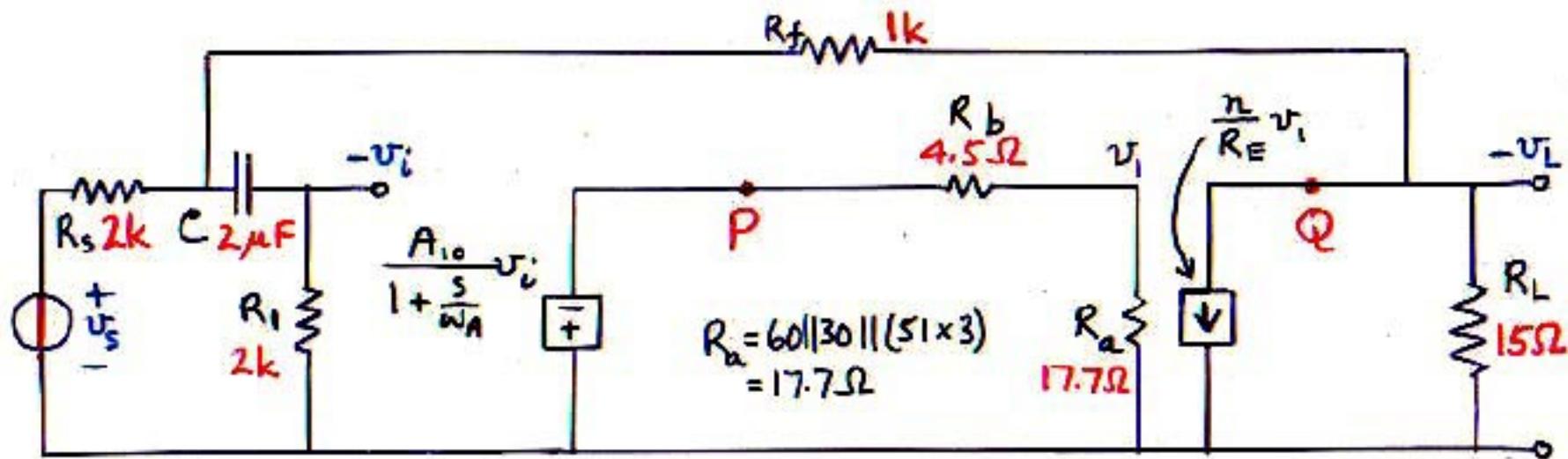


For all calculations concerning loop gain, the input voltage v_s is zero.

Suitable injection points:

Series voltage at point P

Shunt current at point Q

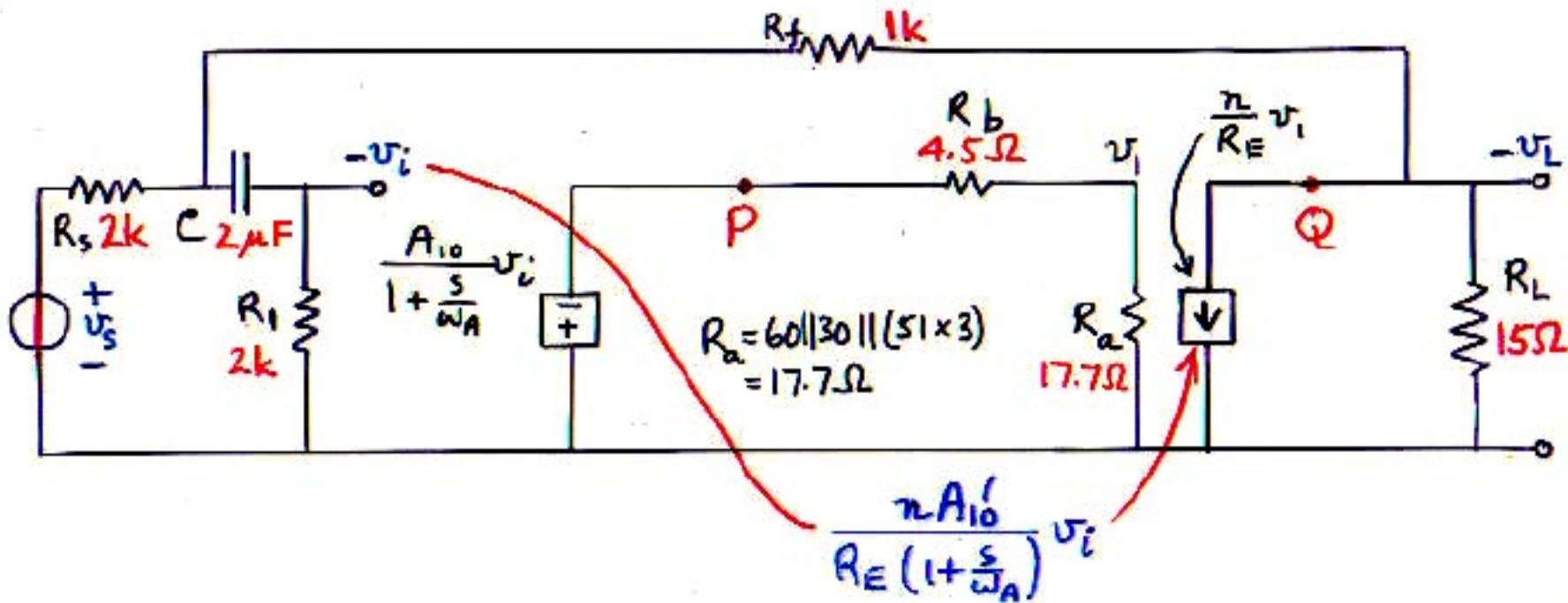


If current injection is chosen, the gain from v_i to the power stage output generator can be condensed into a single factor:

$$\frac{A_{1o}}{1 + \frac{s}{\omega_A}} \frac{R_a}{R_a + R_b} \frac{n}{R_E} v_i = \frac{n A_{1o}'}{R_E (1 + \frac{s}{\omega_A})} v_i$$

where

$$A_{1o}' = A_{1o} \frac{R_a}{R_a + R_b} = 8 \text{dB} \times \frac{17.7}{17.7 + 4.5} = 2.51 \times 0.80$$

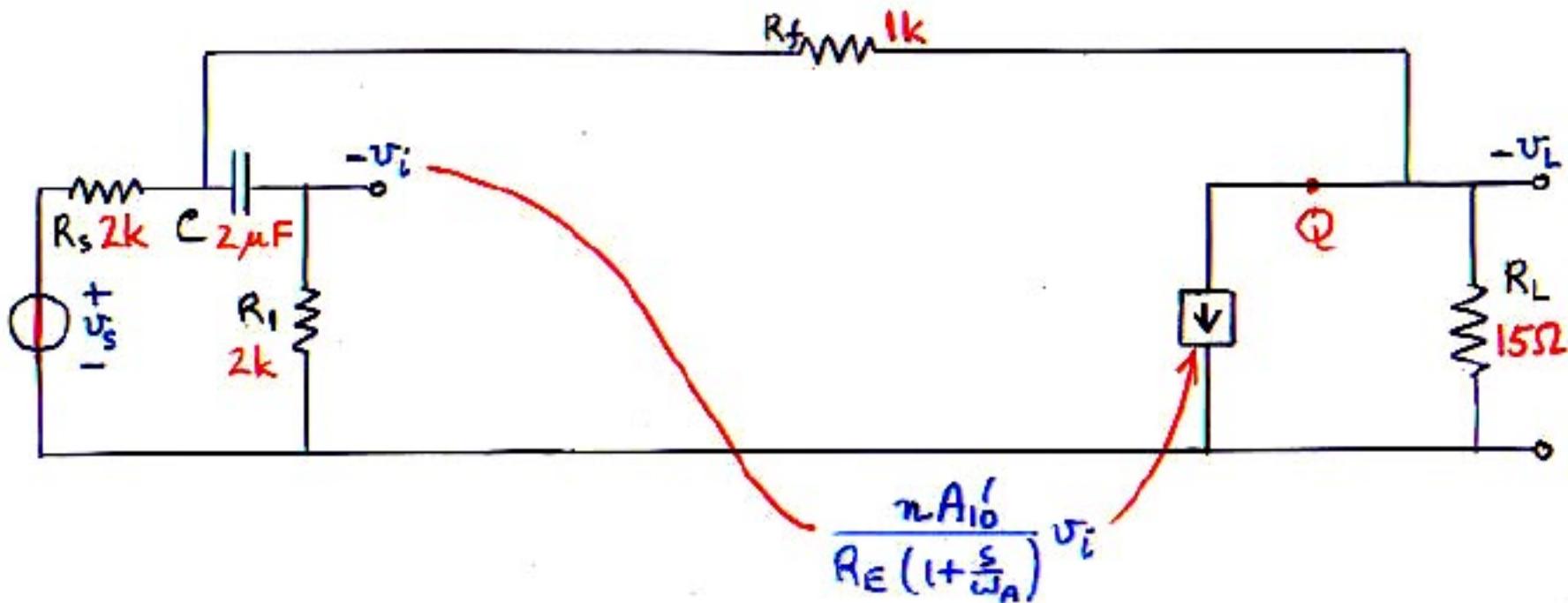is the loaded gain of the opamp. $= 2.0 \Rightarrow 6 \text{dB}$



If current injection is chosen, the gain from v_i to the power stage output generator can be condensed into a single factor:

$$\frac{A_{10}}{1 + \frac{s}{\omega_A}} \frac{R_a}{R_a + R_b} \frac{n}{R_E} v_i = \frac{nA_{10}'}{R_E(1 + \frac{s}{\omega_A})} v_i$$


where

$$A_{10}' \equiv A_{10} \frac{R_a}{R_a + R_b} = 8 \text{dB} \times \frac{17.7}{17.7 + 4.5} = 2.51 \times 0.80$$


is the loaded gain of the opamp.

$$= 2.0 \Rightarrow 6 \text{dB}$$

Ac model

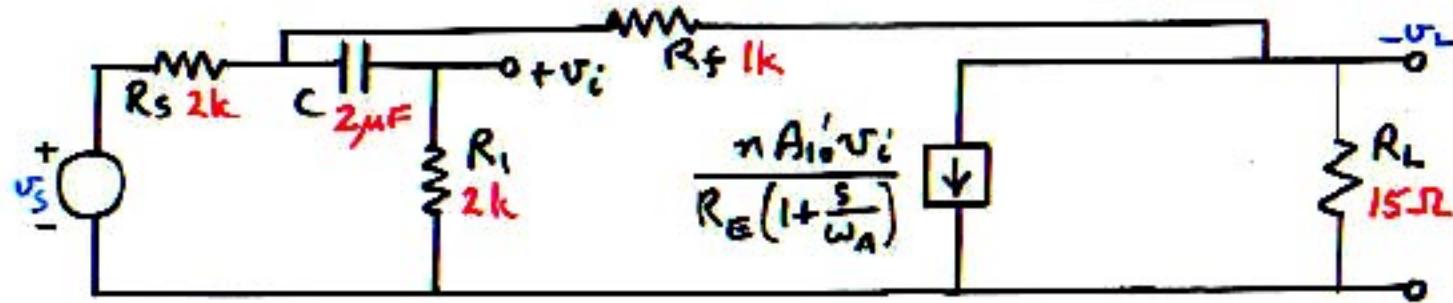


AC model

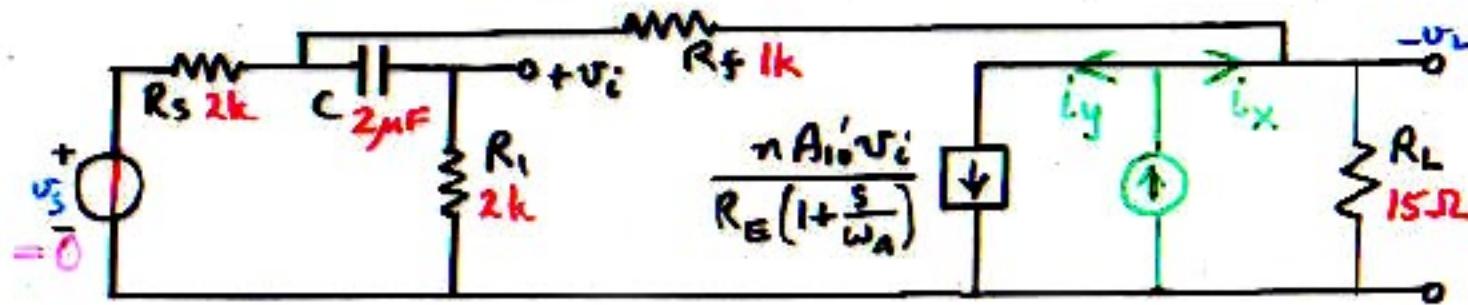

$$T = \left. \frac{i_y}{i_x} \right|_{u_s=0} = \frac{R_L}{R_L + R_f + R_s || R_1 (1 + \frac{\omega_1}{s})} \frac{R_s}{R_s + R_1 (1 + \frac{\omega_1}{s})} \frac{R_1 n A_{10}}{R_g (1 + \frac{s}{\omega_A})}$$

where

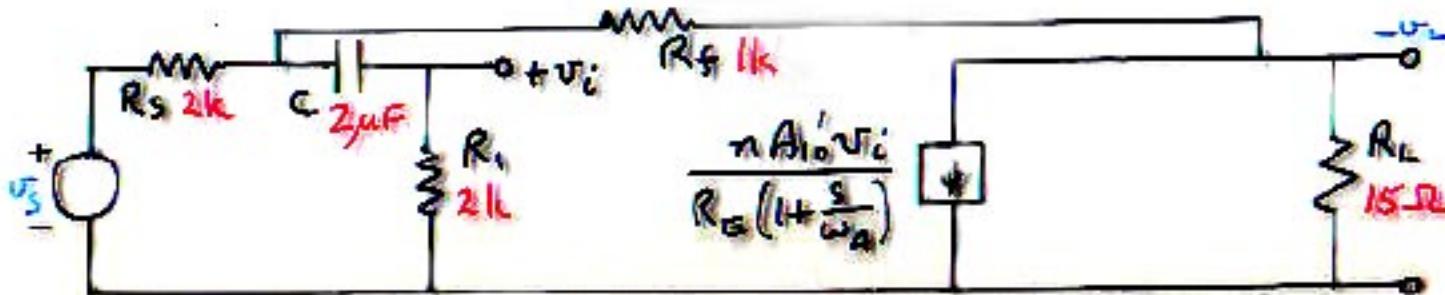
$$\omega_1 = \frac{1}{CR_1} \quad f_1 = \frac{159}{2 \times 2} = 40 \text{ Hz}$$



This method requires additional algebraic force to find the corner frequencies. Therefore, choose Better Method:

First, find \$T_m\$:

$$\begin{aligned}
 T_m &= \left. \frac{i_y}{i_x} \right|_{v_s=0} = \frac{R_L}{R_i + R_f + R_s || R_i} (R_s || R_i) \frac{nA_{10}}{R_E} \\
 &= \frac{(R_s || R_s || R_i) n A_{10} R_L}{R_s R_E} = \frac{0.5 \times 2 \times 2 \times 15}{1 \times 3} \\
 &= 10 \Rightarrow 20 \text{dB}
 \end{aligned}$$

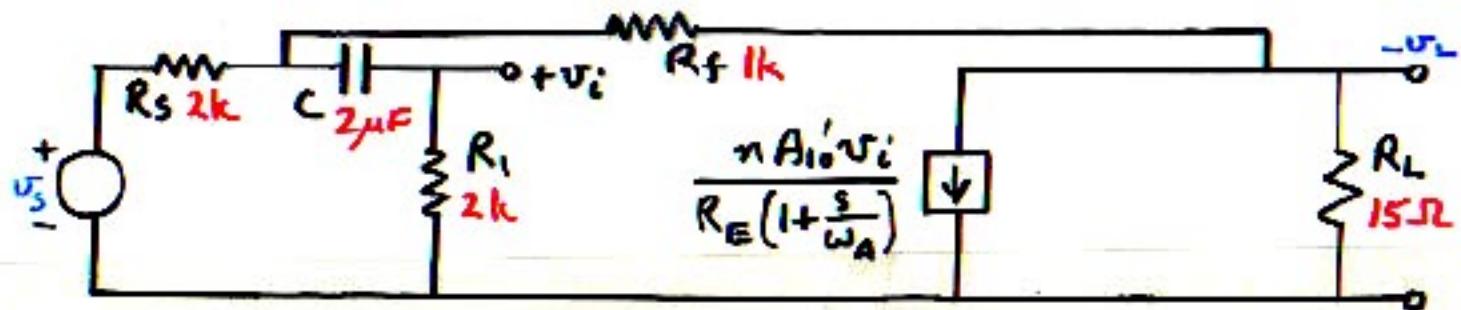

Second, find corner frequencies due to C by use of Extra Element Theorem.

Apply test signal v_x in place of C.

To find $Z_n = R_n$: "input" signal for T ($v_s = 0$)


Adjust v_x in presence of i_x to null i_y
"output" signal for T

Hence: $v_i = 0$, and $R_n = \infty$

To find $Z_d = R_d$:

Apply v_x with $i_x = 0$

Hence: $R_d = (R_L + R_f) \| R_s + R_1$

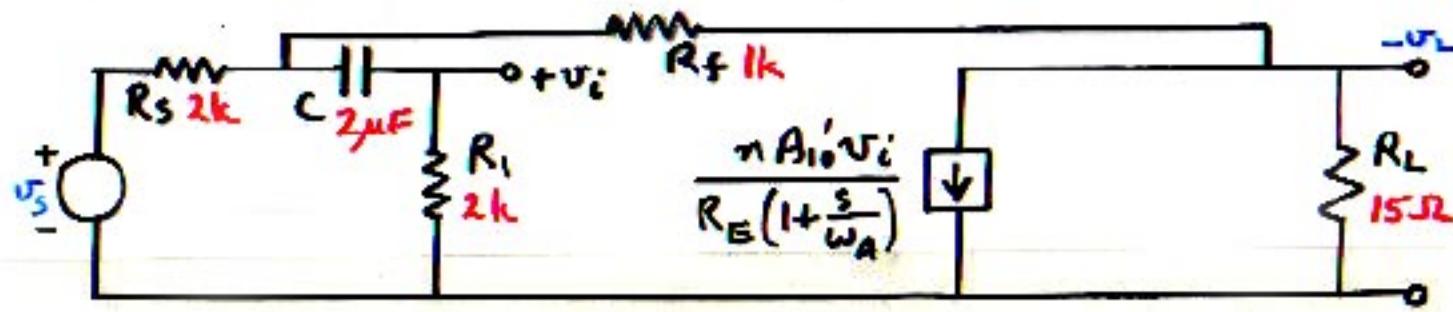

Then:


$$T = T_m \frac{1 + \frac{s}{\omega_n}}{1 + \frac{s}{\omega_d}} \frac{1}{1 + \frac{s}{\omega_A}}$$

↓
 $\frac{1}{SC}$ R_d ∞
 already explicit

$$= T_m \frac{1}{(1 + \frac{\omega_2}{s})(1 + \frac{s}{\omega_A})}$$

where


$$\omega_2 \equiv \frac{1}{CR_d} = \frac{1}{C[R_f || R_s + R_i]} \quad f_2 = \frac{159}{2[1/12 + 2]} = 30\text{Hz}$$

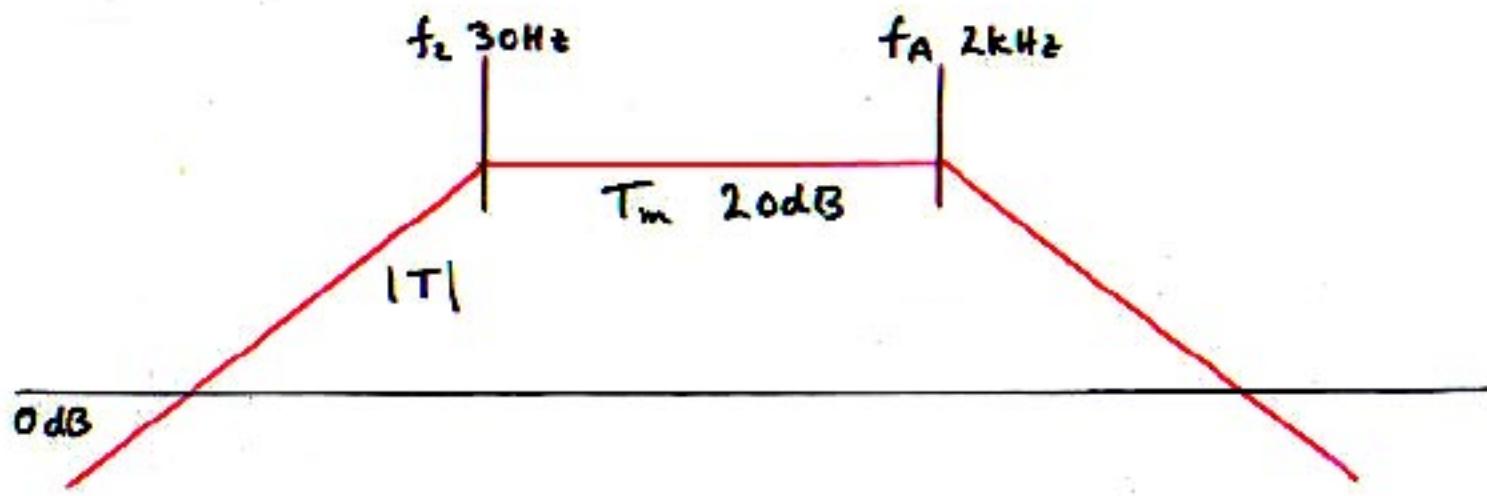


Exercise

By "doing the algebra on the picture," find the analytic pole-zero forms for $F = 1 + T$ and $D = T/(1 + T)$

Ac model

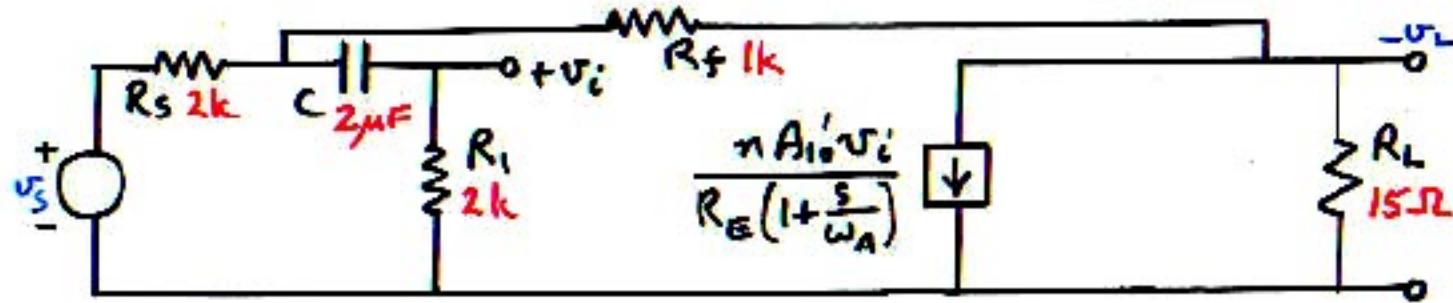


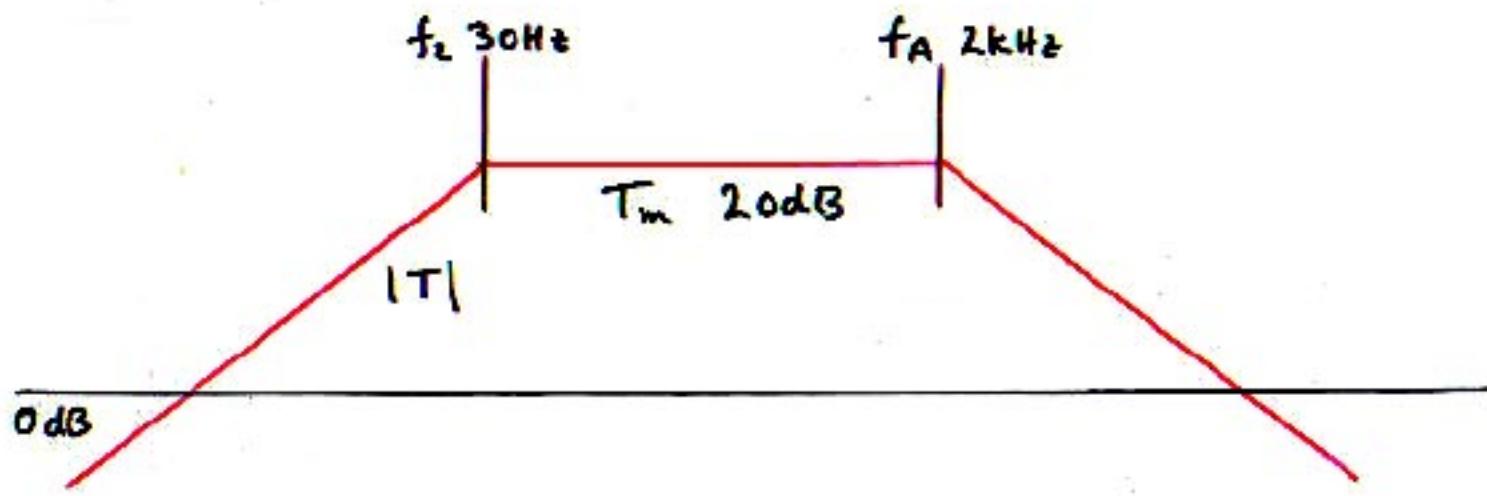

Exercise

By "doing the algebra on the picture," find the analytic pole-zero forms for $F = 1 + T$ and $D = T/(1 + T)$

Exercise Solution

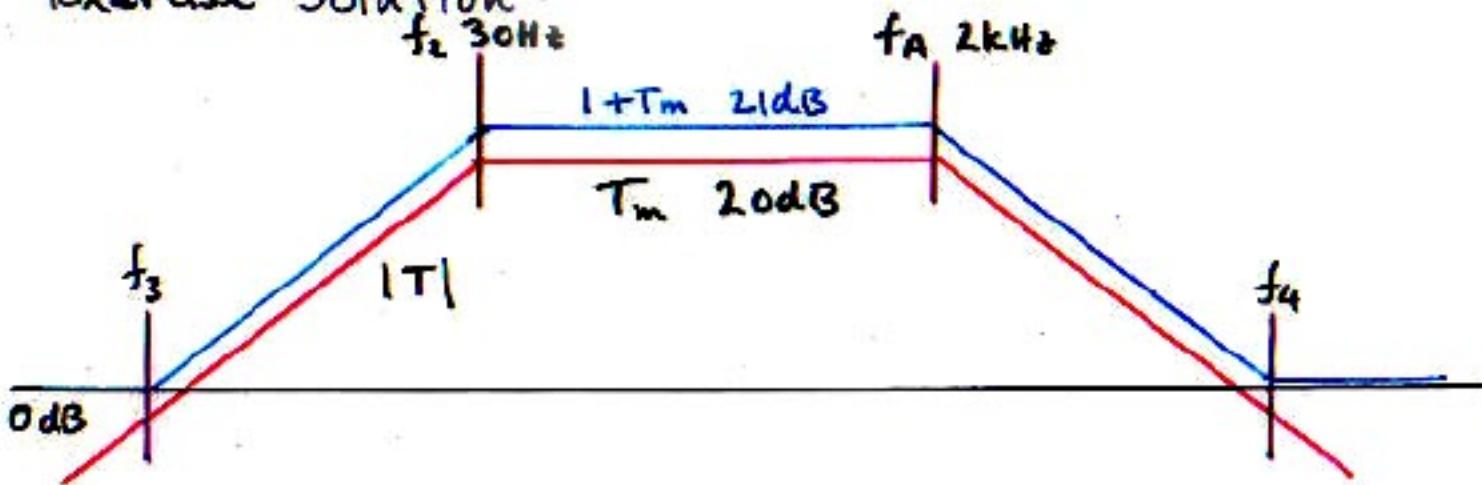

Exercise

By "doing the algebra on the picture," find the analytic pole-zero forms for $F=1+T$ and $D=T/(1+T)$

$$F = (1 + T_m) \frac{(1 + \frac{\omega_3}{s})(1 + \frac{s}{\omega_4})}{(1 + \frac{\omega_2}{s})(1 + \frac{s}{\omega_A})}$$

where $\omega_3 = \frac{\omega_2}{1 + T_m}$ $f_3 = \frac{30}{1 + 10} = 2.7 \text{ Hz}$

$$\omega_4 = (1 + T_m)\omega_A \quad f_4 = 11 \times 2 = 22 \text{ kHz}$$

Calculation of $F = 1 + T$ the Hard Way (by algebra):

$$\begin{aligned}
 F = 1 + T &= 1 + \frac{T_m \frac{s}{\omega_2}}{(1 + \frac{s}{\omega_2})(1 + \frac{s}{\omega_A})} = \frac{(1 + \frac{s}{\omega_2})(1 + \frac{s}{\omega_A}) + T_m \frac{s}{\omega_2}}{(1 + \frac{s}{\omega_2})(1 + \frac{s}{\omega_A})} \\
 &= \frac{1 + \left(\frac{1 + T_m}{\omega_2} + \frac{1}{\omega_A} \right)s + \left(\frac{1}{\omega_2 \omega_A} \right)s^2}{(1 + \frac{s}{\omega_2})(1 + \frac{s}{\omega_A})} \\
 &= \frac{\left(1 + \left[\frac{1}{2} \left(\frac{1 + T_m}{\omega_2} + \frac{1}{\omega_A} \right) + \frac{1}{2} \sqrt{\left(\frac{1 + T_m}{\omega_2} + \frac{1}{\omega_A} \right)^2 - \frac{4}{\omega_2 \omega_A}} \right] s \right) \left(1 + \left[\frac{1}{2} \left(\frac{1 + T_m}{\omega_2} + \frac{1}{\omega_A} \right) - \frac{1}{2} \sqrt{\left(\frac{1 + T_m}{\omega_2} + \frac{1}{\omega_A} \right)^2 - \frac{4}{\omega_2 \omega_A}} \right] s \right)}{(1 + \frac{s}{\omega_2})(1 + \frac{s}{\omega_A})} \\
 &= \frac{\left(1 + \frac{s}{\omega_{z1}} \right) \left(1 + \frac{s}{\omega_{z2}} \right)}{(1 + \frac{s}{\omega_2})(1 + \frac{s}{\omega_A})} = \frac{\omega_2}{\omega_{z1}} \frac{\left(1 + \frac{\omega_{z1}}{s} \right) \left(1 + \frac{s}{\omega_{z2}} \right)}{(1 + \frac{\omega_2}{s})(1 + \frac{s}{\omega_A})}
 \end{aligned}$$

This result gives no insight into the interpretation of the two zeros ω_{z1} and ω_{z2} , or into the midband value $F_m \equiv \frac{\omega_2}{\omega_{z1}}$.

However, a much simpler result is obtained if the approximate real root form is used.

Check the value of $Q^2 = ac/b^2$ for the numerator quadratic of F :

$$Q^2 = \frac{1}{\omega_2 \omega_A \left(\frac{1+T_m}{\omega_2} + \frac{1}{\omega_A} \right)^2} = \frac{\omega_2}{\omega_A (1+T_m)^2 \left(1 + \frac{\omega_2}{\omega_A (1+T_m)} \right)^2} \ll (0.5)^2$$


Hence, the approximate factorization for well-separated real roots can be adopted:

$$\begin{aligned} F &\approx \frac{\left(1 + \left[\frac{1+T_m}{\omega_2} + \cancel{\frac{1}{\omega_A}} \right] s \right) \left(1 + \frac{s}{\omega_2 \omega_A \left[\frac{1+T_m}{\omega_2} + \cancel{\frac{1}{\omega_A}} \right]} \right)}{\left(1 + \frac{s}{\omega_2} \right) \left(1 + \frac{s}{\omega_A} \right)} \\ &= \left(1 + T_m + \cancel{\frac{\omega_2}{\omega_A}} \right) \frac{\left(1 + \frac{\omega_2 / (1+T_m)}{\left[1 + \cancel{\frac{\omega_2}{(1+T_m)\omega_A}} \right] s} \right) \left(1 + \frac{s}{\left[1 + \cancel{\frac{\omega_2}{(1+T_m)\omega_A}} \right] (1+T_m) \omega_A} \right)}{\left(1 + \frac{\omega_2}{s} \right) \left(1 + \frac{s}{\omega_A} \right)} \end{aligned}$$

This is the same result obtained by Doing the Algebra on the Graph.

The algebraic factorization could not have been done at all if T had three or more poles.

Exercise Solution

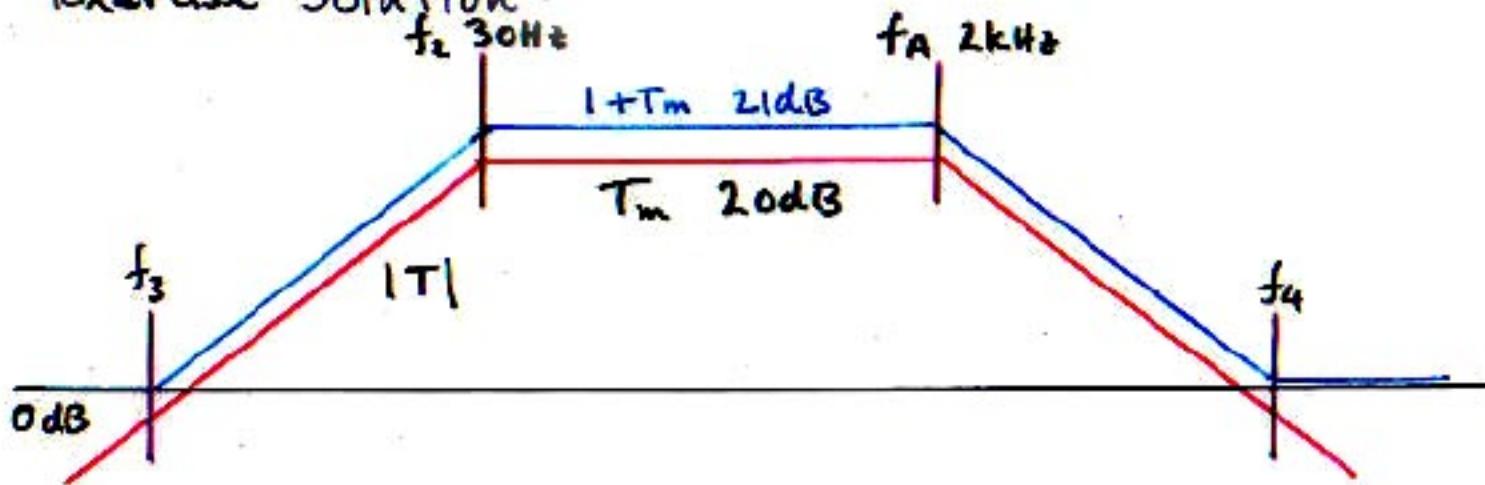


Exercise

By "doing the algebra on the picture," find the analytic pole-zero forms for $F=1+T$ and $D=T/(1+T)$

$$F = (1 + T_m) \frac{(1 + \frac{\omega_3}{s})(1 + \frac{s}{\omega_4})}{(1 + \frac{\omega_2}{s})(1 + \frac{s}{\omega_A})}$$

where $\omega_3 = \frac{\omega_2}{1 + T_m}$ $f_3 = \frac{30}{1 + 10} = 2.7 \text{ Hz}$
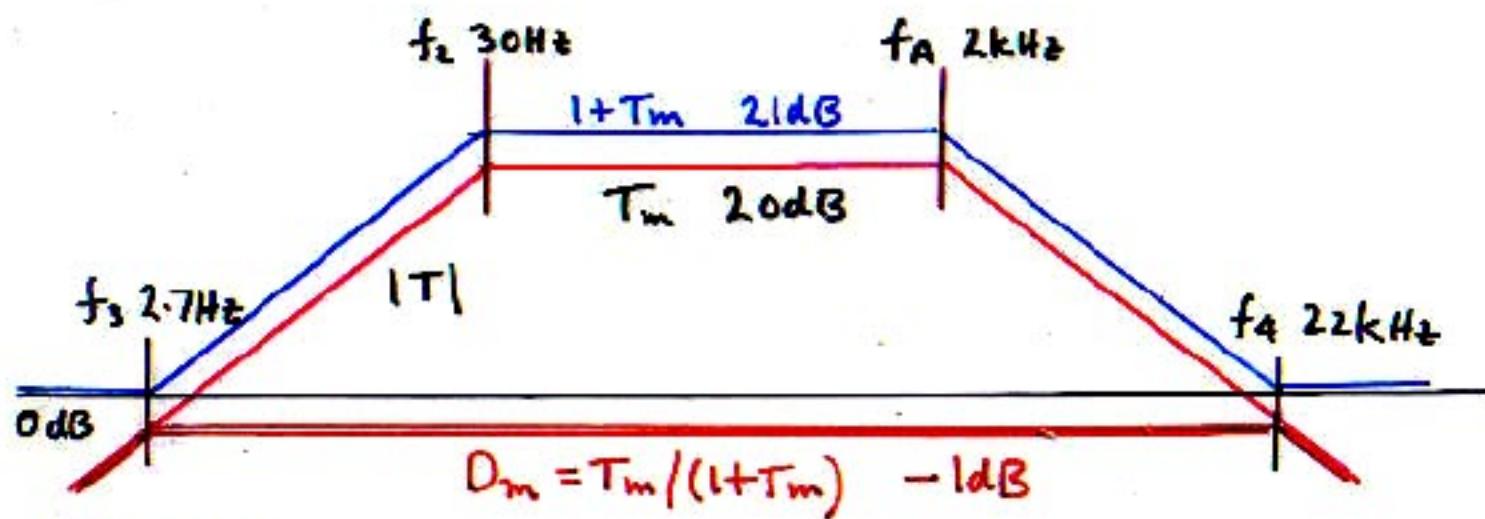
$$\omega_4 = (1 + T_m)\omega_A \quad f_4 = 11 \times 2 = 22 \text{ kHz}$$




Exercise

By "doing the algebra on the picture," find the analytic pole-zero forms for $F = 1 + T$ and $D = T/(1 + T)$

$$D = \frac{T_m}{1 + T_m} \cdot \frac{1}{\left(1 + \frac{\omega_3}{s}\right)\left(1 + \frac{s}{\omega_4}\right)}$$

Ac model
Exercise



Find G_{∞}

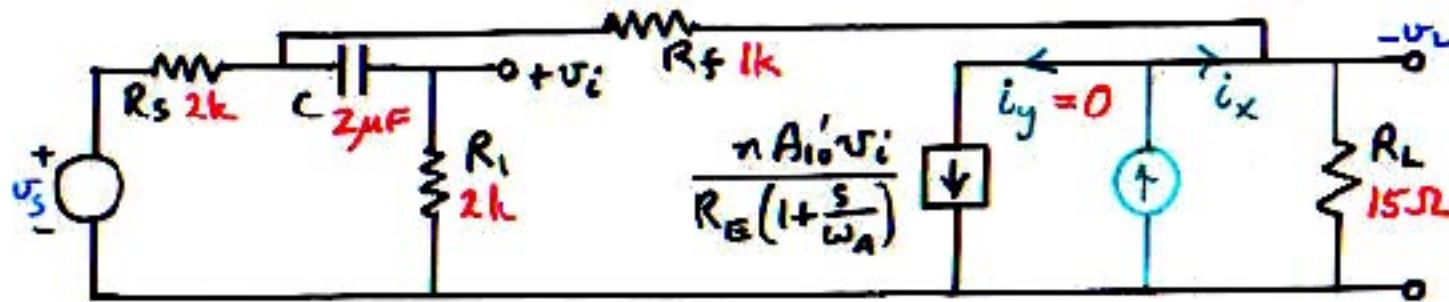

$$\frac{nA_{10}'U_i}{R_E(1 + \frac{s}{\omega_A})}$$

Ac model
Exercise


Find $G_{1\infty}$

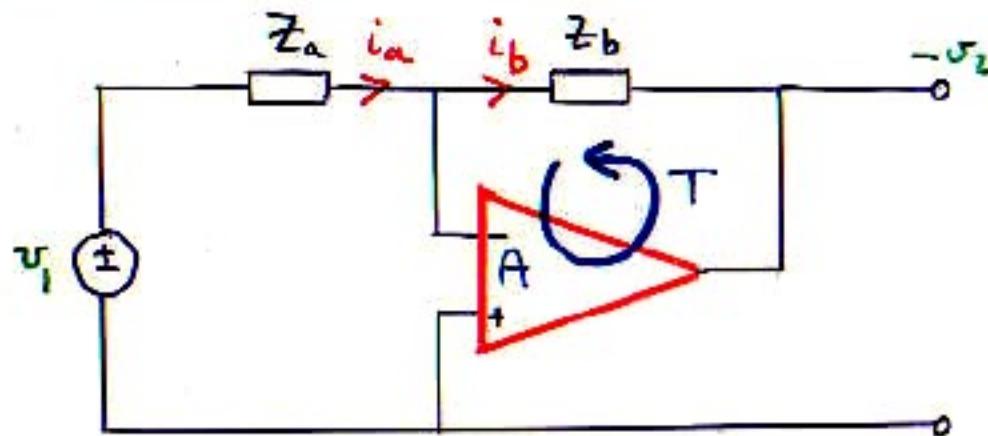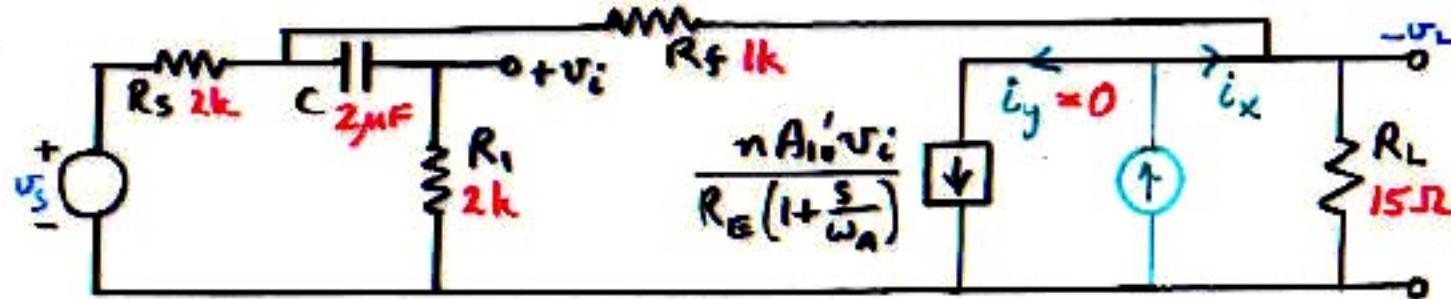

Ac model

Exercise Solution


$$G_{\infty} = \frac{v_L}{v_s} \Big|_{i_y=0}$$

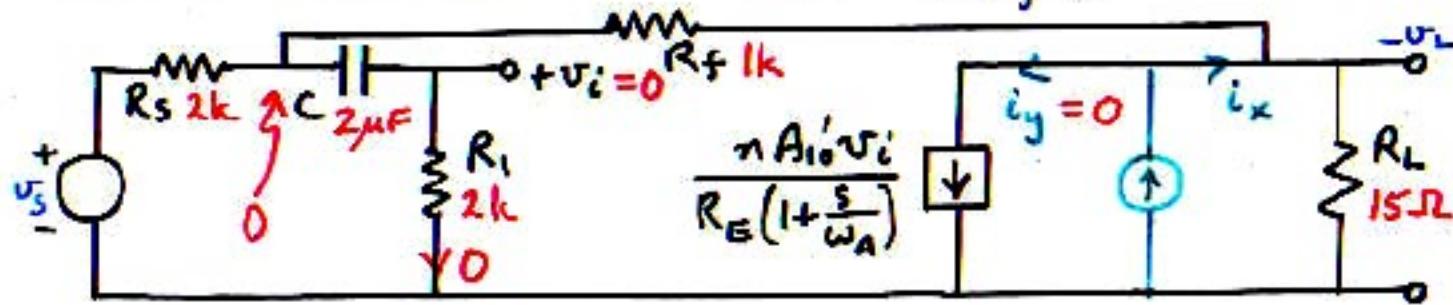

$$\frac{v_s}{R_s} = \frac{v_L}{R_f}$$

$$G_{\infty} = \frac{R_f}{R_s} = \frac{1}{2} \Rightarrow -6dB$$

Hence the closed-loop gain G_1 is

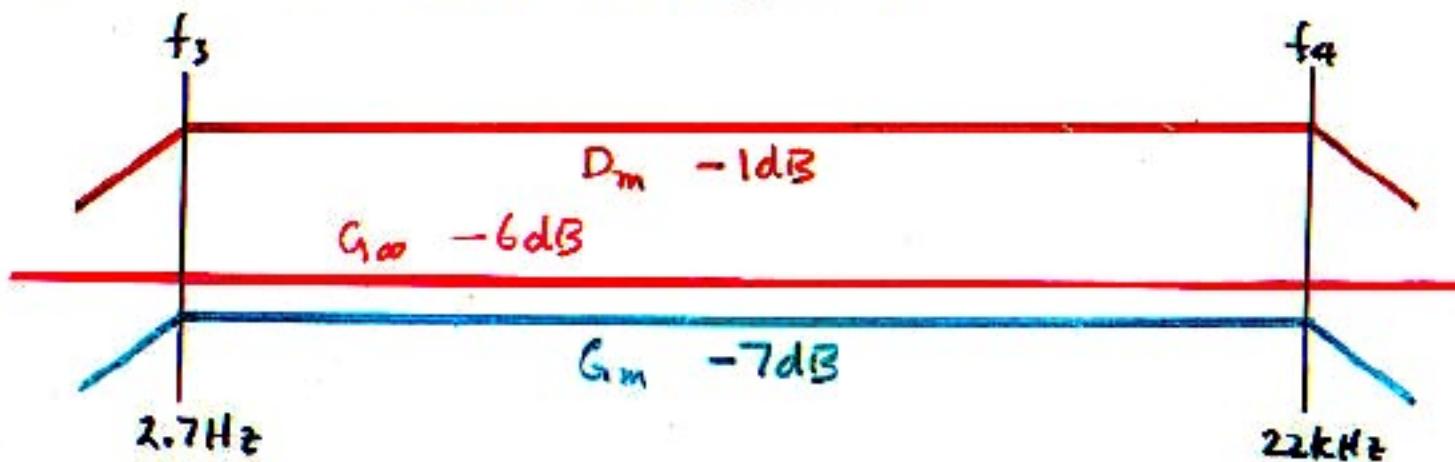





$$G_1 = G_m \frac{1}{(1 + \frac{\omega_3}{s})(1 + \frac{s}{\omega_4})}$$

Generalization: Two Conditions for Injection of a Test Signal
into a Closed Loop

1. Must be inside the feedback loop
2. Injected signal must add to the forward signal without affecting the impedance loading


Condition 2 can be met by injection of a voltage in series with a dependent voltage source, or by injection of a current in parallel with a current source.

Ideal amplifiers

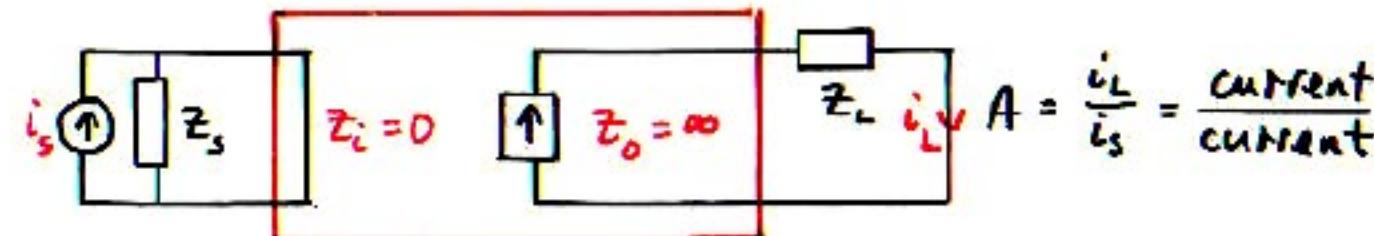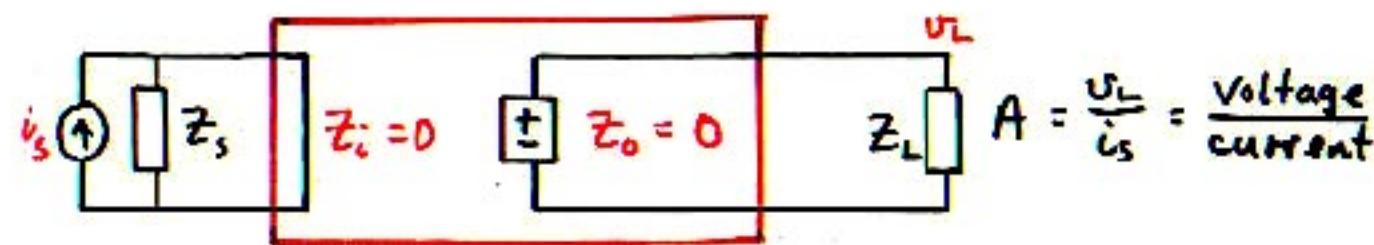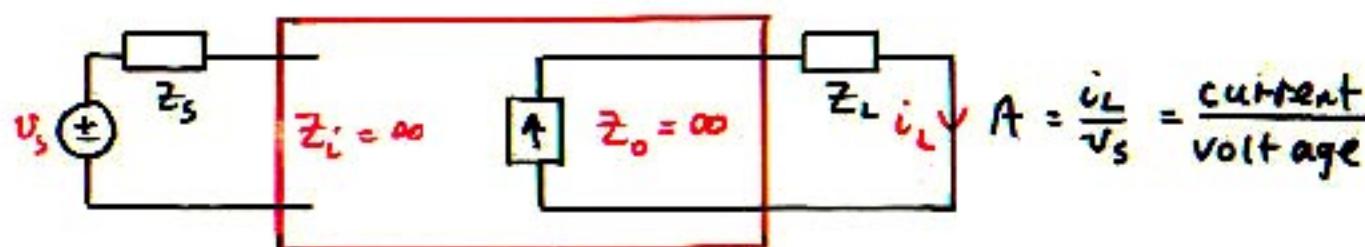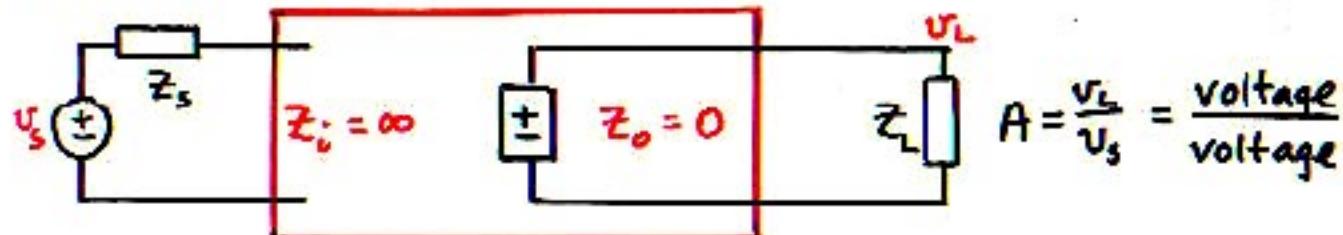


In the ideal cases, the gain is independent of z_s and z_L

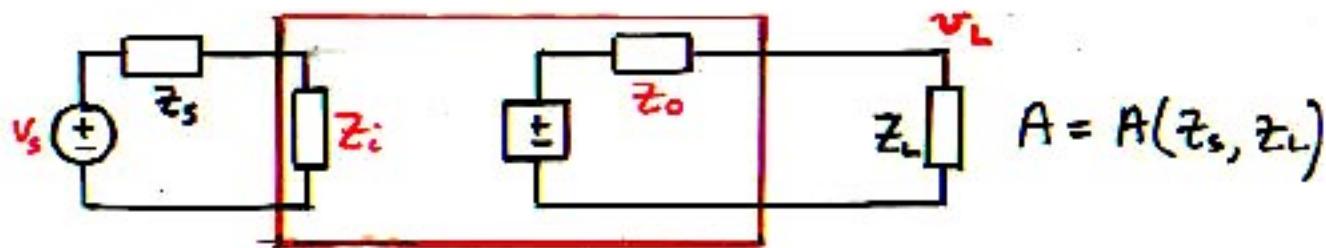
A practical amplifier is not ideal, and the gain does depend on z_s and z_L :



However, an appropriate connection of feedback can make a nonideal amplifier approach more closely the properties of any one of the ideal amplifiers.

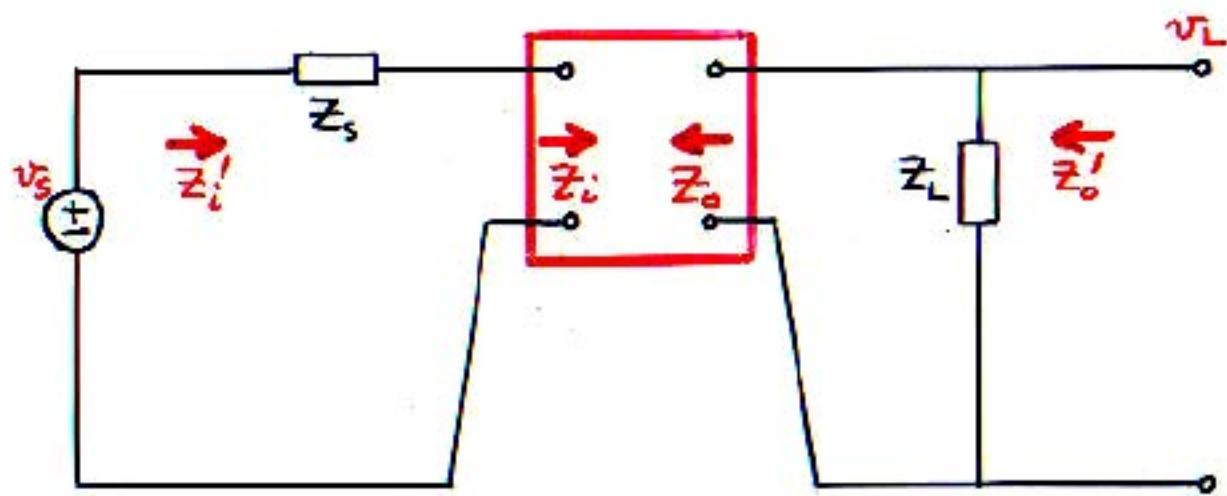Feedback causes the closed-loop gain G_1 to approach the reciprocal feedback ratio $1/K = G_{\infty}$. Thus, G_{∞} must be designed to have the same current or voltage transfer properties as the desired ideal amplifier.



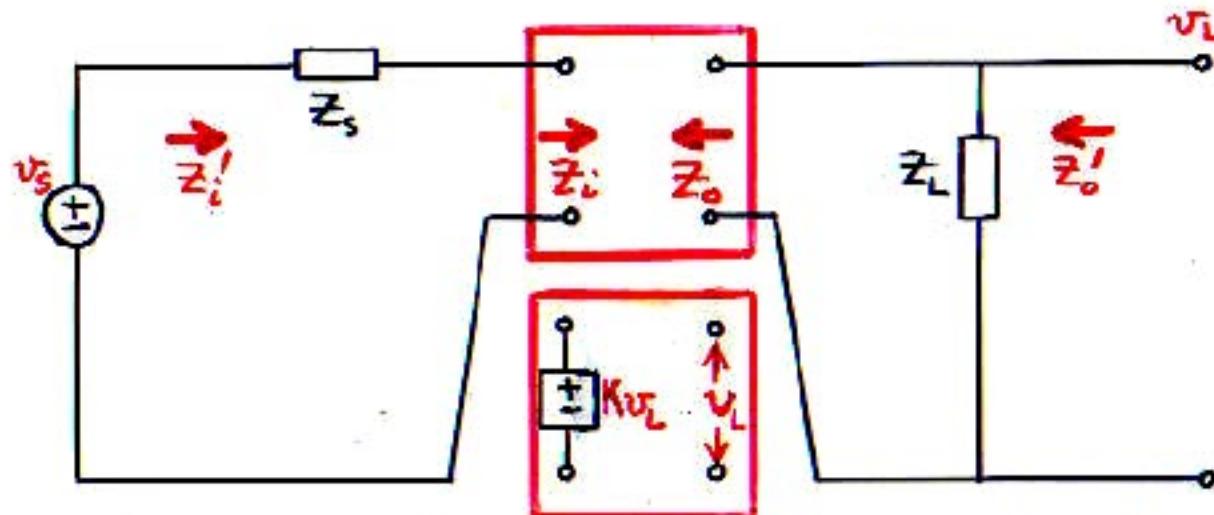


Ideal feedback path must "sense" output voltage and convert it to a feedback voltage. Voltage summing is done in series.

$$G = \frac{v_L}{v_s} = \frac{\text{Voltage}}{\text{Voltage}} = \frac{A}{1+T} = G_{\infty} \frac{T}{1+T}$$


where

$$A = \left. \frac{v_L}{v_s} \right|_{K=1/G_{\infty} = 0}$$

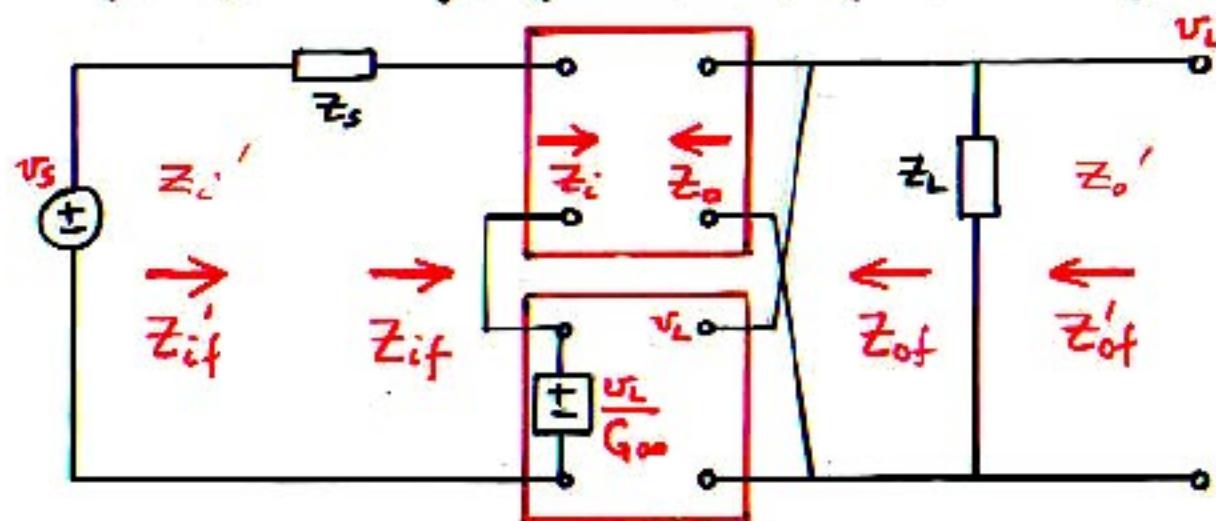1. Voltage - to - voltage (series voltage feedback)



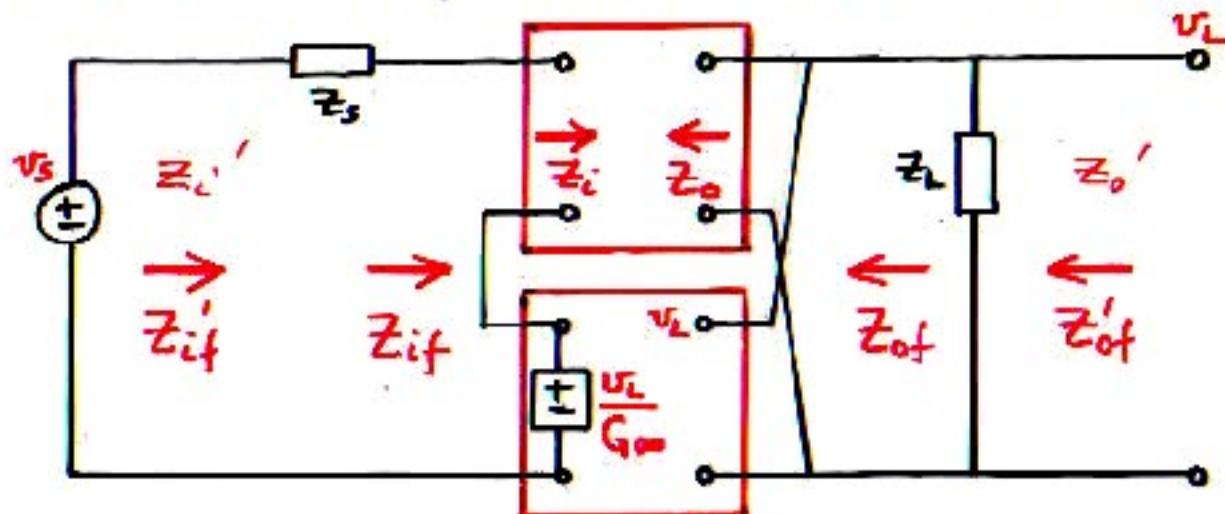1. Voltage - to - voltage (series voltage feedback)



$$Z_{of}' = \frac{G}{\left. \frac{G}{z_L} \right|_{z_L \rightarrow 0}} = \frac{\frac{A}{1+T}}{\left. \frac{A}{z_L} \right|_{z_L \rightarrow 0} \frac{1}{1+T} \left. \frac{1}{z_L} \right|_{z_L \rightarrow 0}} = \frac{A}{\left. A \right|_{z_L \rightarrow 0}} \frac{1+T \left. \frac{1}{z_L} \right|_{z_L \rightarrow 0}}{1+T} = \frac{z_o'}{1+T}$$

$$Z_{of} = \frac{z_o}{1+T \left. \frac{1}{z_L} \right|_{z_L \rightarrow \infty}}$$

OR:

$$Z_{of}' = \frac{G_\infty \frac{T}{1+T}}{\left. G_\infty \frac{T}{z_L} \right|_{z_L \rightarrow 0} \frac{1}{1+T \left. \frac{1}{z_L} \right|_{z_L \rightarrow 0}}} = \frac{T}{1+T} \left[\left. \frac{z_L}{T} \right|_{z_L \rightarrow 0} \right]$$


$$Z_{of} = \frac{T}{1+T} \left. \left[\frac{z_L}{T} \right] \right|_{z_L \rightarrow \infty}$$

Outside output impedance is reduced by the factor $1+T$.

Inside output impedance is reduced by the factor $|1+T|_{z_o \rightarrow \infty}$,
which is larger than $1+T$.

Outside and inside output impedances Z_{of}' and Z_{if}'
can each be found directly from the loop gain T .
They are almost equal (for large T), hence both
are much smaller than Z_L .

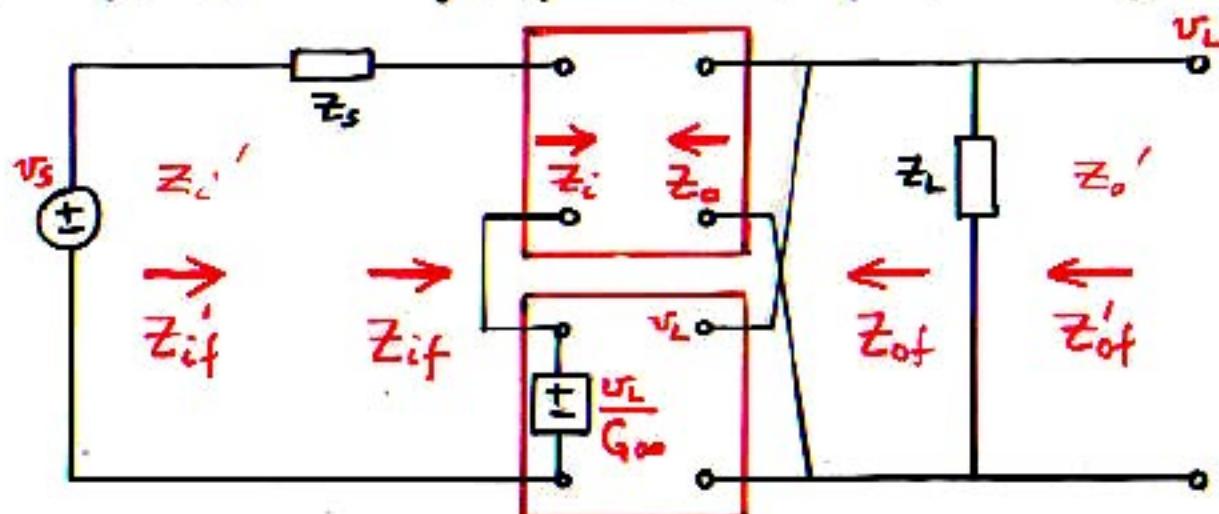1. Voltage - to - voltage (series voltage feedback)



$$Z_{if}' = \frac{z_s G|_{z_s \rightarrow \infty}}{G} = \frac{\frac{z_s A|_{z_s \rightarrow \infty}}{1 + T|_{z_s \rightarrow \infty}}}{\frac{A}{1 + T}} = \frac{z_s A|_{z_s \rightarrow \infty}}{A} \frac{1 + T}{1 + T|_{z_s \rightarrow \infty}} = z_i'(1 + T)$$

$$Z_{if} = Z_i(1 + T|_{z_s \rightarrow 0})$$

OR:

$$Z_{if}' = \frac{G_\infty \frac{z_s T|_{z_s \rightarrow \infty}}{1 + T|_{z_s \rightarrow \infty}}}{G_\infty \frac{T}{1 + T}} = \frac{1 + T}{T} [z_s T|_{z_s \rightarrow \infty}]$$

$$Z_{if} = \frac{1 + T}{T} \Big|_{z_s \rightarrow 0} [z_s T|_{z_s \rightarrow \infty}]$$

Outside input impedance is increased by the factor $1+T$.


Inside input impedance is increased by the factor $|1+T|_{z_s \geq 0}$
which is larger than $1+T$.

Outside and inside input impedances Z_{if}' and Z_{if}
can each be found directly from the loop gain T .
They are almost equal (for large T), hence both
are much larger than Z_s .

Bottom Line:

The input and output impedances of a feedback amplifier can be found from a knowledge solely of the loop gain, which further emphasizes the fact that the loop gain T is the single central, important property of a feedback amplifier.

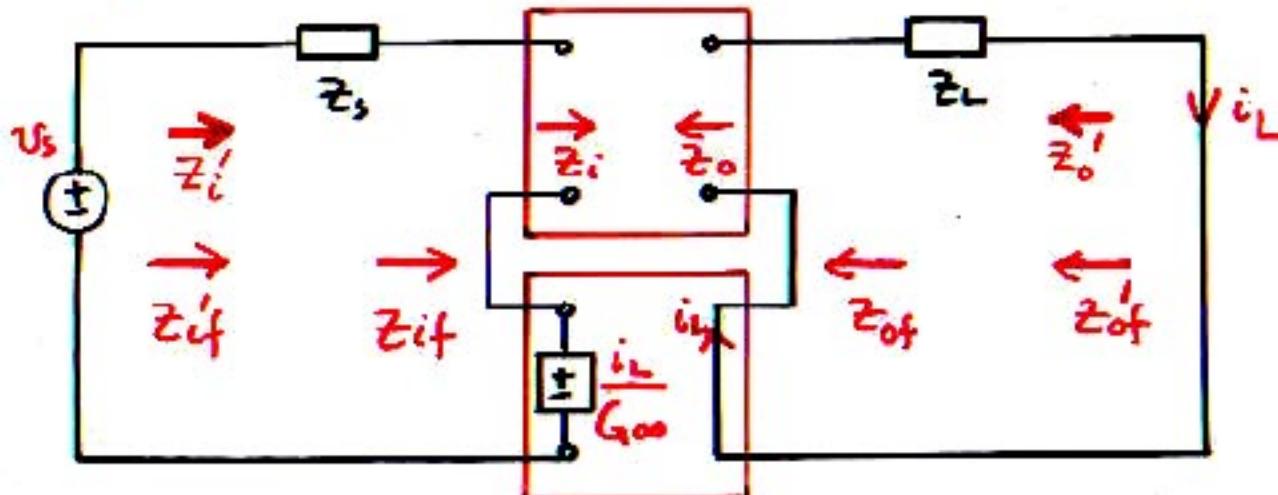2. Voltage -to -current (Series current feedback)




Ideal feedback path must "sense" output current and convert it to a feedback voltage. Voltage summing is done in series.

$$G = \frac{i_L}{U_s} = \frac{\text{Current}}{\text{Voltage}} = \frac{A}{1+T} = G_{oo} \frac{T}{1+T}$$

where

$$A = \left. \frac{i_L}{U_s} \right|_{K=1/G_{oo}=0}$$

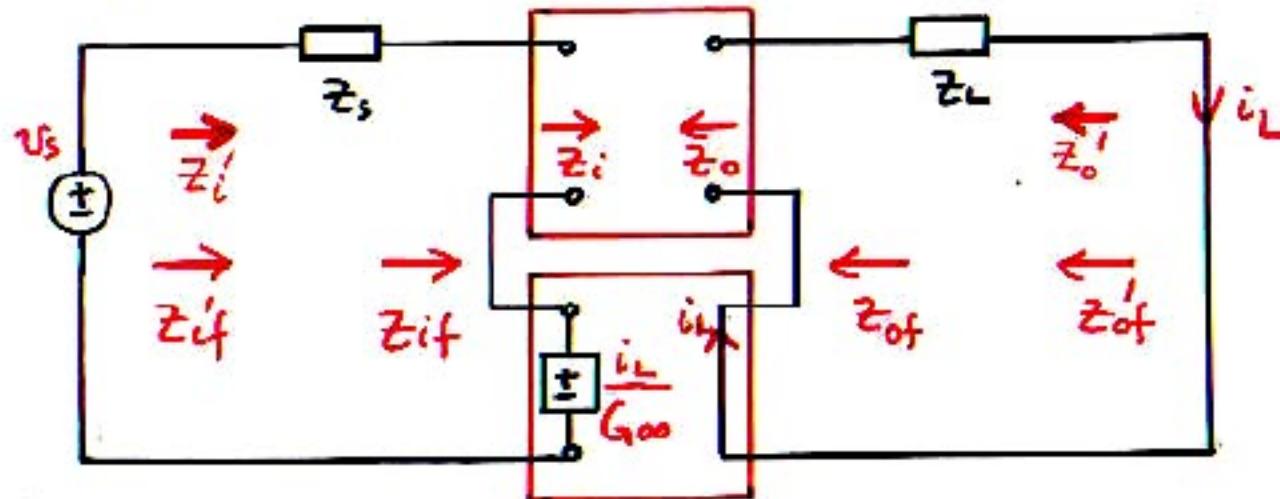2. Voltage -to -current (Series current feedback)



$$Z'_{of} = \frac{Z_L G}{G} \Big|_{Z_L \rightarrow \infty} = \frac{\frac{Z_L A \Big|_{Z_L \rightarrow \infty}}{1 + T \Big|_{Z_L \rightarrow \infty}}}{\frac{A}{1 + T}} = \frac{Z_L A \Big|_{Z_L \rightarrow \infty}}{A} \cdot \frac{1 + T}{1 + T \Big|_{Z_L \rightarrow \infty}} = Z'_o (1 + T)$$


$$Z'_{of} = Z_o (1 + T \Big|_{Z_L \rightarrow \infty})$$

OR:

$$Z'_{of} = \frac{G_{\infty} \frac{Z_L T \Big|_{Z_L \rightarrow \infty}}{1 + T \Big|_{Z_L \rightarrow \infty}}}{G_{\infty} \frac{T}{1 + T}} = \frac{1 + T}{T} [Z_L T \Big|_{Z_L \rightarrow \infty}]$$

$$Z'_{of} = \frac{1 + T}{T} \Big|_{Z_L \rightarrow 0} [Z_L T \Big|_{Z_L \rightarrow \infty}]$$

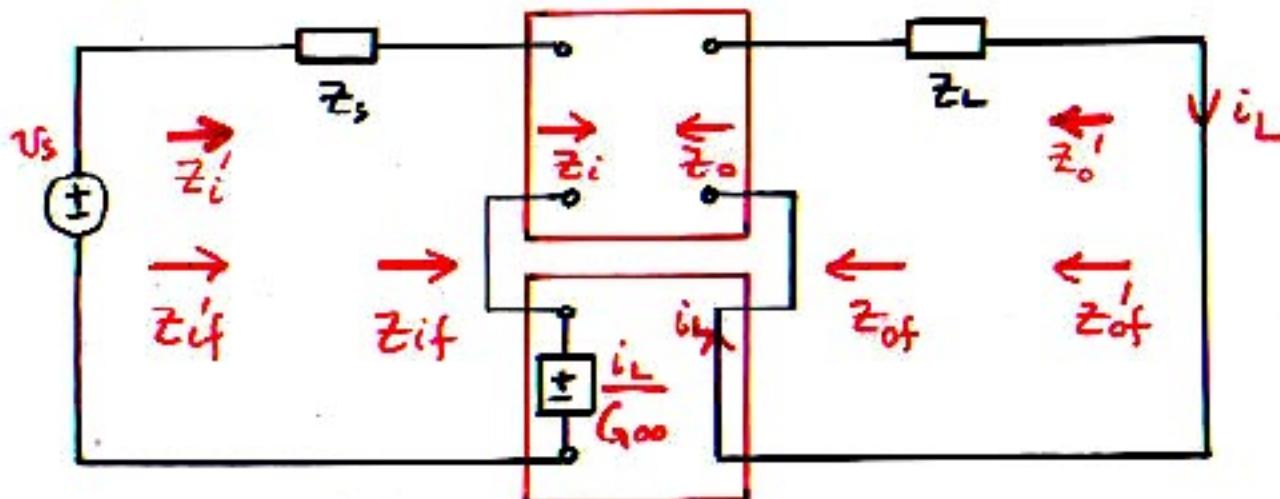2. Voltage -to -current (Series current feedback)



$$Z'_{if} = \frac{Z_s G|_{Z_s \rightarrow \infty}}{G} = \frac{\frac{Z_s A|_{Z_s \rightarrow \infty}}{1 + T|_{Z_s \rightarrow \infty}}}{\frac{A}{1 + T}} = \frac{Z_s A|_{Z_s \rightarrow \infty}}{A} \frac{1 + T}{1 + T|_{Z_s \rightarrow \infty}} = Z'_i (1 + T)$$


$$Z'_{if} = Z_i (1 + T|_{Z_s \rightarrow 0})$$

OR:

$$Z'_{if} = \frac{G_{oo} \frac{Z_s T|_{Z_s \rightarrow \infty}}{1 + T|_{Z_s \rightarrow \infty}}}{G_{oo} \frac{T}{1 + T}} = \frac{1 + T}{T} [Z_s T|_{Z_s \rightarrow \infty}]$$

$$Z'_{if} = \frac{1 + T}{T} \Big|_{Z_s \rightarrow 0} [Z_s T|_{Z_s \rightarrow \infty}]$$

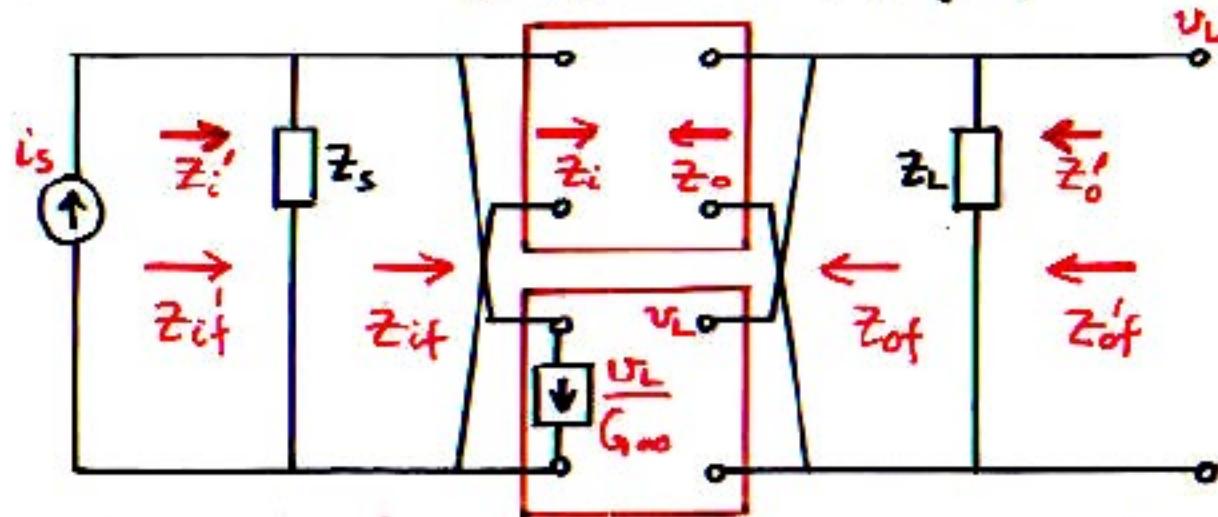3. Current-to-voltage (Shunt voltage feedback)




Ideal feedback path must "sense" output voltage and convert it to a feedback current. Current summing is done in shunt.

$$G = \frac{v_L}{i_s} = \frac{\text{voltage}}{\text{current}} = \frac{A}{1+T} = G_{\infty} \frac{T}{1+T}$$

where

$$A = \frac{v_L}{i_s} \Big|_{K=1/G_{\infty}=0}$$

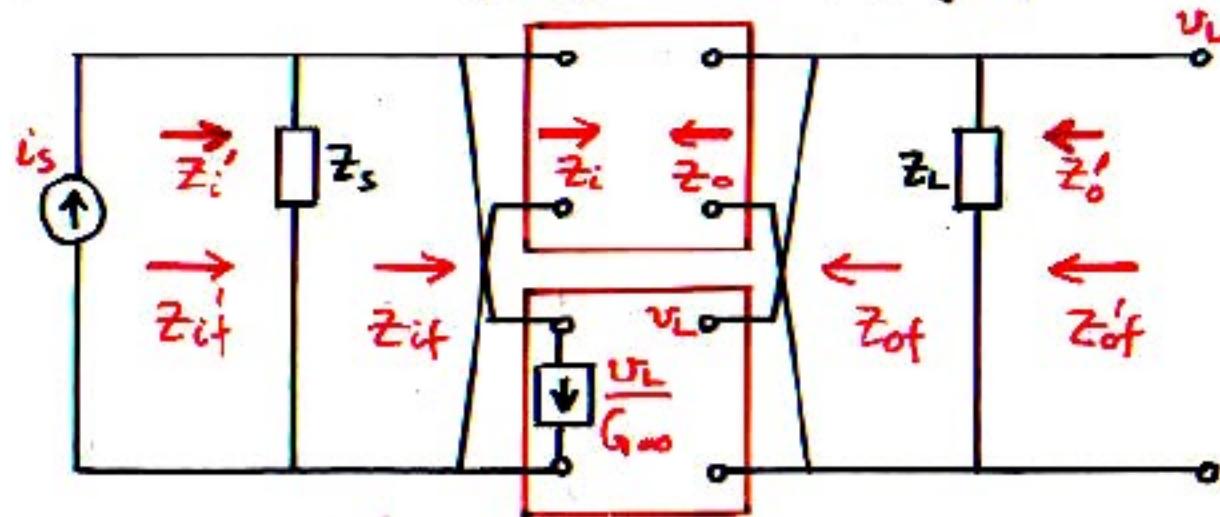3. Current-to-voltage (Shunt voltage feedback)



$$Z_{of}' = \frac{\frac{G}{G|_{z_L \rightarrow 0}}}{\frac{z_L}{z_L|_{z_L \rightarrow 0}}} = \frac{\frac{A}{A|_{z_L \rightarrow 0}} \frac{1}{\frac{1}{1+T|_{z_L \rightarrow 0}}}}{\frac{z_L}{z_L|_{z_L \rightarrow 0}}} = \frac{A}{A|_{z_L \rightarrow 0}} \frac{1+T|_{z_L \rightarrow 0}}{\frac{1}{1+T|_{z_L \rightarrow 0}}} = \frac{z_o'}{1+T}$$


$$Z_{of} = \frac{z_o}{1+T|_{z_L \rightarrow \infty}}$$

OR:

$$Z_{of}' = \frac{\frac{G_\infty \frac{T}{1+T}}{G_\infty \frac{T}{z_L|_{z_L \rightarrow 0}}}}{\frac{1}{1+T|_{z_L \rightarrow 0}}} = \frac{T}{1+T} \left[\frac{z_L}{T} \right]_{z_L \rightarrow 0}$$

$$Z_{of} = \frac{T}{1+T} \left[\frac{z_L}{T} \right]_{z_L \rightarrow \infty}$$

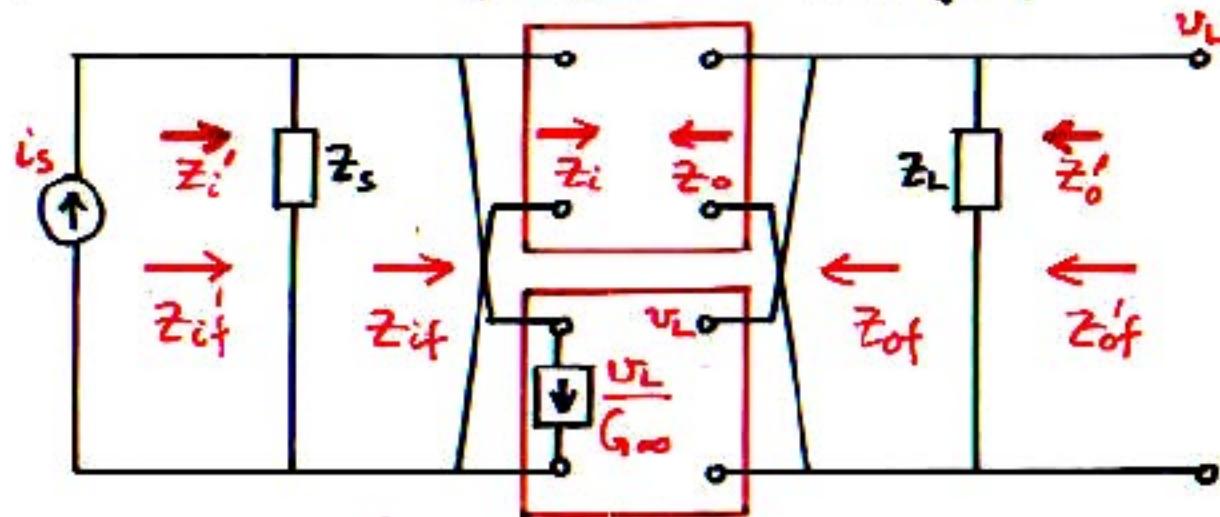3. Current-to-voltage (Shunt voltage feedback)



$$z'_{if} = \frac{G}{\left. \frac{G}{z_s} \right|_{z_s \rightarrow 0}} = \frac{\frac{A}{1+\tau}}{\left. \frac{A}{z_s} \right|_{z_s \rightarrow 0} \left. \frac{1}{1+\tau} \right|_{z_s \rightarrow 0}} = \left. \frac{A}{z_s} \right|_{z_s \rightarrow 0} \frac{1 + \cancel{\tau} z_s \rightarrow 0}{1 + \tau} = \frac{z'_i}{1 + \tau}$$


$$z'_i = \frac{z_i}{1 + \tau \left. z_s \right|_{z_s \rightarrow \infty}}$$

OR:

$$z'_i = \frac{G_{oo} \frac{\tau}{1 + \tau}}{\left. G_{oo} \frac{\tau}{z_s} \right|_{z_s \rightarrow 0} \left. \frac{1}{1 + \tau} \right|_{z_s \rightarrow 0}} = \frac{\tau}{1 + \tau} \left[\left. \frac{z_s}{\tau} \right|_{z_s \rightarrow 0} \right]$$

$$z'_{if} = \frac{\tau}{1 + \tau} \left. \left[\left. \frac{z_s}{\tau} \right|_{z_s \rightarrow 0} \right] \right|_{z_s \rightarrow \infty}$$

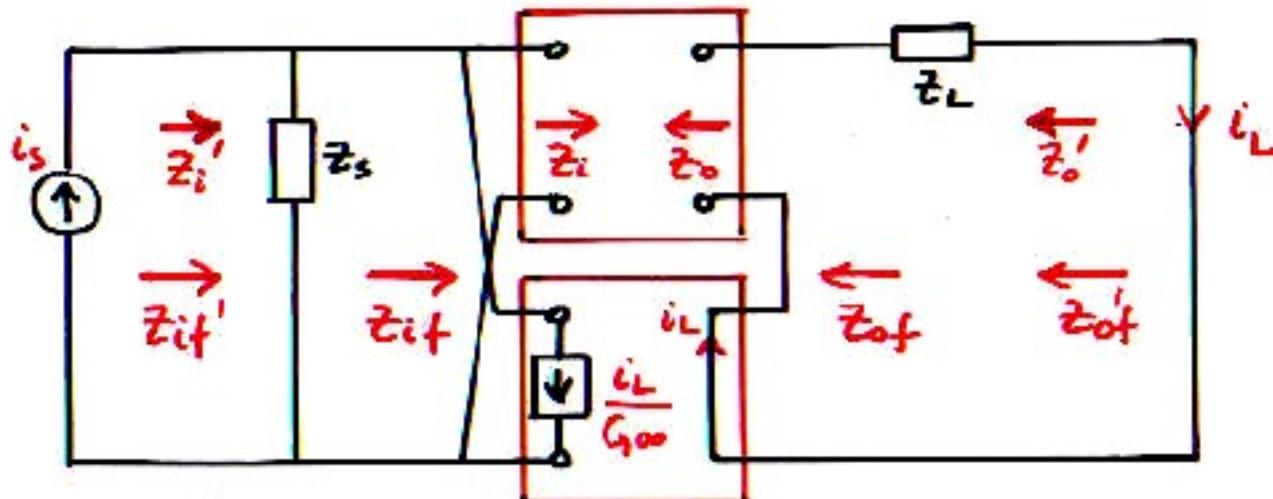4. Current-to-current (shunt current feedback)




Ideal feedback path must "sense" output current and convert it to a feedback current. Current summing is done in shunt.

$$G_i = \frac{i_L}{i_s} = \frac{\text{current}}{\text{current}} = \frac{A}{1+T} = G_{oo} \frac{T}{1+T}$$

where

$$A = \left. \frac{i_L}{i_s} \right|_{K=1/G_{oo}=0}$$

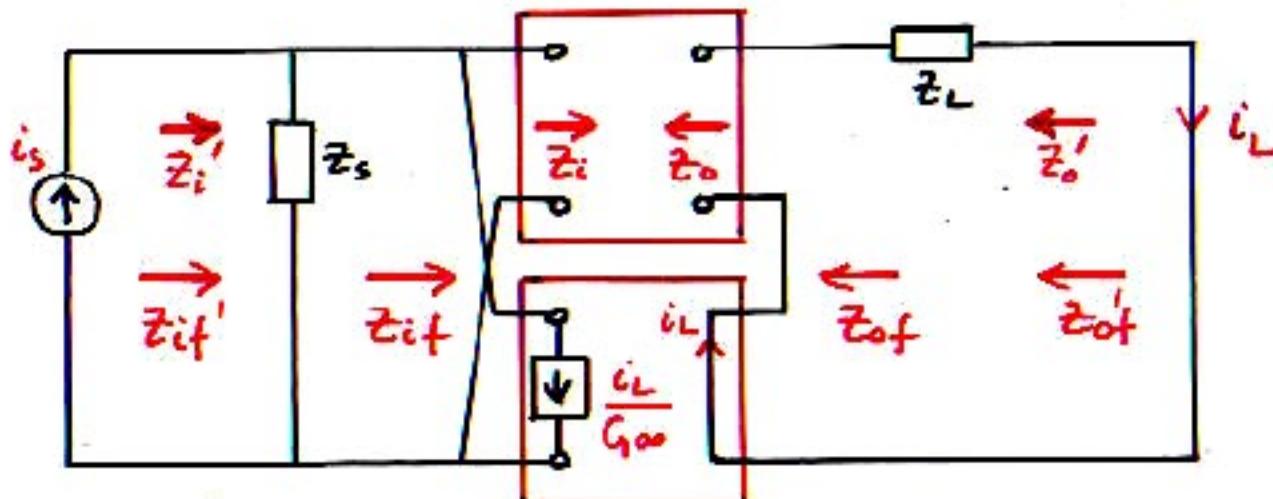4. Current-to-current (shunt current feedback)



$$z_{of}' = \frac{z_L G_m |_{z_L \rightarrow \infty}}{G} = \frac{\frac{z_L A |_{z_L \rightarrow \infty}}{1 + T |_{z_L \rightarrow \infty}}}{\frac{A}{1 + T}} = \frac{z_L A |_{z_L \rightarrow \infty}}{A} \cdot \frac{1 + T}{1 + T |_{z_L \rightarrow \infty}} = z_o' (1 + T)$$


$$z_{of}' = z_o' (1 + T |_{z_L \rightarrow \infty})$$

OR:

$$z_{of}' = \frac{G_m \frac{z_L T |_{z_L \rightarrow \infty}}{1 + T |_{z_L \rightarrow \infty}}}{G \frac{T}{1 + T}} = \frac{1 + T}{T} [z_L T |_{z_L \rightarrow \infty}]$$

$$z_{of}' = \frac{1 + T}{T} |_{z_L \rightarrow \infty} [z_L T |_{z_L \rightarrow \infty}]$$

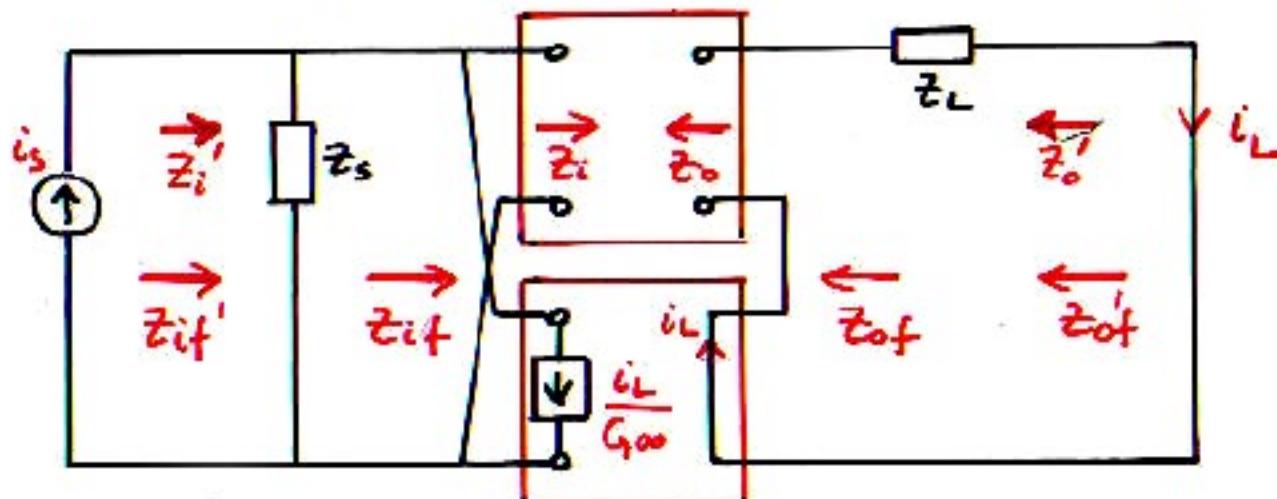4. Current-to-current (shunt current feedback)



$$Z'_{if} = \frac{G}{\left. \frac{G}{z_s} \right|_{z_s \rightarrow 0}} = \frac{\frac{A}{1+T}}{\left. \frac{A}{z_s} \right|_{z_s \rightarrow 0} \left. \frac{1}{1+T} \right|_{z_s \rightarrow 0}} = \frac{A}{\left. \frac{A}{z_s} \right|_{z_s \rightarrow 0}} \frac{1+T \cancel{|}_{z_s \rightarrow 0}}{1+T} = \frac{z'_i}{1+T}$$


$$Z'_4 = \frac{z_i}{1+T \left. \frac{1}{z_s} \right|_{z_s \rightarrow \infty}}$$

OR:

$$Z'_4 = \frac{G_{oo} \frac{T}{1+T}}{\left. G_{oo} \frac{T}{z_s} \right|_{z_s \rightarrow 0} \left. \frac{1}{1+T} \right|_{z_s \rightarrow 0}} = \frac{T}{1+T} \left[\left. \frac{z_s}{T} \right|_{z_s \rightarrow 0} \right]$$


$$Z'_4 = \frac{T}{1+T} \left. \left[\left. \frac{z_s}{T} \right|_{z_s \rightarrow 0} \right] \right|_{z_s \rightarrow \infty}$$

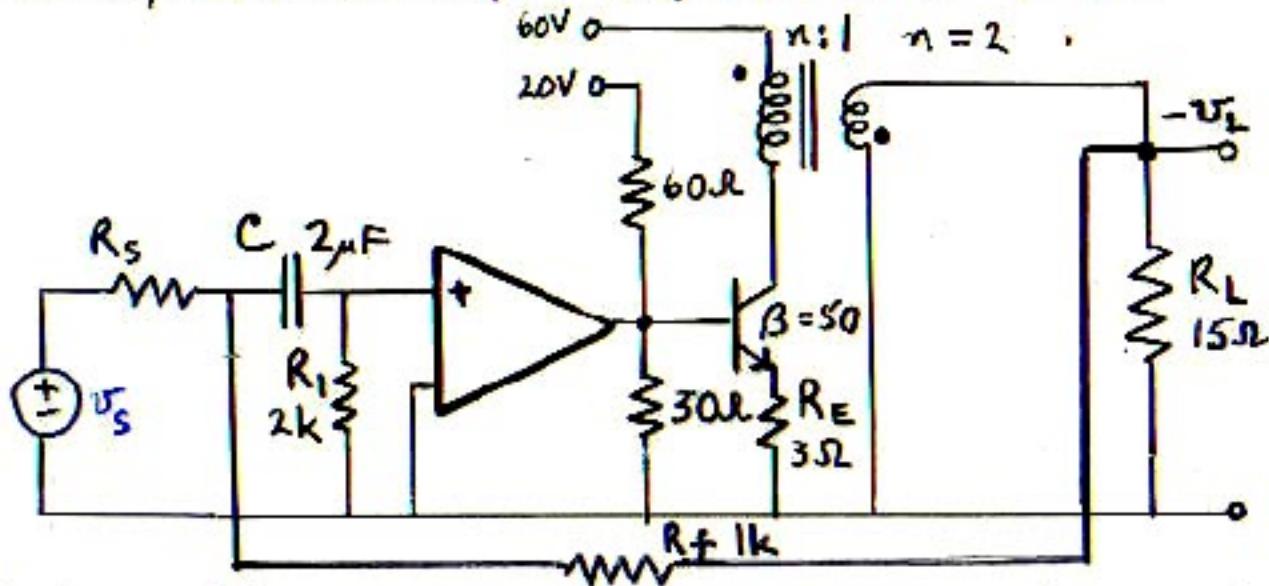Single-ended Class A audio feedback power amplifier, based on the same power stage previously discussed. The driver opamp has a gain $A_1 = A_{10} / (1 + s/\omega_A)$, where $A_{10} = 8\text{dB}$ and $f_A = 2\text{kHz}$, and an output impedance of 4.5Ω .




Although the gain is expressed as a voltage ratio, this is really a "Type 3" current-to-voltage feedback amplifier, because the feedback signal is connected at a shunt current-summing junction.

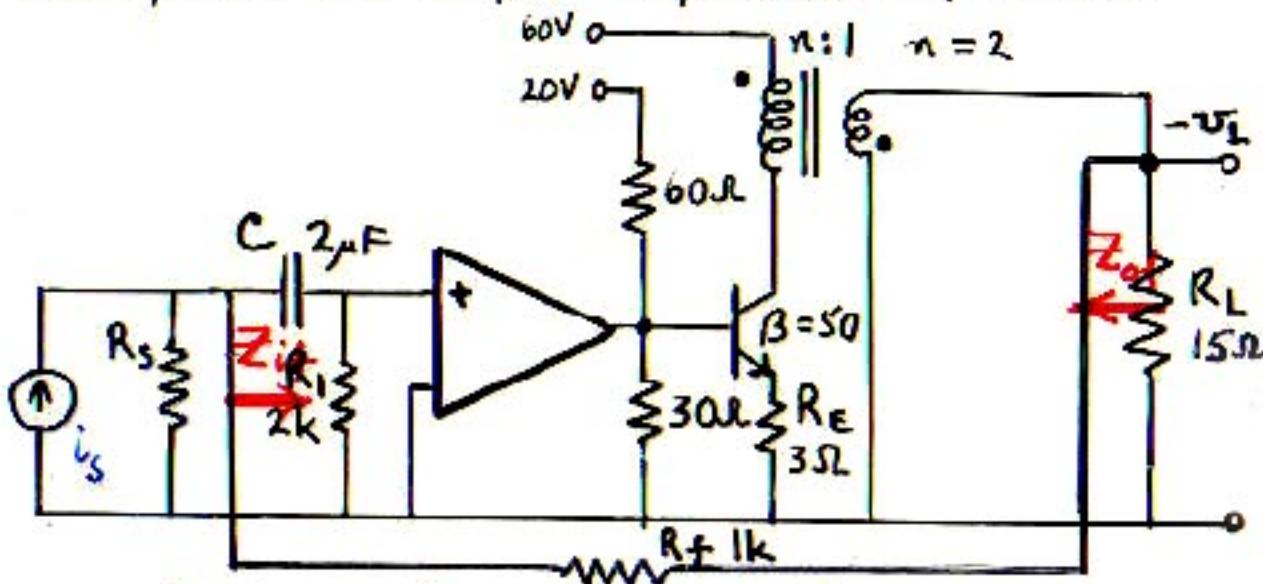Single-ended Class A audio feedback power amplifier, based on the same power stage previously discussed. The driver opamp has a gain $A_1 = A_{1o} / (1 + s/\omega_A)$, where $A_{1o} = 8\text{dB}$ and $\omega_A = 2\text{kHz}$, and an output impedance of 4.5Ω .




Hence, the "inside" output and input impedances Z_{of} and Z_{if} are both lowered by the feedback.

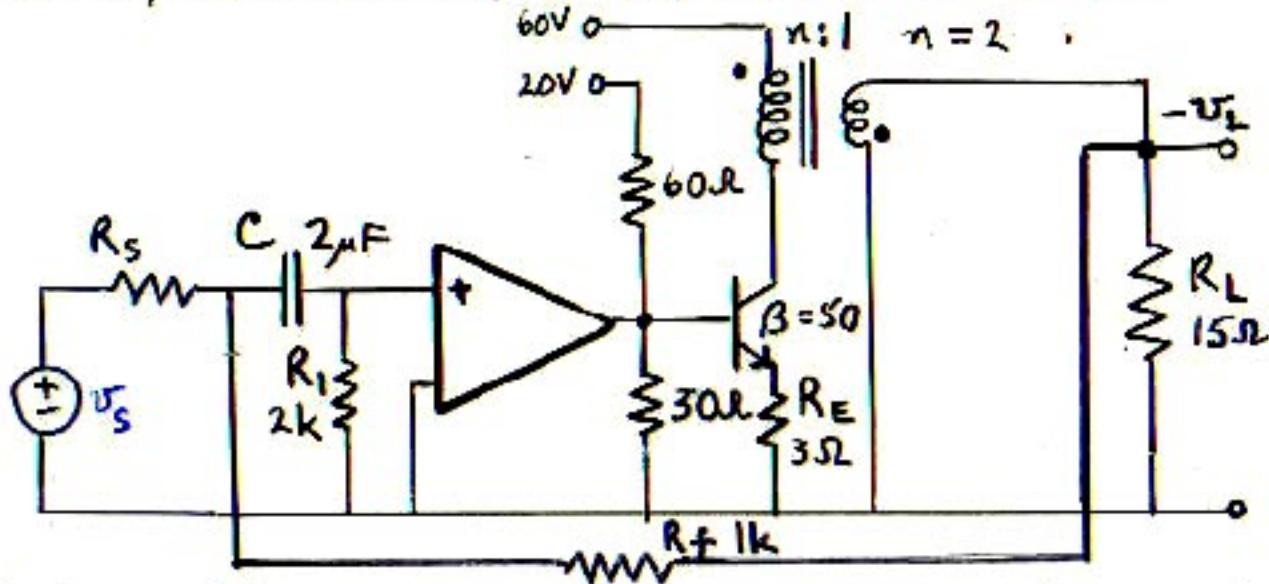Single-ended Class A audio feedback power amplifier, based on the same power stage previously discussed. The driver opamp has a gain $A_1 = A_{10} / (1 + s/\omega_A)$, where $A_{10} = 8\text{dB}$ and $\omega_A = 2\text{kHz}$, and an output impedance of 4.5Ω .




Although the gain is expressed as a voltage ratio, this is really a "Type 3" current-to-voltage feedback amplifier, because the feedback signal is connected at a shunt current-summing junction.

Ac model

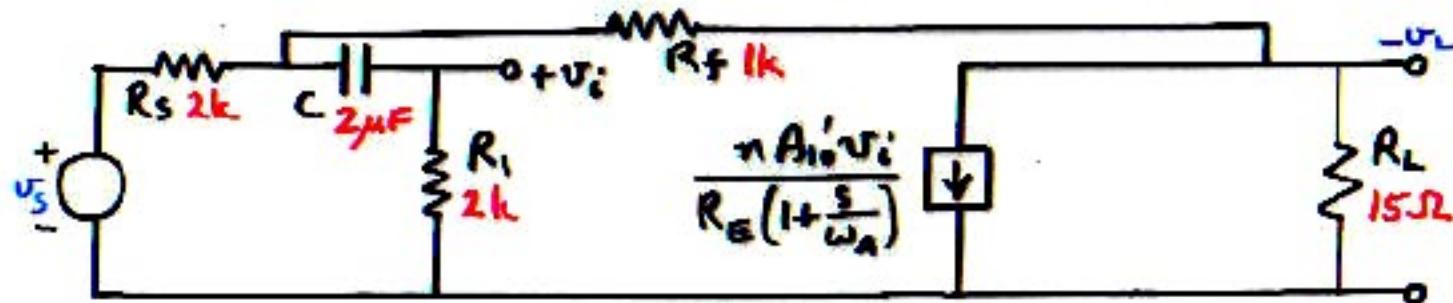

Ac model

Find Z_{of}

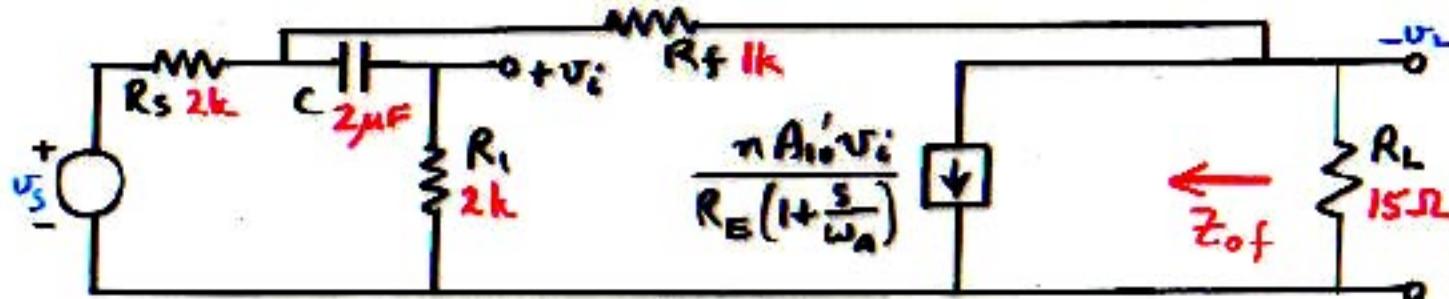

Use $Z_{of} = \frac{T}{1+T} \Big|_{R_L \rightarrow \infty} \left[\frac{R_L}{T} \Big|_{R_L \rightarrow 0} \right]$

where

$$T = T_m \frac{1}{(1 + \frac{\omega_2}{s})(1 + \frac{s}{\omega_n})}$$

$$T_m = \frac{(R + nR_s || R_1)nA_{1o}R_L}{R_f R_E}$$

$$\omega_2 = \frac{1}{C[R_f || R_s + R_1]}$$

$$\frac{R_L}{T} \Big|_{R_L \rightarrow 0} = \frac{R_f R_E}{(R_f + R_s + R_1) n A_{v0}} \left(1 + \frac{\omega_2}{s} \right) \left(1 + \frac{s}{\omega_A} \right)$$


$$T \Big|_{R_L \rightarrow \infty} = \infty, \text{ so } \frac{T}{1+T} \Big|_{R_L \rightarrow \infty} = 1$$

Hence



$$Z_{af} = R_{af} \left(1 + \frac{\omega_2}{s} \right) \left(1 + \frac{s}{\omega_A} \right)$$

where

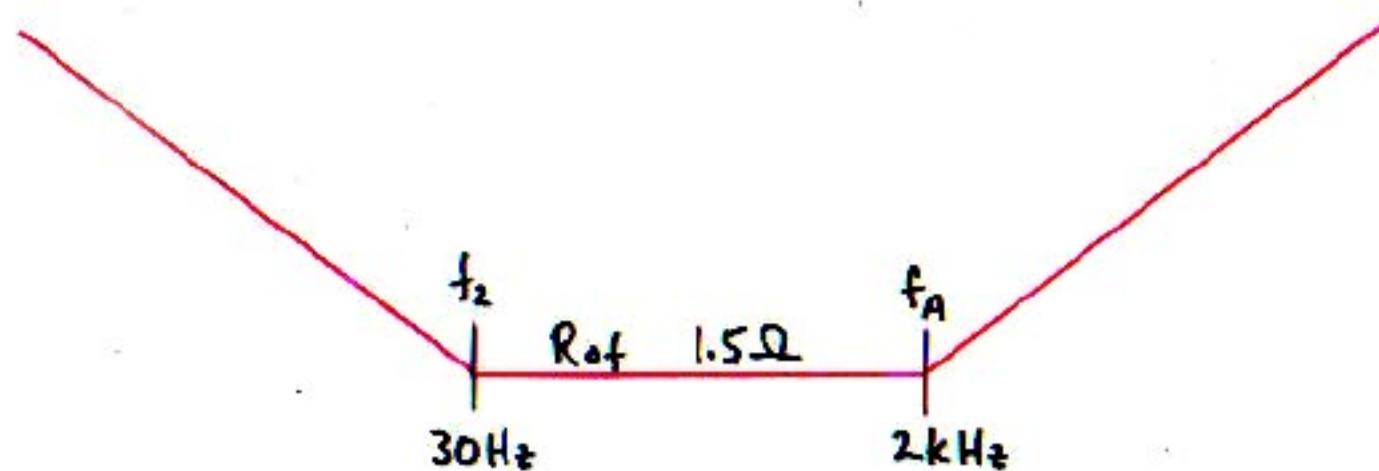
$$R_{af} = \frac{R_f R_E}{(R_f + R_s + R_1) n A_{v0}} = \frac{1 \times 3}{0.5 \times 2 \times 2} = 1.5 \Omega$$



Ac model

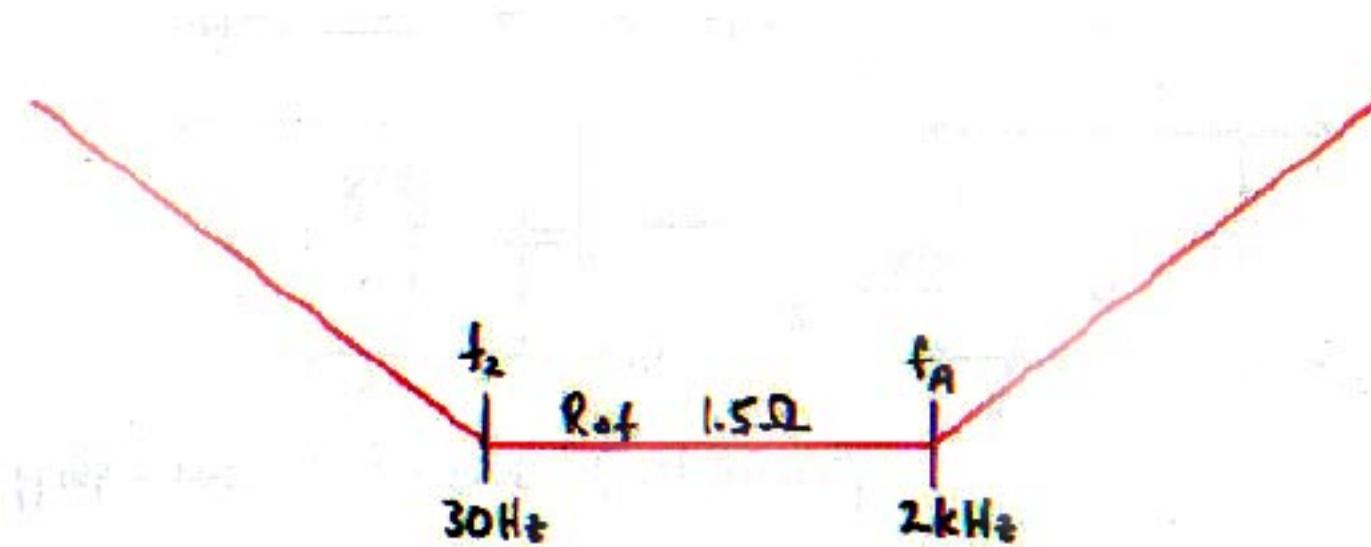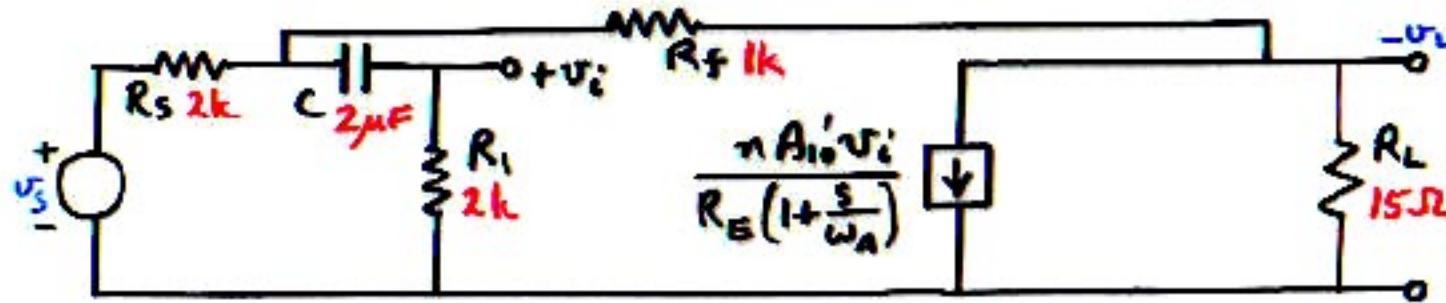

AC model

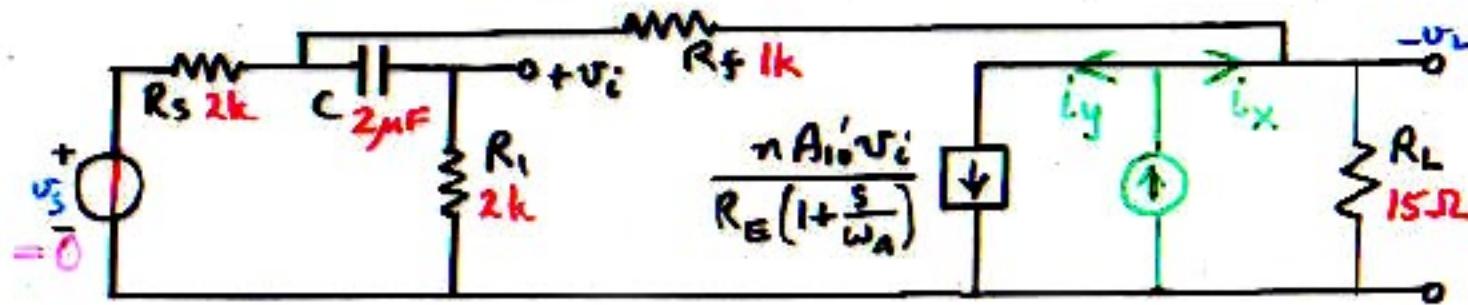


$$T = \left. \frac{i_y}{i_x} \right|_{u_s=0} = \cancel{R_L + R_f + R_s || R_i (1 + \frac{\omega_1}{s})} \quad \frac{R_s}{R_s + R_i (1 + \frac{\omega_1}{s})} \frac{R_i n A_{10}'}{R_E (1 + \frac{s}{\omega_A})}$$

where

$$\omega_1 = \frac{1}{C R_i} \quad f_1 = \frac{159}{2 \times 2} = 40 \text{ Hz}$$

Ac model

Find Z_{of}

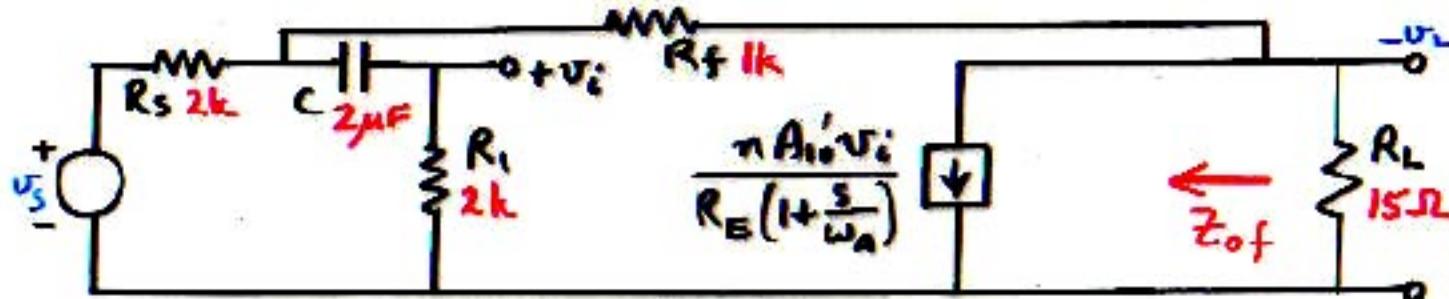


Use $Z_{of} = \frac{T}{1+T} \Big|_{R_L \rightarrow \infty} \left[\frac{R_L}{T} \Big|_{R_L \rightarrow 0} \right]$

where

$$T = T_m \frac{1}{\left(1 + \frac{\omega_2}{s}\right)\left(1 + \frac{s}{\omega_n}\right)}$$

$$T_m = \frac{(R + nR_s || R_1)nA_{10}'R_L}{R_f R_E}$$


$$\omega_2 = \frac{1}{C[R_f || R_s + R_1]}$$

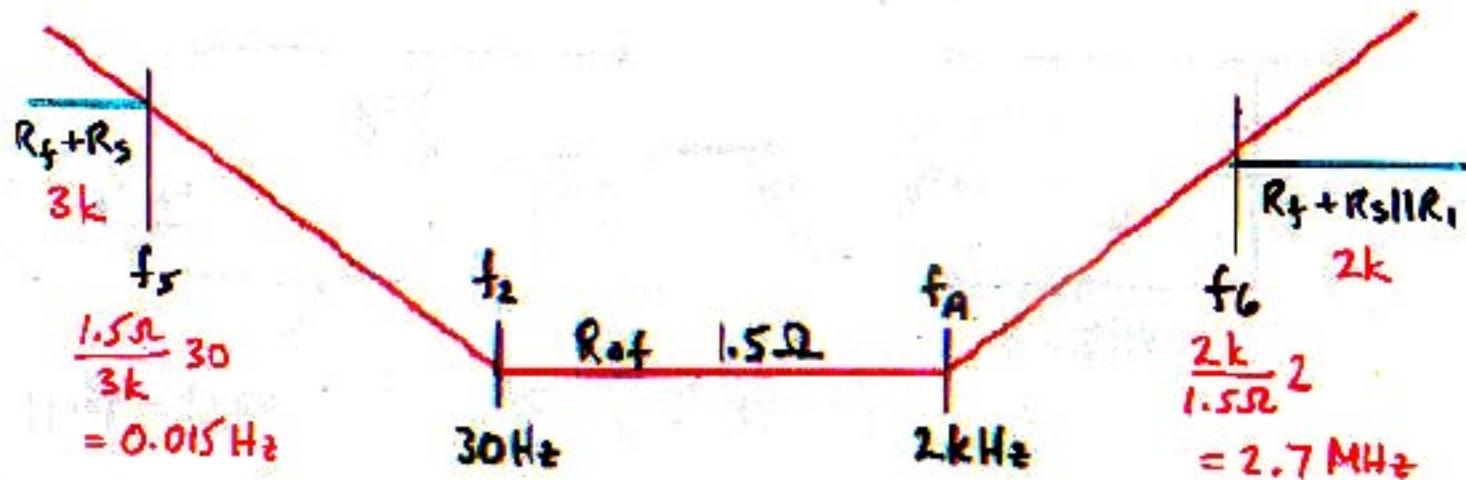

Note from the actual circuit that Z_{af} would limit at both low and high frequencies, because of the loading effect of the feedback path on R_L . This nonideality was ignored in the solution, but could have been included with further complication but no additional difficulty.

Ac model

Find Z_{if}

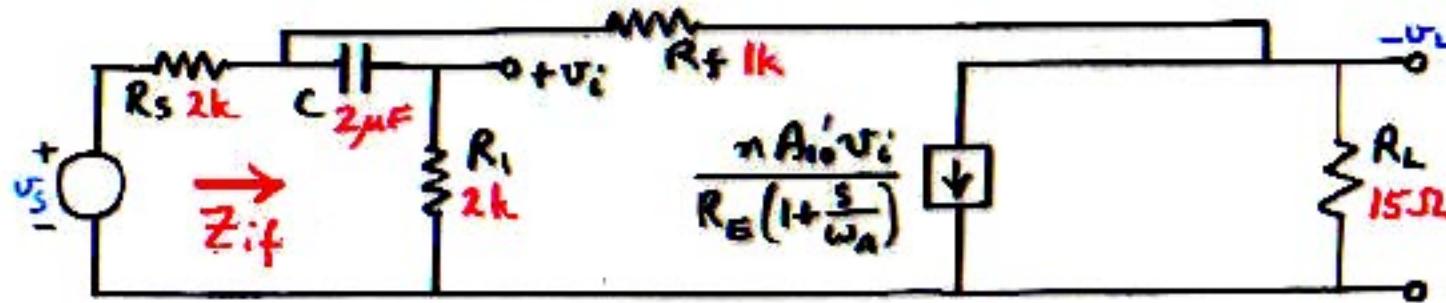

Use $Z_{if} = \frac{T}{1+T} \Big|_{R_s \rightarrow \infty} \cdot \frac{R_s}{T} \Big|_{R_s \rightarrow 0}$

where $D = \frac{T}{1+T} = \frac{T_m}{1+T_m} \frac{1}{\left(1 + \frac{\omega_3}{\omega}\right)\left(1 + \frac{\omega}{\omega_4}\right)}$

$$\omega_3 = \frac{\omega_2}{1+T_m}$$

$$\omega_2 = \frac{1}{C[R_f || R_s + R_i]}$$

$$\omega_4 = (1+T_m)\omega_A$$

$$\left. \frac{R_s}{T} \right|_{R_s \rightarrow 0} = \frac{R_f + R_E}{n A_{10}' R_L} \left(1 + \frac{\omega_2}{s} \right) \left(1 + \frac{s}{\omega_A} \right)$$

where

$$\omega_2 \equiv \omega_2|_{R_s \rightarrow 0} = \frac{1}{C R_i} = \omega_1$$

$$D|_{R_s \rightarrow \infty} = \frac{(R_f + R_i) n A_{10}' R_L}{R_f R_E (1 + T_m|_{R_s \rightarrow \infty})} \frac{1}{\left(1 + \frac{\omega_E}{s} \right) \left(1 + \frac{s}{\omega_q} \right)}$$

where

$$\begin{aligned} \omega_S &\equiv \omega_3|_{R_s \rightarrow \infty} = \frac{\omega_2|_{R_s \rightarrow \infty}}{1 + T_m|_{R_s \rightarrow \infty}} \\ &= \frac{1}{C(R_f + R_i)(1 + T_m|_{R_s \rightarrow \infty})} \end{aligned}$$

$$T_m|_{R_s \rightarrow \infty} = \frac{(R_f + R_i) n A_{10}' R_L}{R_f R_E} = \frac{(112) 2 \times 2 \times 15}{1 \times 3} = 13$$

$$f_S = \frac{159}{2(1+2)(1+13)} = 1.9 \text{ Hz}$$

$$\omega_q \equiv (1 + T_m|_{R_s \rightarrow \infty}) \omega_A$$

$$f_q = 14 \times 2 = 28 \text{ kHz}$$


Hence

$$Z_{if} = \frac{(R_f || R_i) n A_{10} R_L}{R_f R_o (1 + T_m |_{R_s \rightarrow \infty})} \frac{R_f + R_o}{n A_{10} R_L} \frac{(1 + \frac{\omega_1}{s})(1 + \frac{s}{\omega_A})}{(1 + \frac{\omega_f}{s})(1 + \frac{s}{\omega_A})}$$

$$= R_{if} \frac{(1 + \frac{\omega_1}{s})(1 + \frac{s}{\omega_A})}{(1 + \frac{\omega_f}{s})(1 + \frac{s}{\omega_A})}$$

$$R_{if} = \frac{R_f || R_i}{1 + T_m |_{R_s \rightarrow \infty}}$$

$$= \frac{1/12}{1/4} = 47 \Omega$$

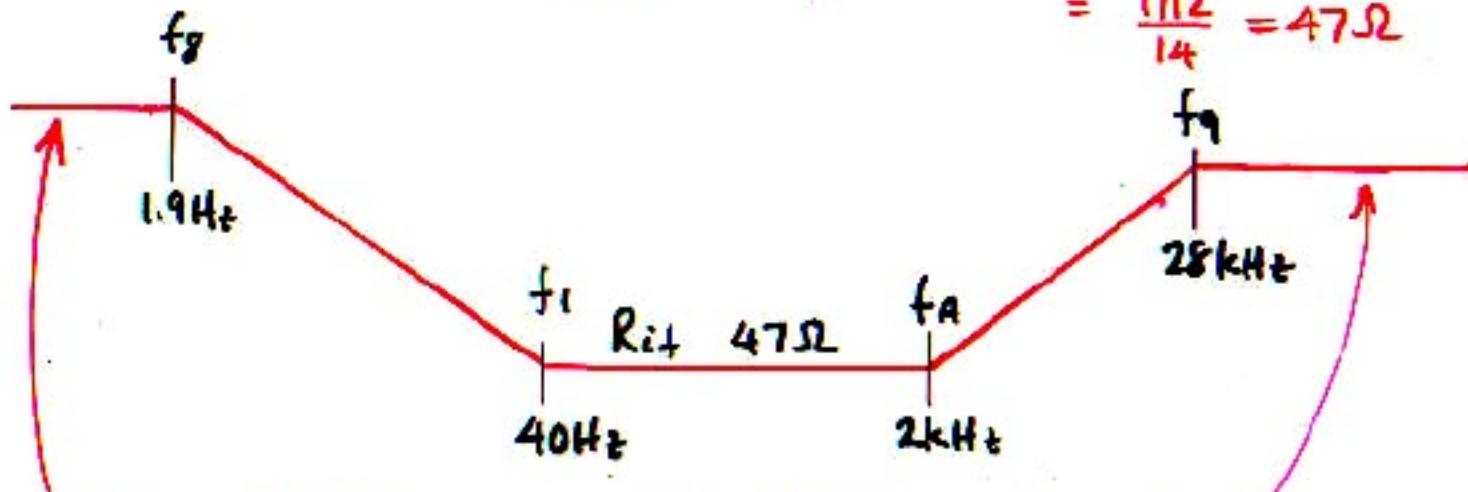

$$R_{if} \frac{\omega_1}{\omega_B} = \frac{R_f || R_i}{1 + T_m |_{R_s \rightarrow \infty}} \frac{C(R_f + R_i)(1 + T_m |_{R_s \rightarrow \infty})}{CR_i}$$

$$= R_f$$

$$= 1k$$


$$R_{if} \frac{\omega_A}{\omega_B} = \frac{R_f || R_i}{1 + T_m |_{R_s \rightarrow \infty}} (1 + T_m |_{R_s \rightarrow \infty})$$

$$= R_f || R_i = 0.67k$$

Example: Distortion

When the open-loop amplifier is delivering full output power at 1kHz, the output stage develops 3% 2nd harmonic and 5% 3rd harmonic distortion. Find the full output power closed-loop total harmonic distortion at 1kHz.

Percentage of each harmonic is reduced by $|1+T|$ at the harmonic frequency.

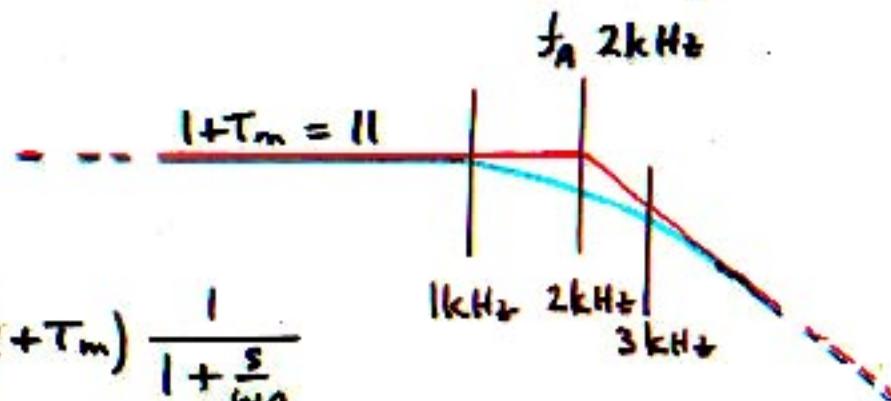

$$1+T = (1+\tau_m) \frac{1}{1 + \frac{s}{\omega_A}}$$

$$|1+T|_{2\text{kHz}} = 11 \sqrt{1 + \left(\frac{2}{2}\right)^2} = \frac{11}{\sqrt{2}} = 7.8$$

$$|1+T|_{3\text{kHz}} = 11 \sqrt{1 + \left(\frac{3}{2}\right)^2} = \frac{11}{\sqrt{3.8}} = 6.1$$

$$\begin{aligned} \text{THD} &= \sqrt{\left(\frac{3\%}{7.8}\right)^2 + \left(\frac{5\%}{6.1}\right)^2} = \sqrt{0.39^2 + 0.82^2} \\ &= 0.91\% \end{aligned}$$

Generalization: Effect of Feedback on Impedances

1. Output impedance is {decreased} by {voltage} feedback from the output.
{increased} by {current}

Input impedance is {increased} by {series} feedback to the input.
{decreased} by {shunt}

2. The "outside" impedances are changed by a factor $(1+T)$

The "inside" impedances are changed by a larger factor.

3. Alternatively, the input and output impedances can be found solely from the loop gain T .

Stability

If the open-loop gain A is stable, the closed-loop gain


$$G = \frac{A}{1+A}$$

is stable if $1+A$ has no roots in the right half-plane (R_{hp}).

By complex variable theory, this implies that a polar plot of $1+A$ must not encircle the origin; or, equivalently, that a polar plot of A must not encircle the $(-1, 0)$ point. (Nyquist Stability Criterion).

Simple cases of the Nyquist plot of loop gain A :


1-pole response:

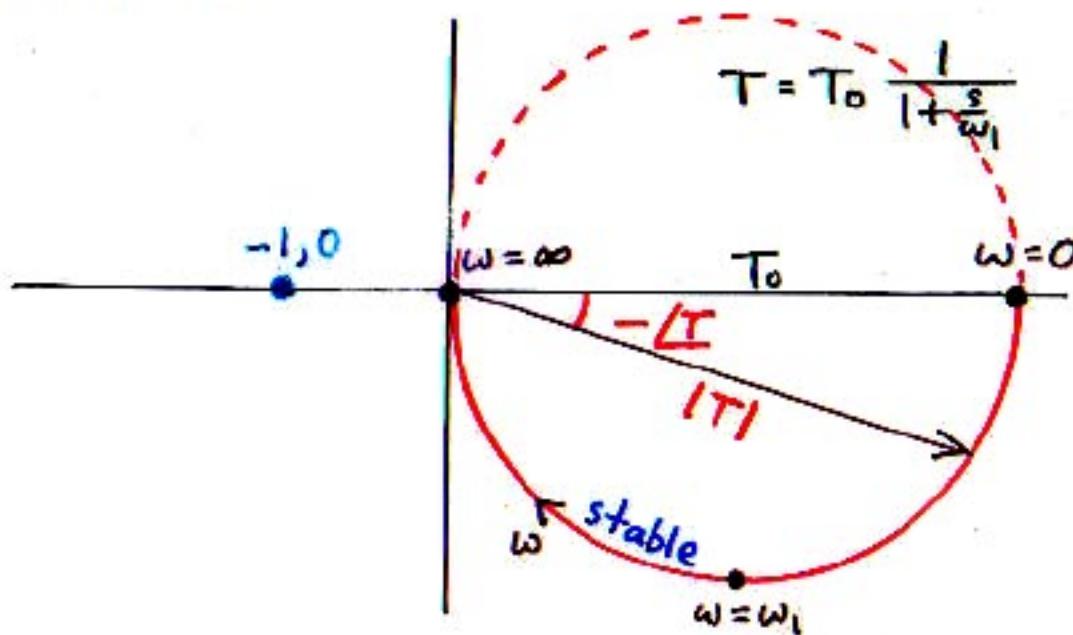

Always stable


2-pole response
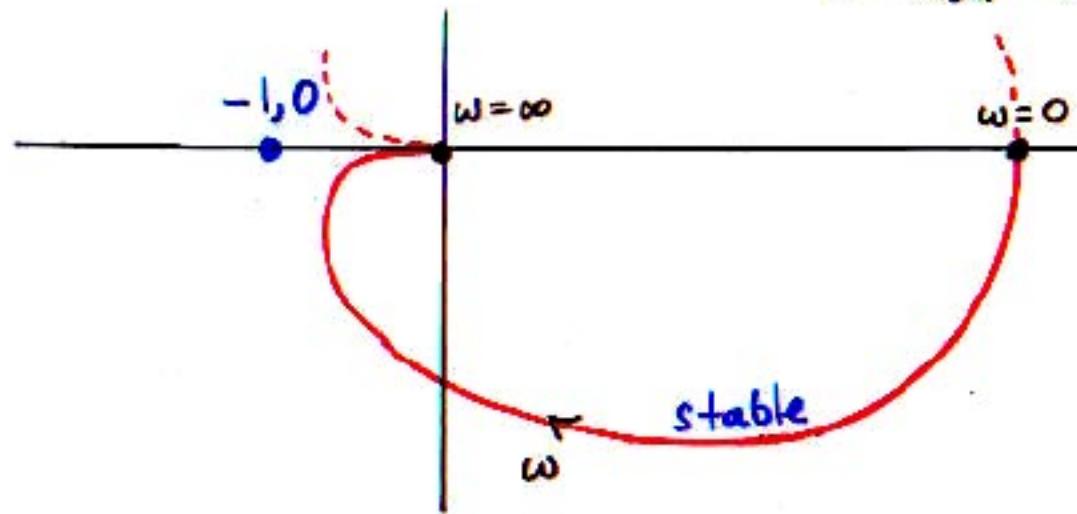
$$T = T_0 \frac{1}{(1 + \frac{\omega}{\omega_1})(1 + \frac{\omega}{\omega_2})}$$




Always stable

3-pole response

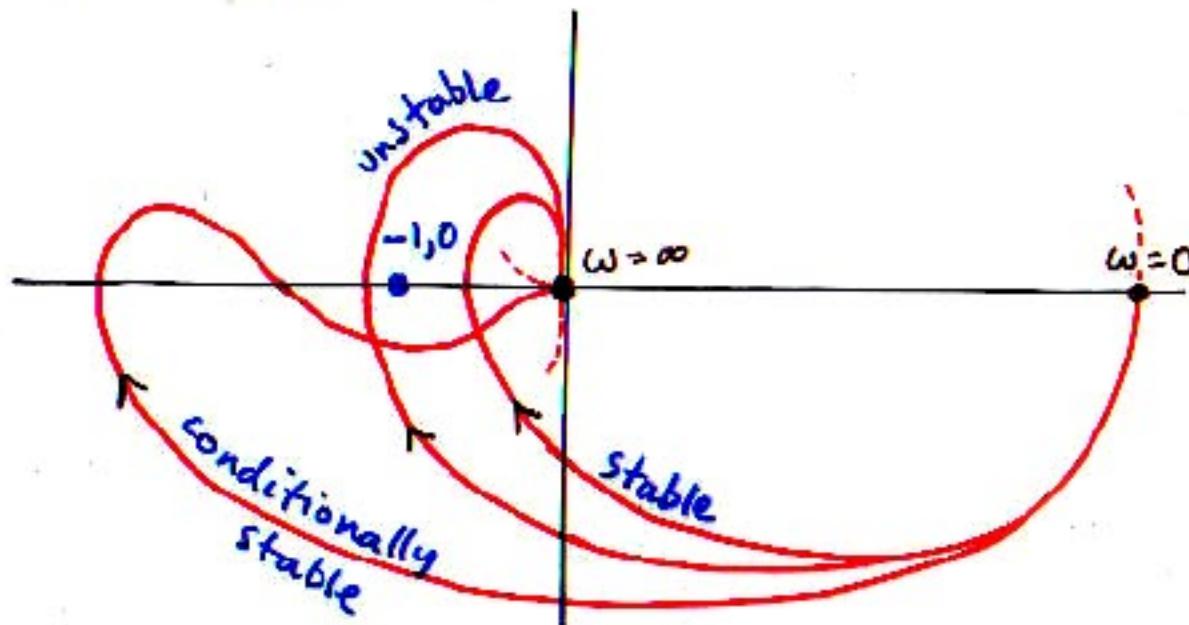

Can be stable or unstable


Stability margins

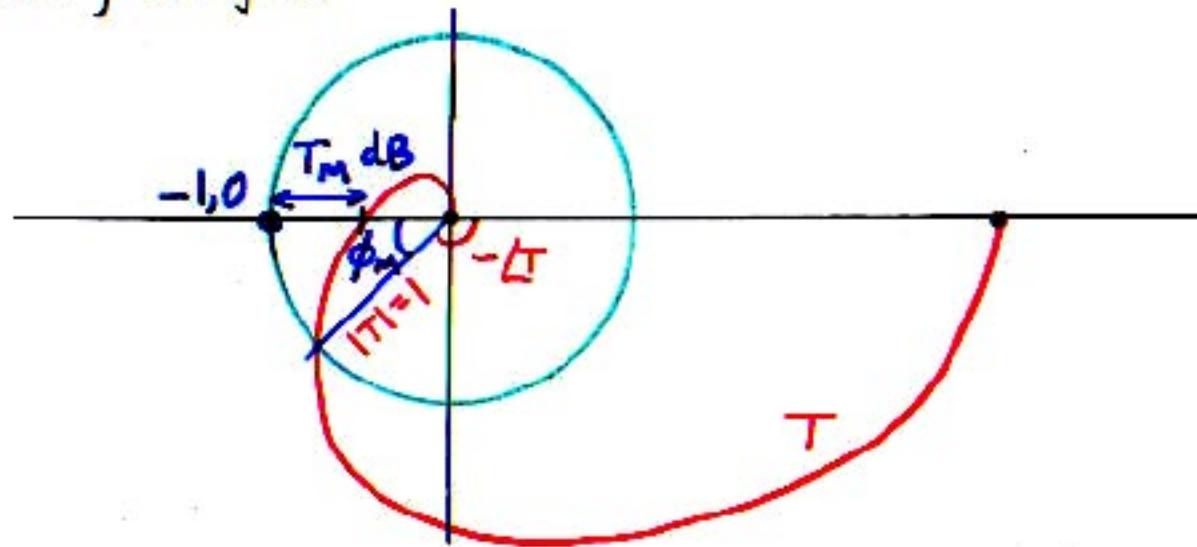


Phase margin $\phi_M = 180^\circ + \angle T$ when $|T| = 1$ (0 dB)
C negative (lag)

Gain margin $T_M \text{ dB} = -T \text{ dB}$ when $\angle T = -180^\circ$

Bode plot:

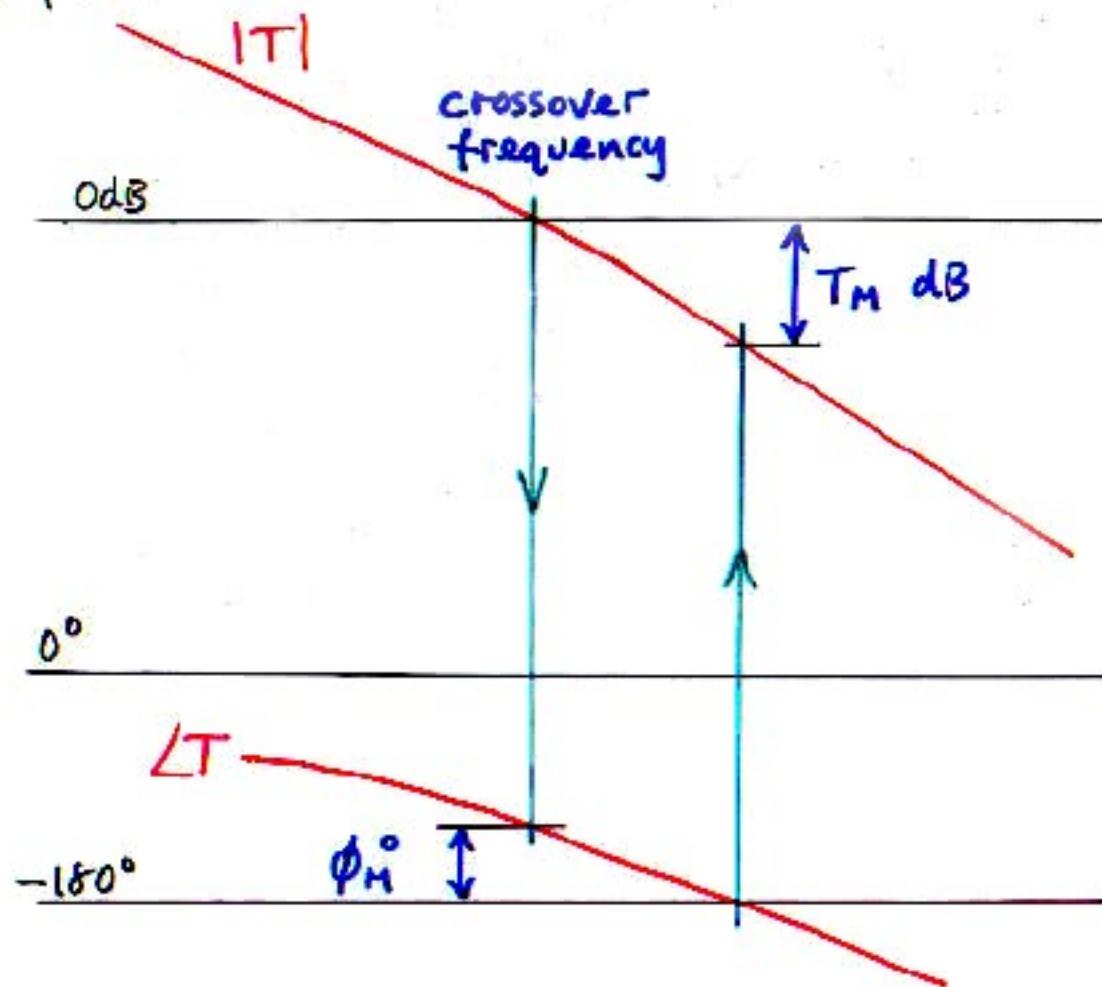


Stability margins

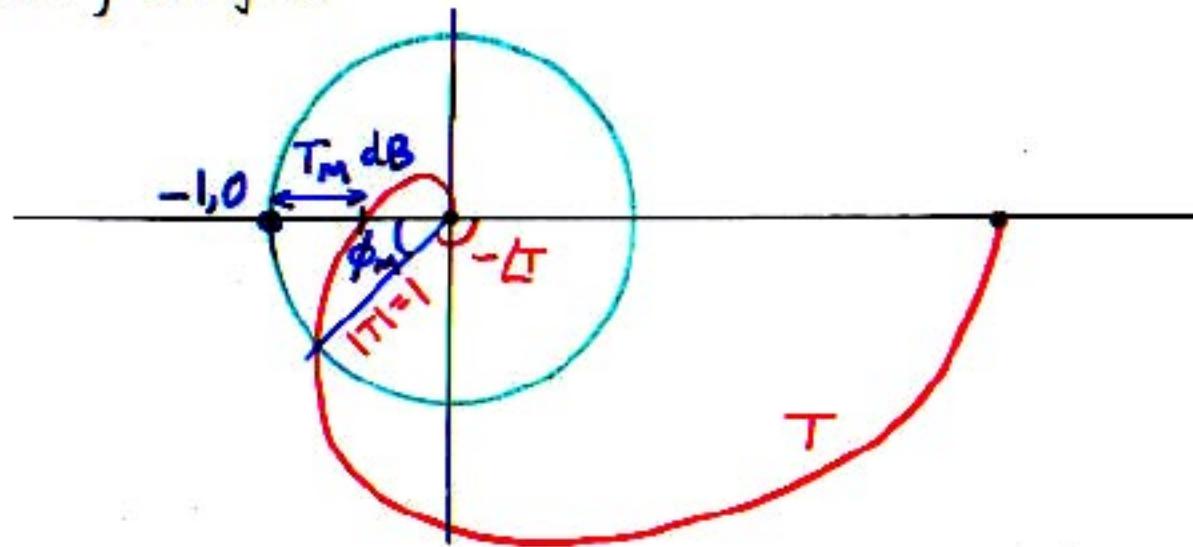

Phase margin $\phi_M = 180^\circ + \angle T$ when $|T| = 1$ (0 dB)
C negative (lag)

Gain margin $T_M \text{ dB} = -T \text{ dB}$ when $\angle T = -180^\circ$


Stability margins

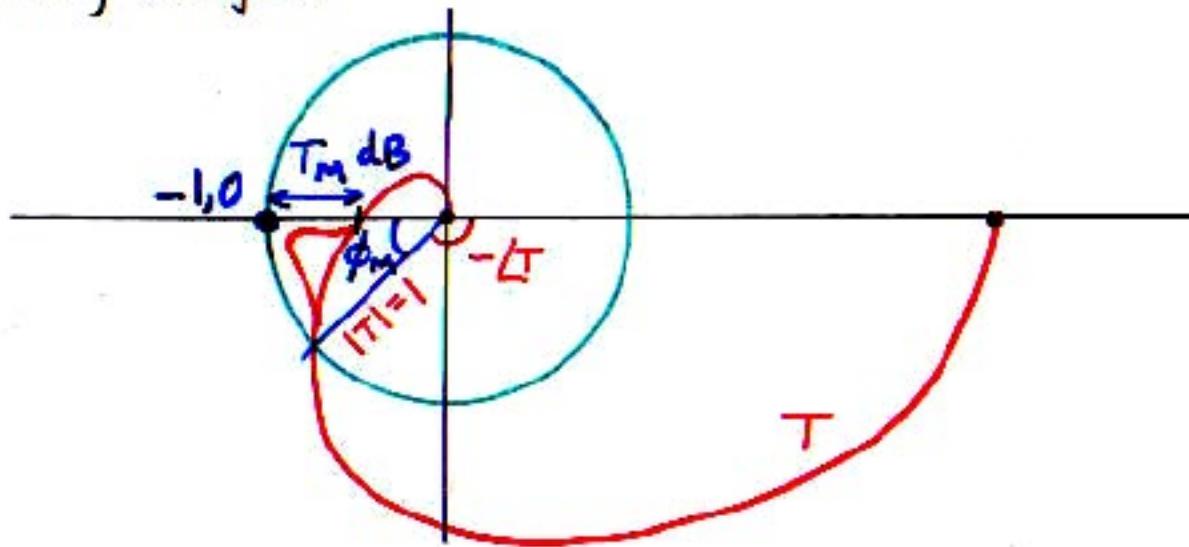

Phase margin $\phi_M = 180^\circ + \angle T$ when $|T| = 1$ (0dB)
↳ negative (lag)

Gain margin $T_M \text{ dB} = -T \text{ dB}$ when $\angle T = -180^\circ$


Stability margins

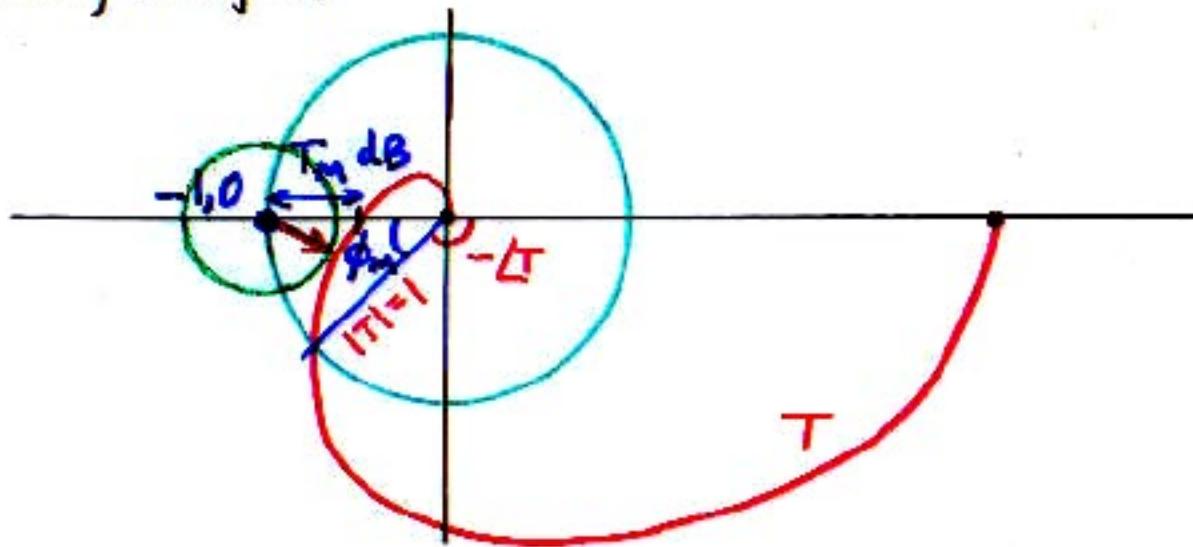


Phase margin $\phi_M = 180^\circ + \angle T$ when $|T| = 1$ (0dB)
C negative (lag)

Gain margin $T_M \text{ dB} = -T \text{ dB}$ when $\angle T = -180^\circ$

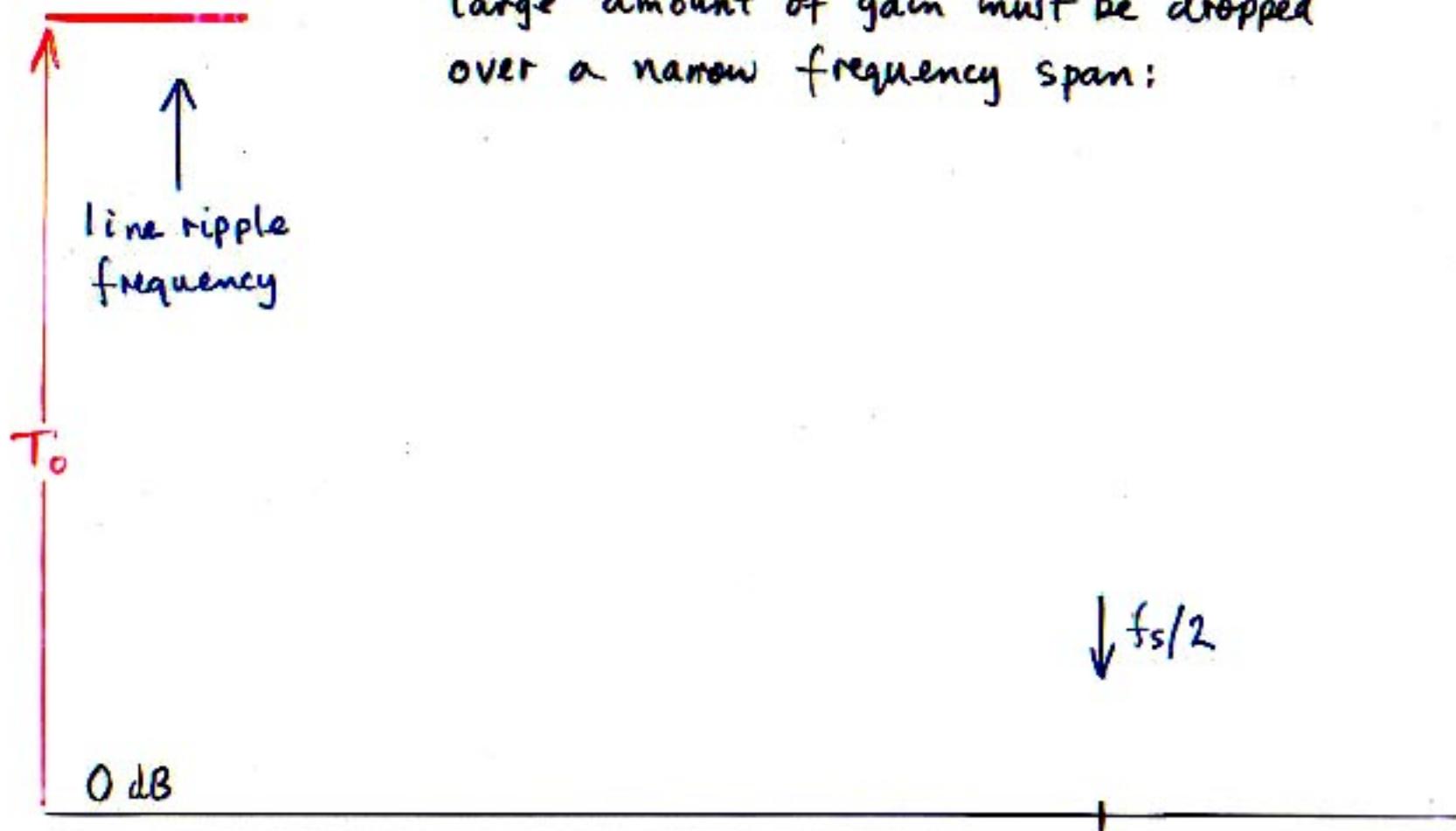
A conditionally stable system may be necessary when a large amount of gain must be dropped over a narrow frequency span:



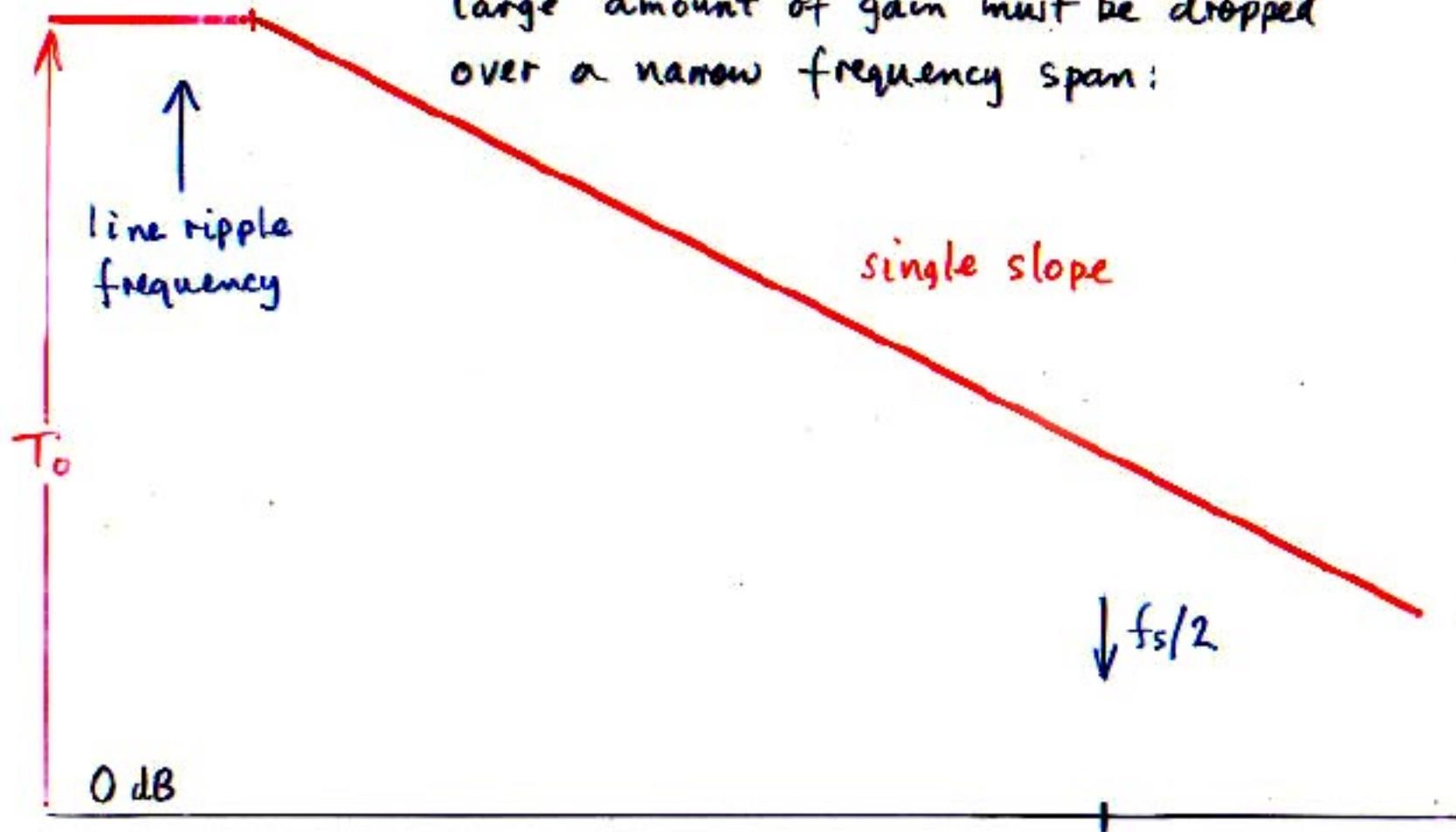A conditionally stable system may be necessary when a large amount of gain must be dropped over a narrow frequency span:



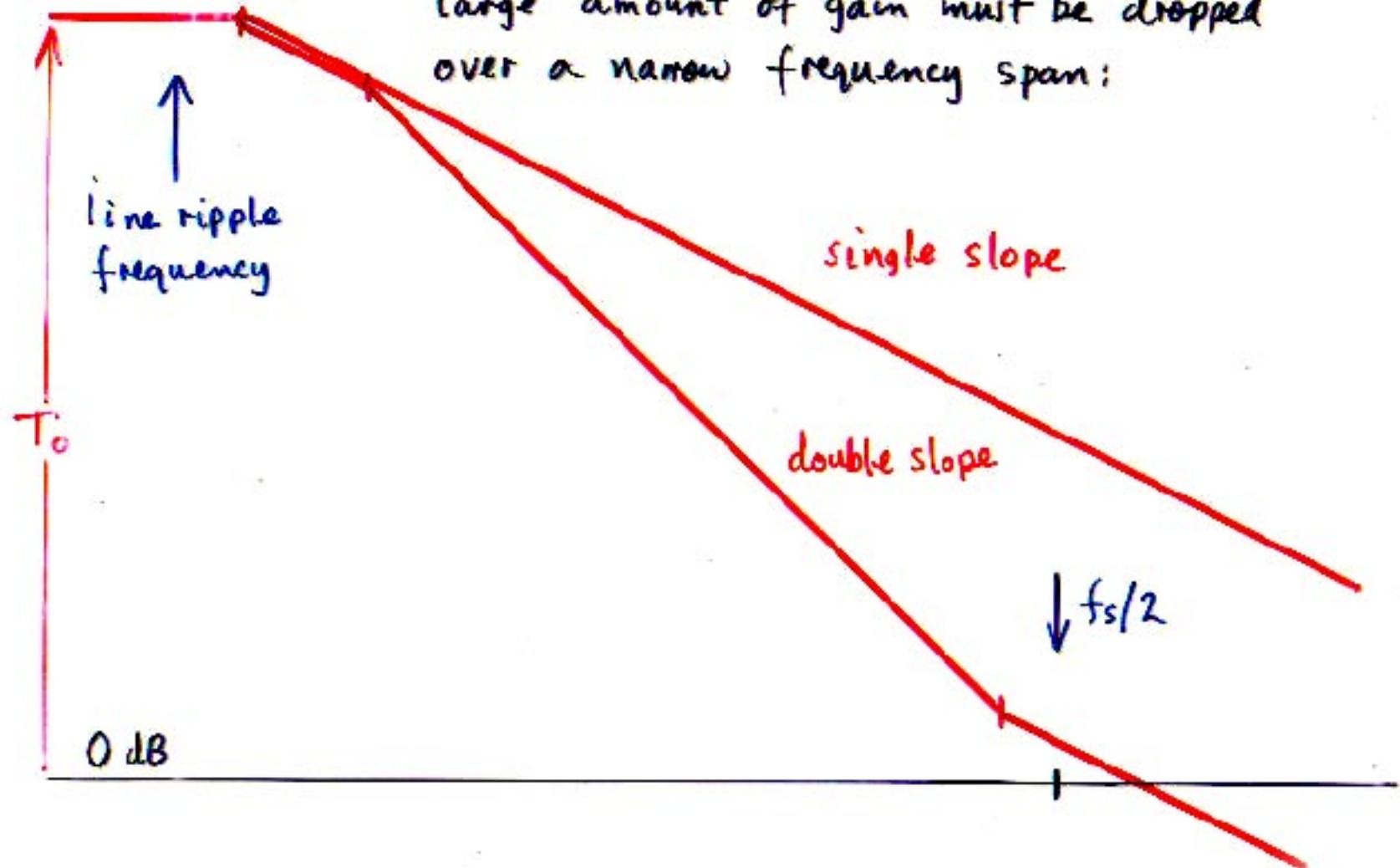A conditionally stable system may be necessary when a large amount of gain must be dropped over a narrow frequency span:



A conditionally stable system may be necessary when a large amount of gain must be dropped over a narrow frequency span:

