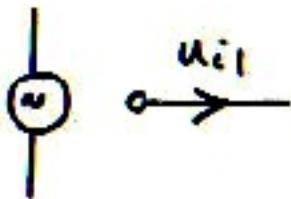


6

NULL DOUBLE INJECTION (NDI)
AND THE
EXTRA ELEMENT THEOREM (EET)

Null Double Injection


Consider a system with a single injected (input) signal u_{i1} , and two dependent (output) signals u_{o1}, u_{o2} :



$$u_{o1} = A_1 u_{i1}$$

$$u_{o2} = B_1 u_{i1}$$

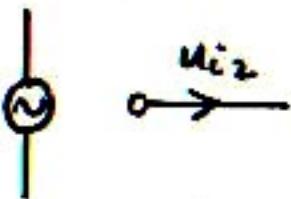Consider a second injected signal u_{i2} which alone would give:



$$u_{o1} = A_2 u_{i2}$$

$$u_{o2} = B_2 u_{i2}$$

If the system is linear, in general each output is a linear sum of the outputs due to each input:

$$u_{i1}$$



$$u_{o1} = A_1 u_{i1} + A_2 u_{i2}$$



$$u_{i2}$$



$$u_{o2} = B_1 u_{i1} + B_2 u_{i2}$$



Note definition of "gains":

$$\frac{u_{o1}}{u_{i1}} \Big|_{u_{i2}=0} = A_1$$

$$\frac{u_{o1}}{u_{i2}} \Big|_{u_{i1}=0} = A_2$$

$$\frac{u_{o2}}{u_{i1}} \Big|_{u_{i2}=0} = B_1$$

$$\frac{u_{o2}}{u_{i2}} \Big|_{u_{i1}=0} = B_2$$

By adjustment of u_{i2} relative to u_{i1} (in magnitude and phase), either output can be nullled:

For example, if u_{o1} is nullled:

$$0 = A_1 u_{i1} + A_2 u_{i2} \Big|_{u_{o1}=0}$$

$$u_{o2} = B_1 u_{i1} + B_2 u_{i2} \Big|_{u_{o1}=0}$$


By elimination of u_{i1} :

$$\frac{u_{o2}}{u_{i2}} \Big|_{u_{o1}=0} = \frac{A_1 B_2 - A_2 B_1}{A_1}$$

Notice the difference from

$$\frac{u_{o2}}{u_{i2}} \Big|_{u_{i1}=0} = B_2$$

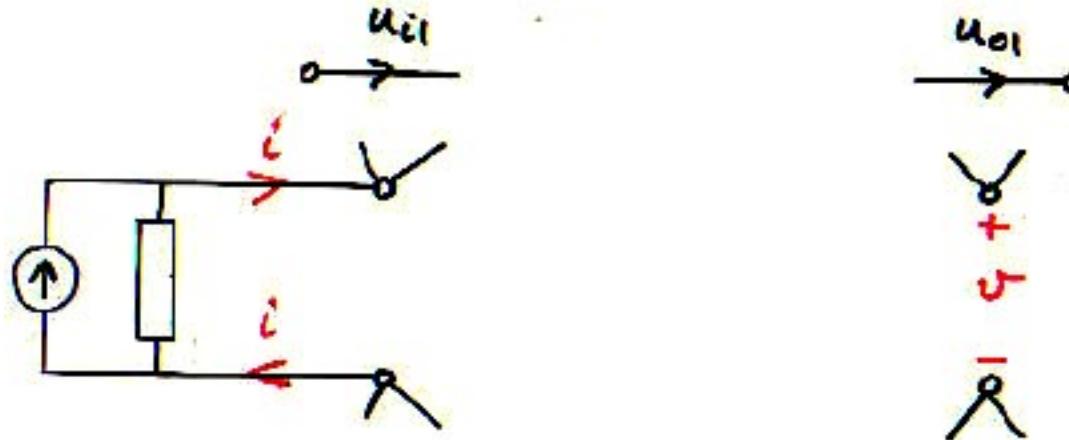Particular example: $u_{i_2} = i$, $u_{o_2} = v$:



$$u_{o_1} = A_1 u_{i_1} + A_2 i$$

$$v = B_1 u_{i_1} + B_2 i$$


So

$$\frac{v}{i} \Big|_{u_{i_1}=0} = B_2$$

$$\frac{v}{i} \Big|_{u_{o_1}=0} = \frac{A_1 B_2 - A_2 B_1}{A_1}$$

Special case: the Extra Element Theorem

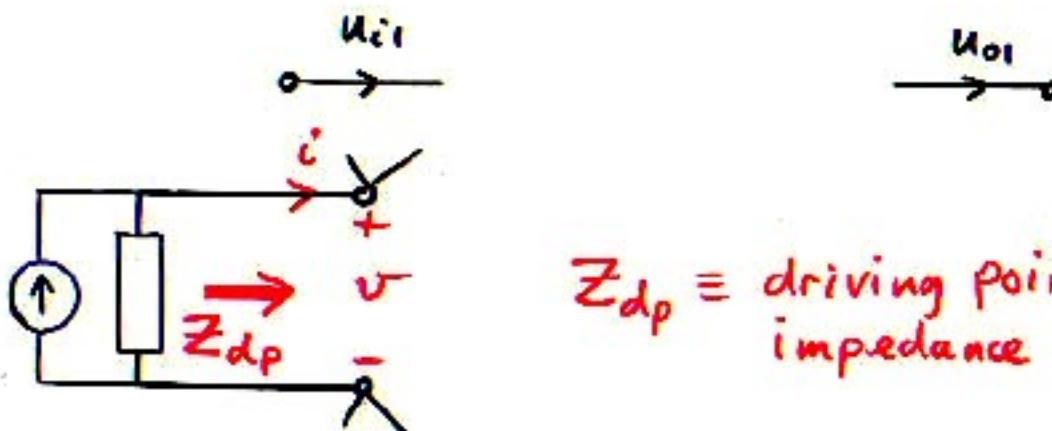The second output v is across the second input terminals:



Z_{dp} = driving point impedance

Then

$$\frac{v}{i} \Big|_{u_{ii}=0} = Z_{dp} \Big|_{u_{ii}=0} \equiv Z_d = B_2$$

$$\frac{v}{i} \Big|_{u_{oi}=0} = Z_{dp} \Big|_{u_{oi}=0} \equiv Z_n = \frac{A_1 B_2 - A_2 B_1}{A_1}$$

Consider the original circuit without $u_{cz} = i$:



$$u_{ci}$$

$$u_{oi}$$



$$\text{Original gain} = A_1 = \frac{u_{oi}}{u_{ci}} \Big|_{u_{cz}=0}$$

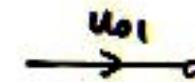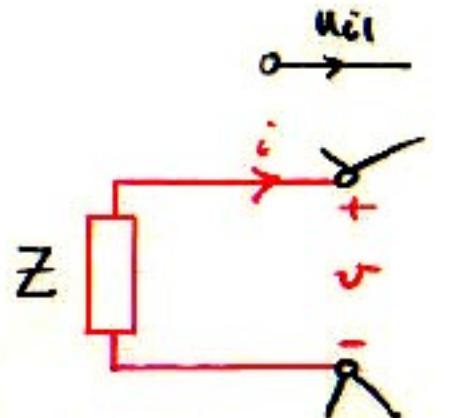Consider the original circuit without $u_{i2} = i$:



$$\text{Original gain} = A_1 = \frac{u_{o1}}{u_{i1}} \Big|_{u_{i2}=0}$$

Now consider the circuit with an extra element Z :

$$i = -\frac{v}{Z}$$

$$\text{So } u_{o1} = A_1 u_{i1} - \frac{A_2}{Z} v$$

$$v = B_1 u_{i1} - \frac{B_2}{Z} v$$

Eliminate v :

$$u_{o1} = A_1 \frac{1 + \frac{1}{Z} \frac{A_1 B_2 - A_2 B_1}{A_1}}{1 + \frac{1}{Z} B_2} u_{i1}$$

Hence

$$u_{o1} = A_1 \frac{1 + \frac{Z_n}{Z}}{1 + \frac{Z_d}{Z}} u_{i1}$$

or

$$\text{gain}|_Z = \text{gain}|_{Z=\infty} \frac{1 + \frac{Z_n}{Z}}{1 + \frac{Z_d}{Z}}$$

This is the Extra Element Theorem: how to calculate the gain, after an extra element is added, by a correction factor instead of starting from scratch.

Hence

$$u_{o1} = A_1 \frac{1 + \frac{Z_N}{Z}}{1 + \frac{Z_d}{Z}} u_{i1}$$

or

$$\text{gain}|_Z = \text{gain}|_{Z=\infty} \frac{1 + \frac{Z_N}{Z}}{1 + \frac{Z_d}{Z}}$$

This is the Extra Element Theorem: how to calculate the gain, after an extra element is added, by a correction factor instead of starting from scratch.

The Theorem also proves that any transfer function (e.g. gain) of a linear system is a bilinear function of any single element (e.g. Z).

forming Δ_{11} the terms by which z is multiplied must be the minor $\Delta_{11,jj}$ obtained by omitting both the first and j th rows and columns. If we let Δ^0 and Δ_{11}^0 represent, respectively, Δ and Δ_{11} when $z = 0$, therefore, we have

$$Z = \frac{\Delta^0 + z\Delta_{jj}}{\Delta_{11}^0 + z\Delta_{11,jj}}. \quad (I-11)$$

Since Δ_{jj} and $\Delta_{11,jj}$ are evidently independent of z they can equally well be written as Δ_{jj}^0 and $\Delta_{11,jj}^0$. This will occasionally be done in later analysis in order to facilitate further transformations.

The relation between Z_T and z can be found in similar fashion. It is given by

$$Z_T = \frac{\Delta^0 + z\Delta_{jj}}{\Delta_{12}^0 + z\Delta_{12,jj}}. \quad (I-12)$$

If z represents a unilateral coupling term, instead of a bilateral element, the expansion is essentially the same. Thus, if we suppose that z is a part of Z_{ij} in the original determinant, we readily find

$$Z = \frac{\Delta^0 + z\Delta_{ij}}{\Delta_{11}^0 + z\Delta_{11,ij}} \quad (I-13)$$

and

$$Z_T = \frac{\Delta^0 + z\Delta_{ij}}{\Delta_{12}^0 + z\Delta_{12,ij}}. \quad (I-14)$$

The "brute-force" method: loop analysis


$$(R_s + R_B) i_1 - R_B \cdot i_B = v_1$$

$$-R_B i_1 + [R_B + (1+\beta)r_E] i_B = 0$$

$$i_B = \frac{\begin{vmatrix} R_s + R_B & v_1 \\ -R_B & 0 \end{vmatrix}}{\begin{vmatrix} R_s + R_B & -R_B \\ -R_B & R_B + (1+\beta)r_E \end{vmatrix}} \frac{R_B v_1}{}$$

$$= \frac{(R_s + R_B)[R_B + (1+\beta)r_E] - R_B^2}{R_B v_1}$$
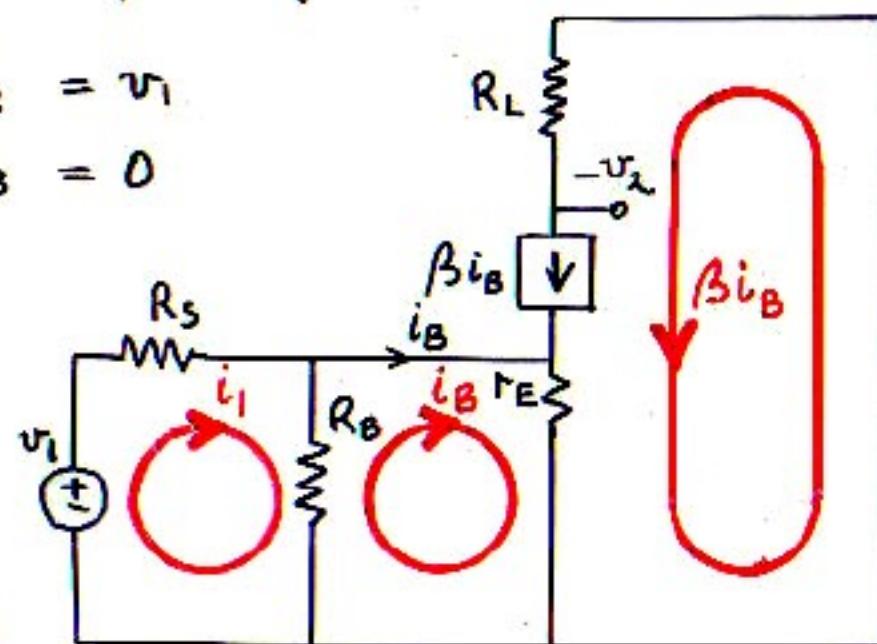
$$= \frac{R_s R_B + (1+\beta)r_E R_s + R_B^2 + (1+\beta)r_E R_B - R_B^2}{R_s R_B + (1+\beta)r_E R_s + R_B^2 + (1+\beta)r_E R_B - R_B^2}$$



Finally, $v_2 = R_L \beta i_B$

which leads to:

$$A_m = \frac{v_2}{v_1} = \frac{\beta R_B R_L}{(1+\beta)r_E R_s + (1+\beta)r_E R_B + R_s R_B}$$

Implementation:


All that is needed is to calculate the driving point impedance across the terminals to which the extra element is to be added, under two conditions:

$$Z_d = Z_{dp} \Big|_{u_{i1}=0} \quad (\text{original input zero})$$

$$Z_n = Z_{dp} \Big|_{u_{o1}=0} \quad (\text{original output nulled})$$

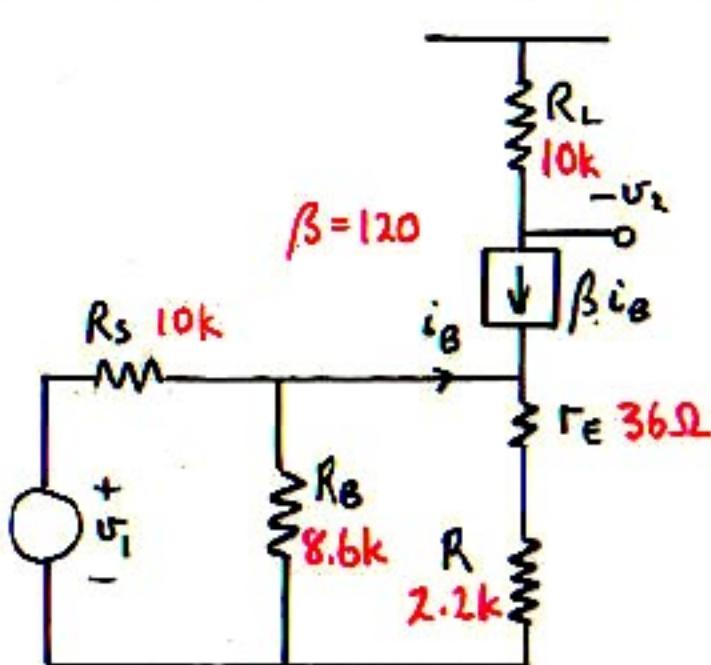
Example: The previously designed CE amplifier

Suppose the gain has been calculated without the emitter bypass capacitance, and the correction factor resulting from addition of the extra element $Z \rightarrow 1/sC_2$ is desired.



Original gain :

$$A_o = \frac{R_L}{R_s + R_B} \frac{\alpha R_L}{R + r_e + (R_s || R_B)/(1+\beta)}$$
$$= 0.46 \frac{10}{2.2 + 0.036 + 0.039}$$
$$= 2.0 \Rightarrow 6\text{dB}$$

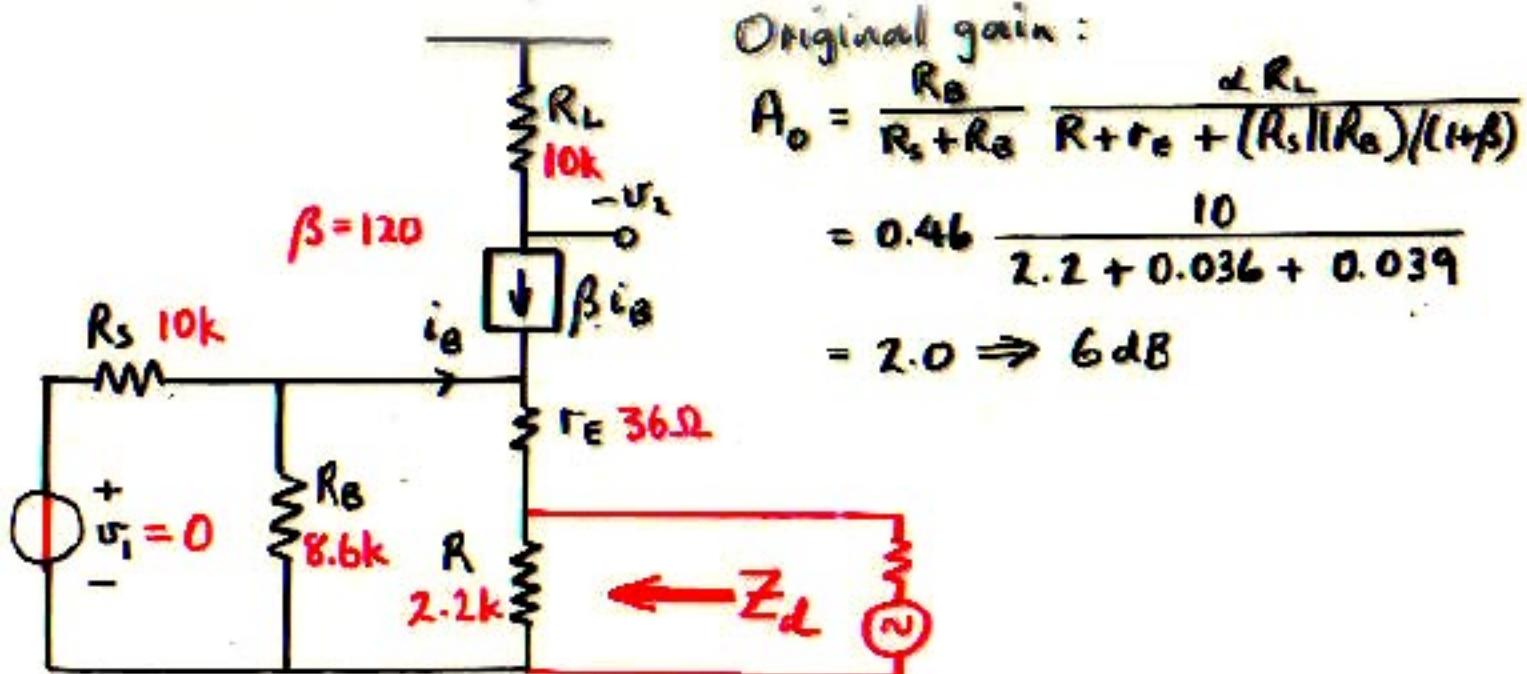


Step 1. Calculate Z_d by shorting $u_{c1} = u_i$, and applying a second injected signal across R :

$$Z_d = R_d = R \parallel [r_e + (R_s || R_B)/(1+\beta)]$$


$$= 2.2 \parallel [0.036 + \underbrace{(10 \parallel 8.6) / 120}_{0.039}]$$


$$= 75.52$$

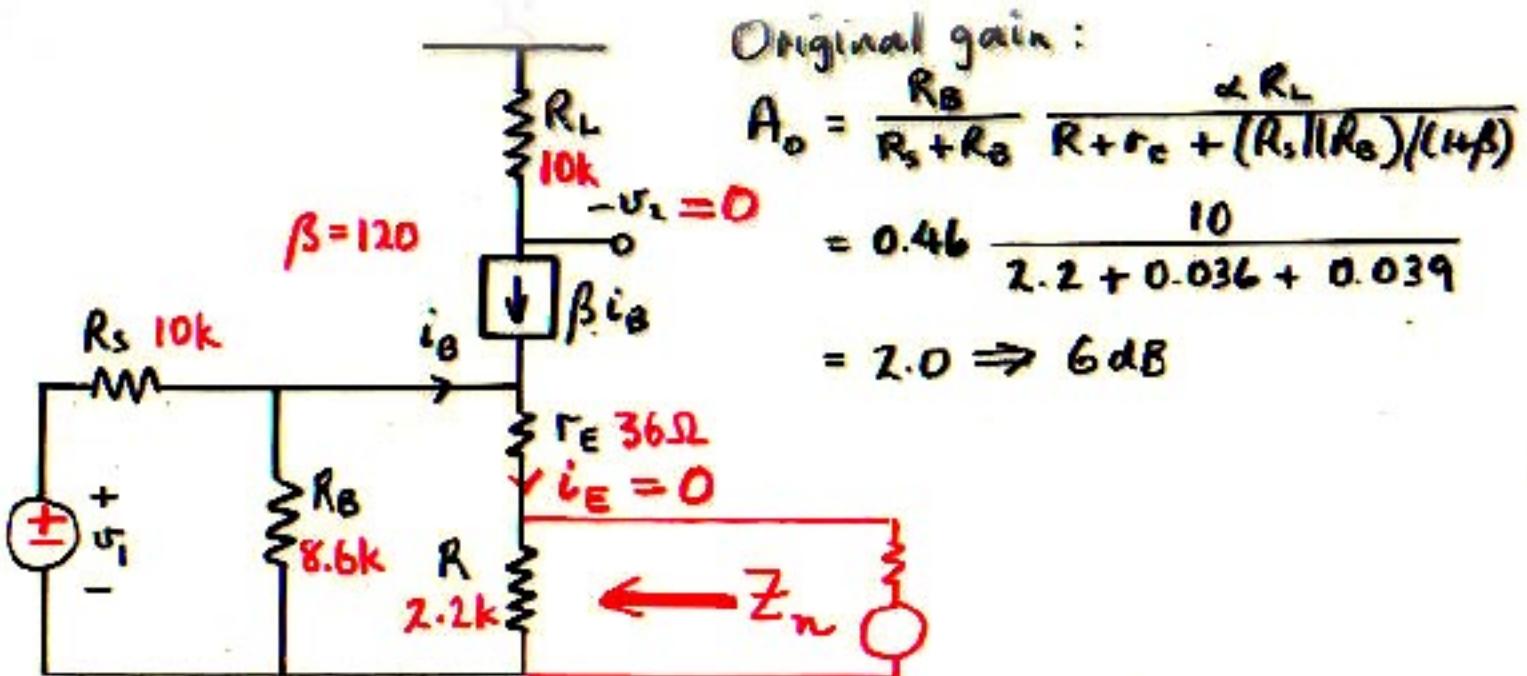


Step 2. Calculate Z_n by applying a second injected signal across R , and adjusting it with respect to v_i to null $v_{o1} = v_2 = 0$. Then, since $v_2 = 0$, $i_E = 0$, hence:

$$Z_n = R_n = R = 2.2\text{k}$$

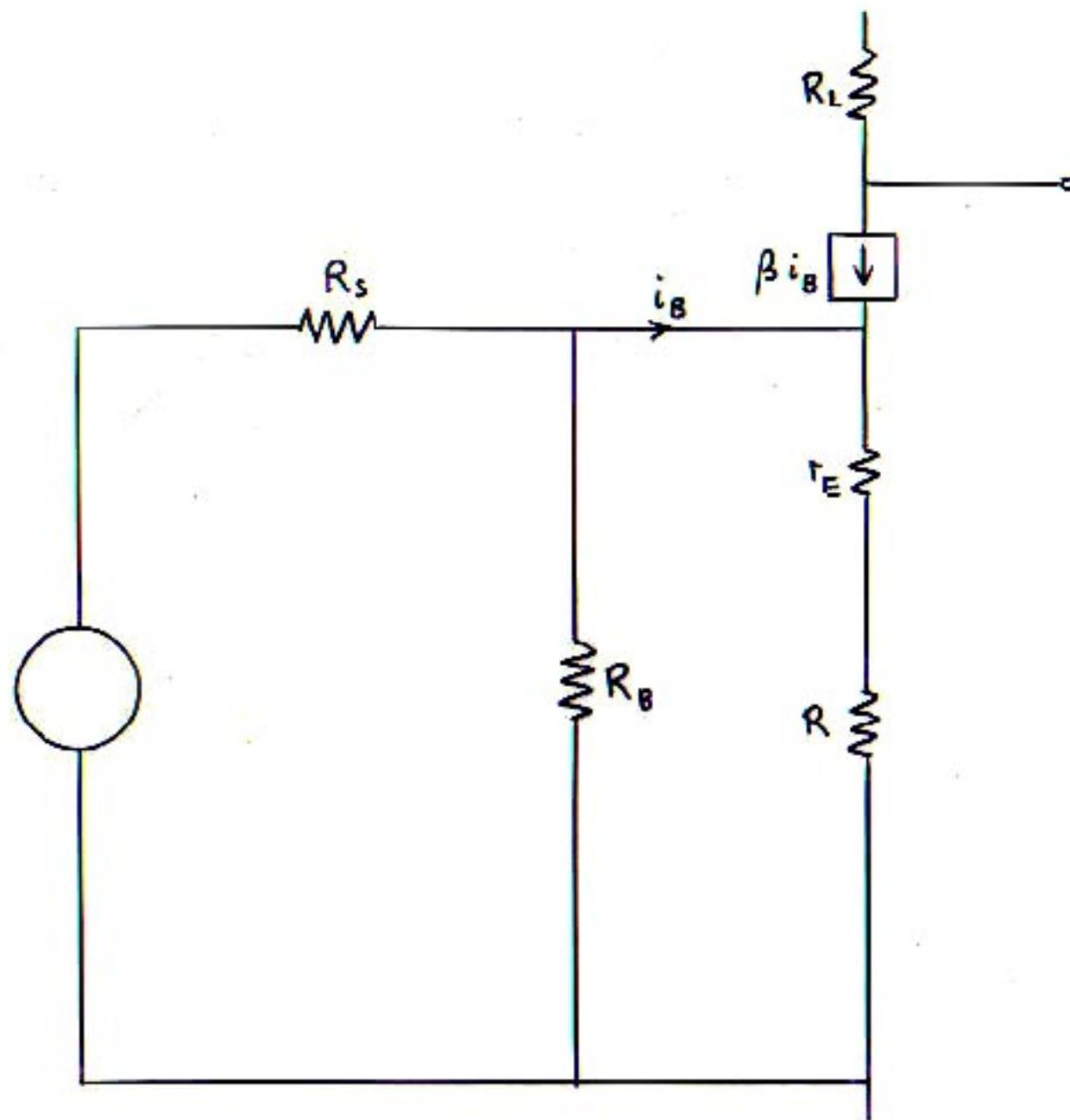


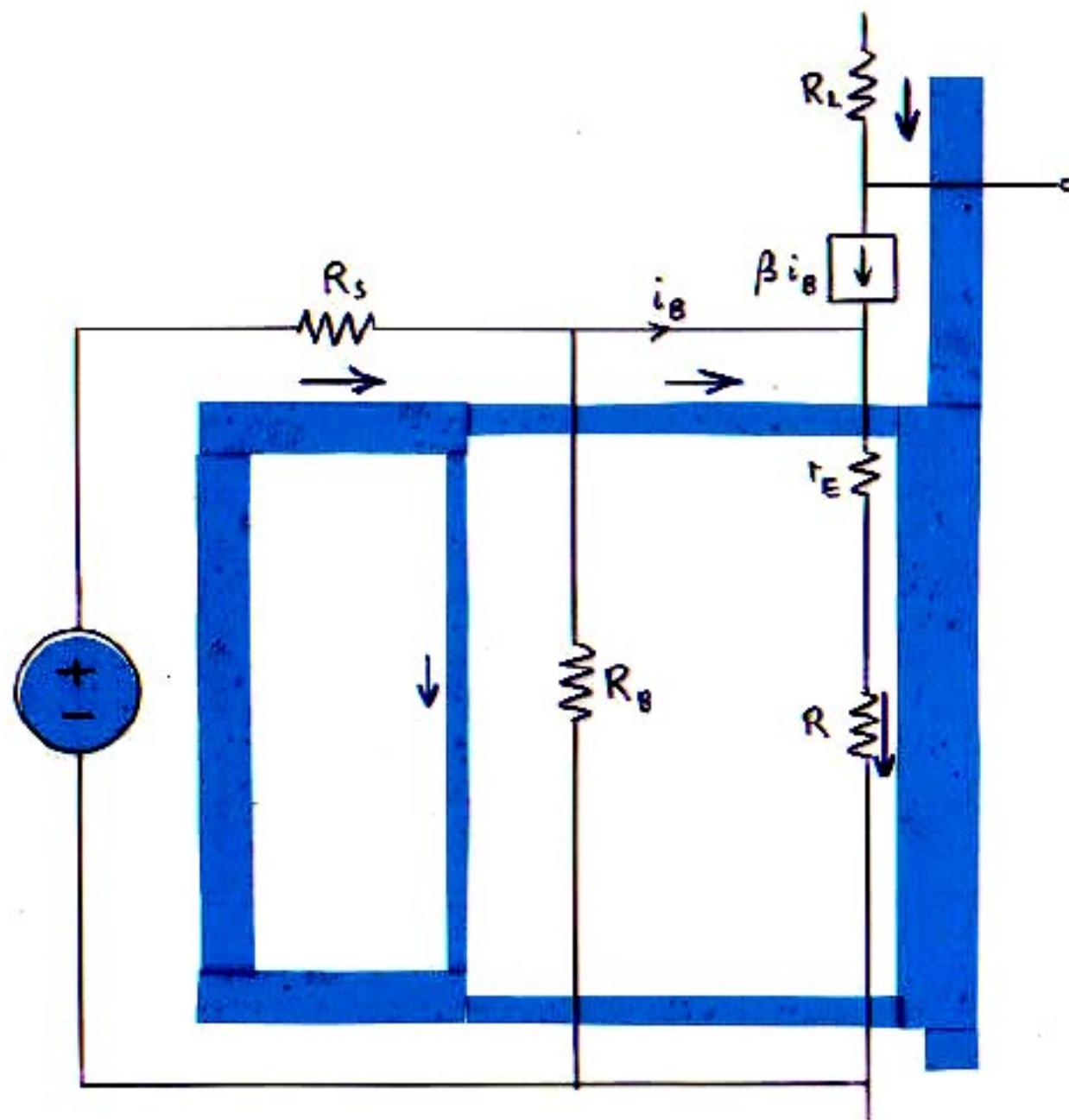


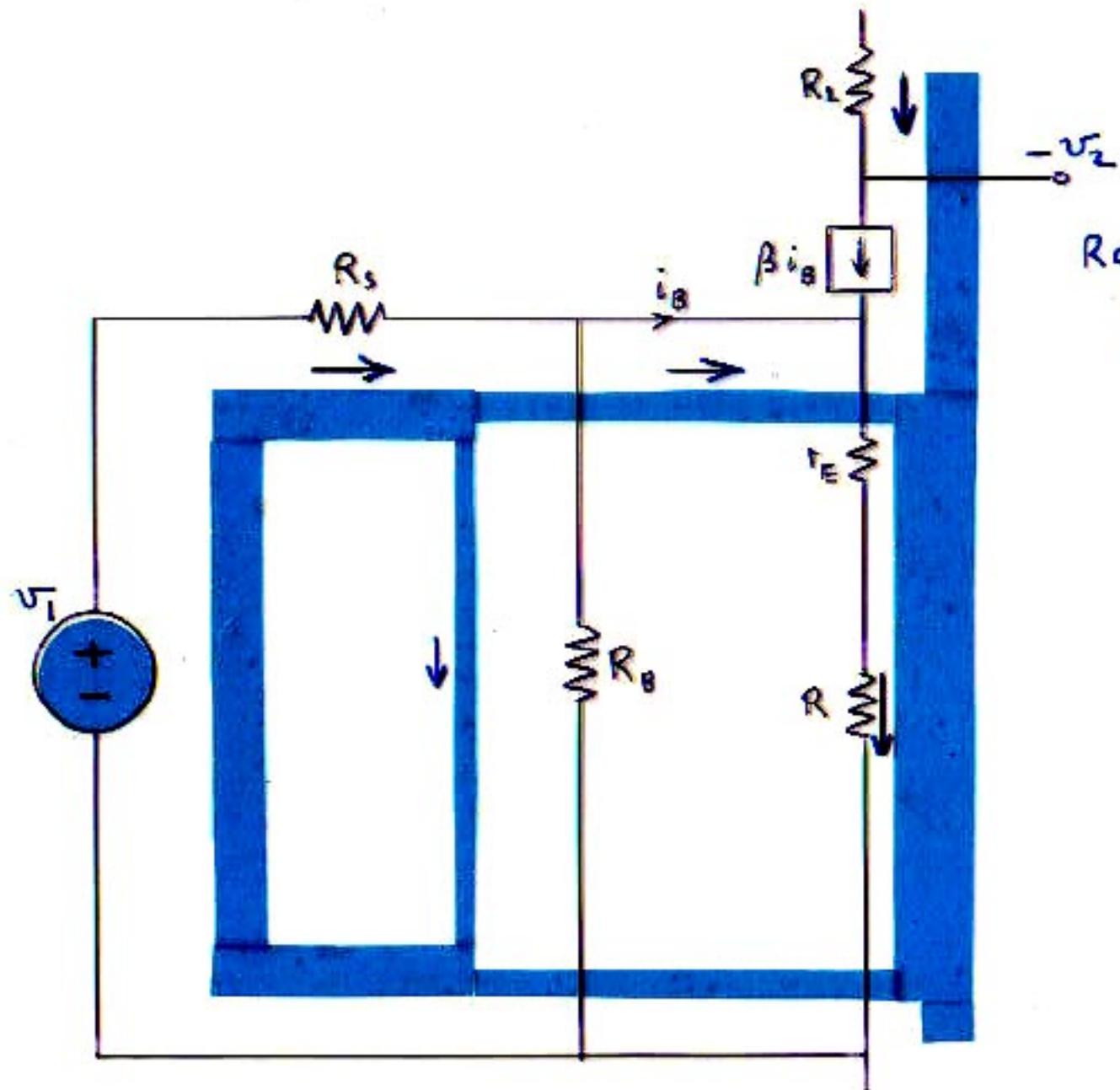



Reference gain:


$$A_o = \frac{v_2}{v_1}$$

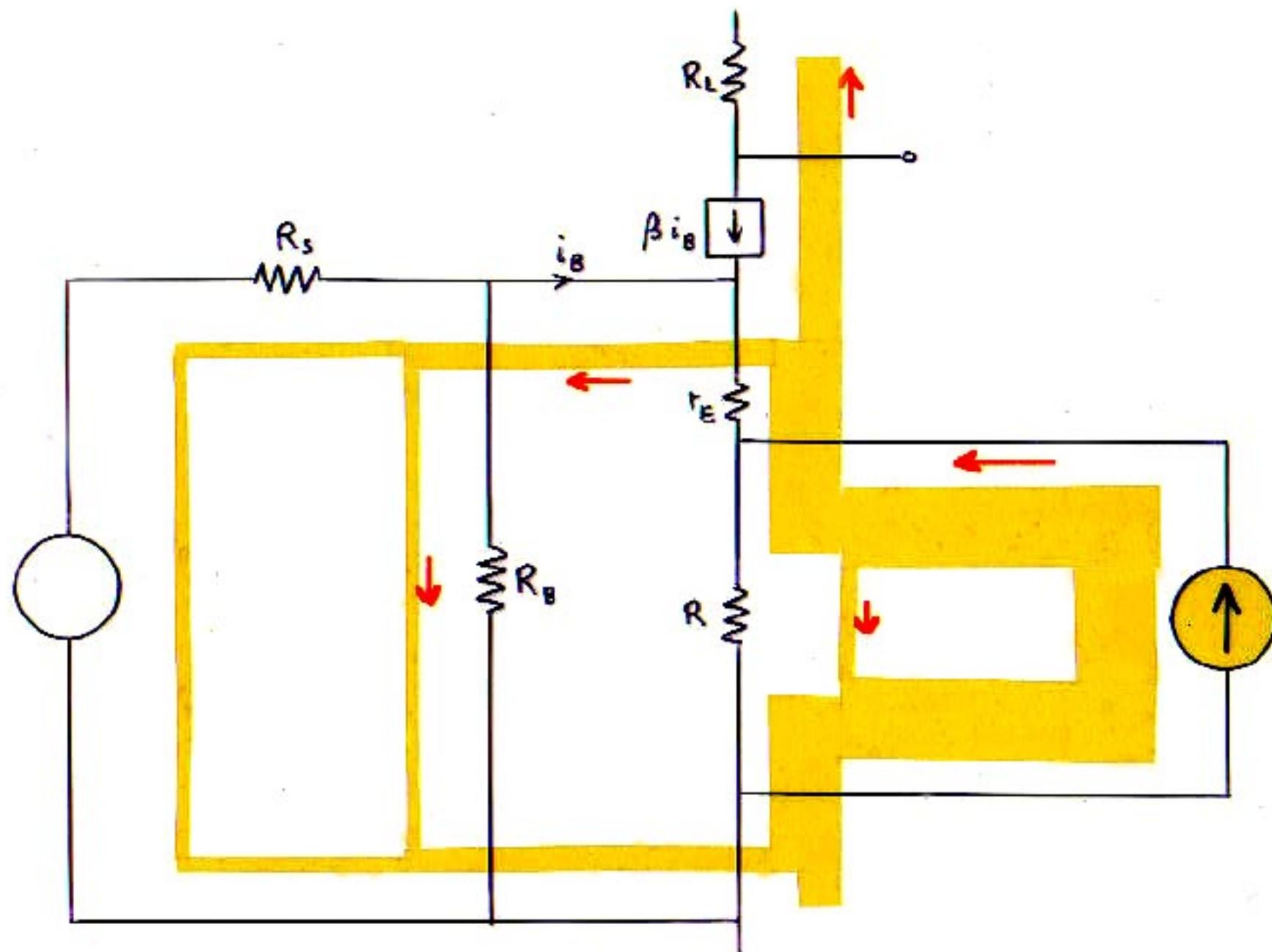

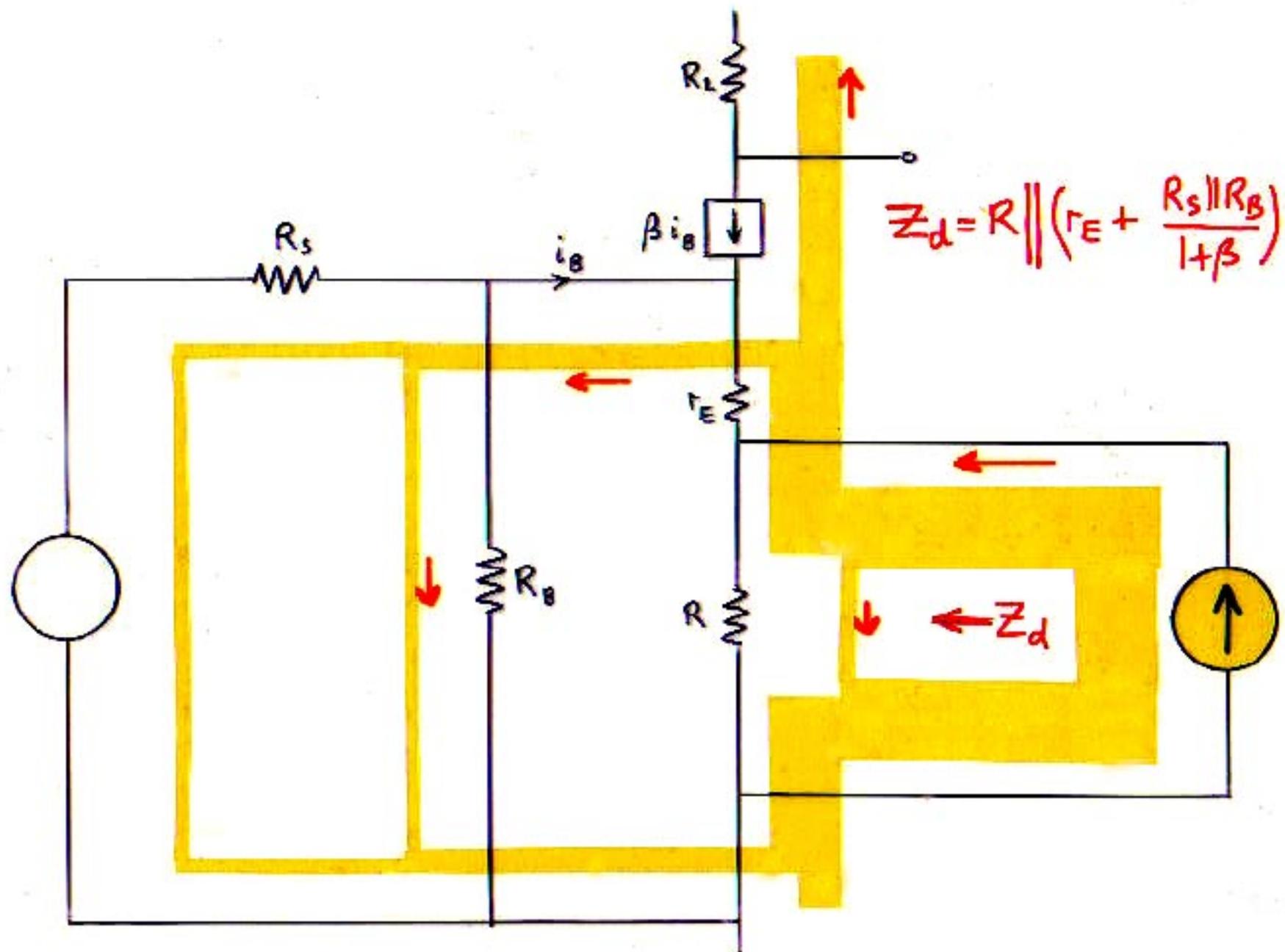

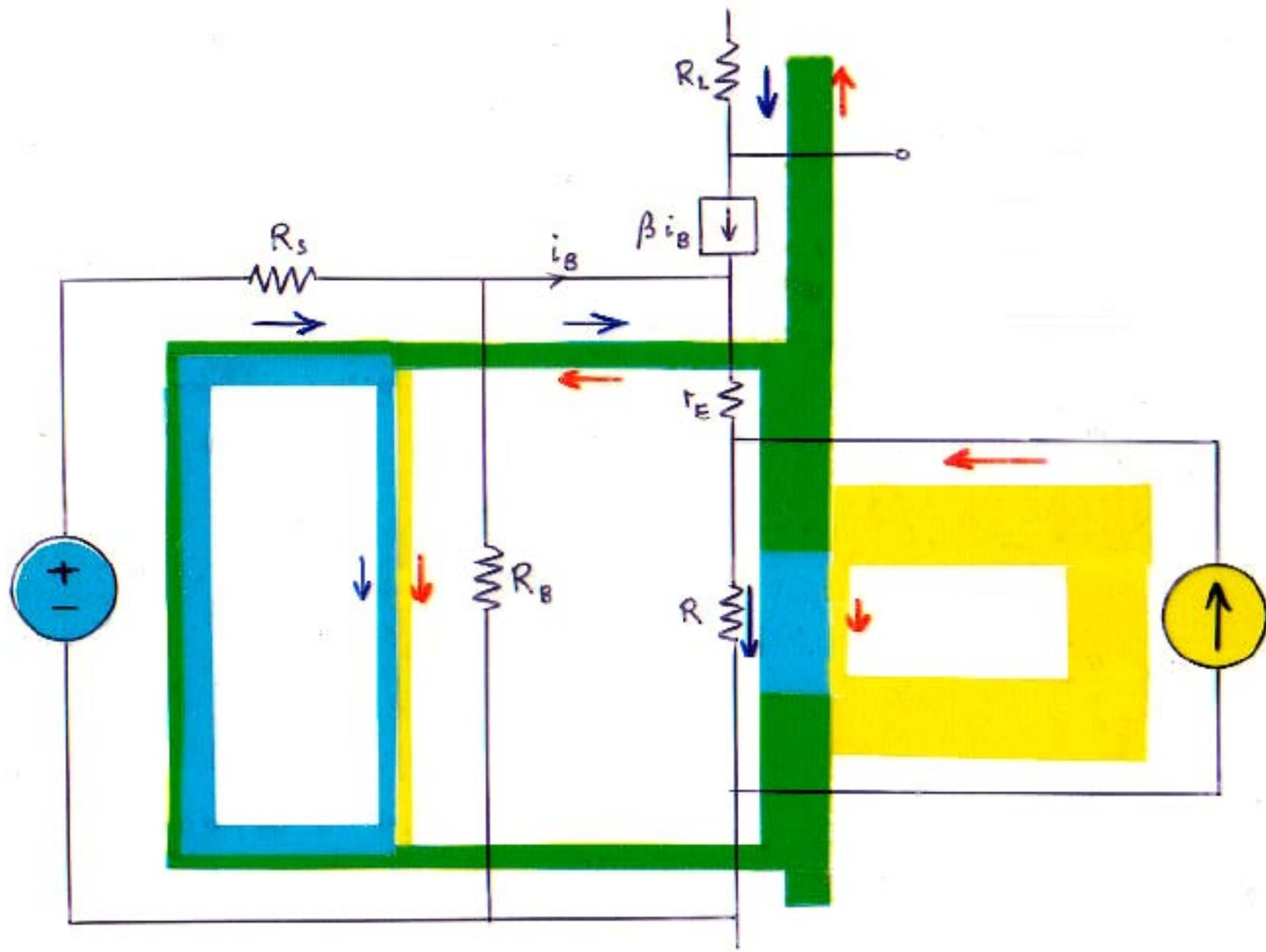


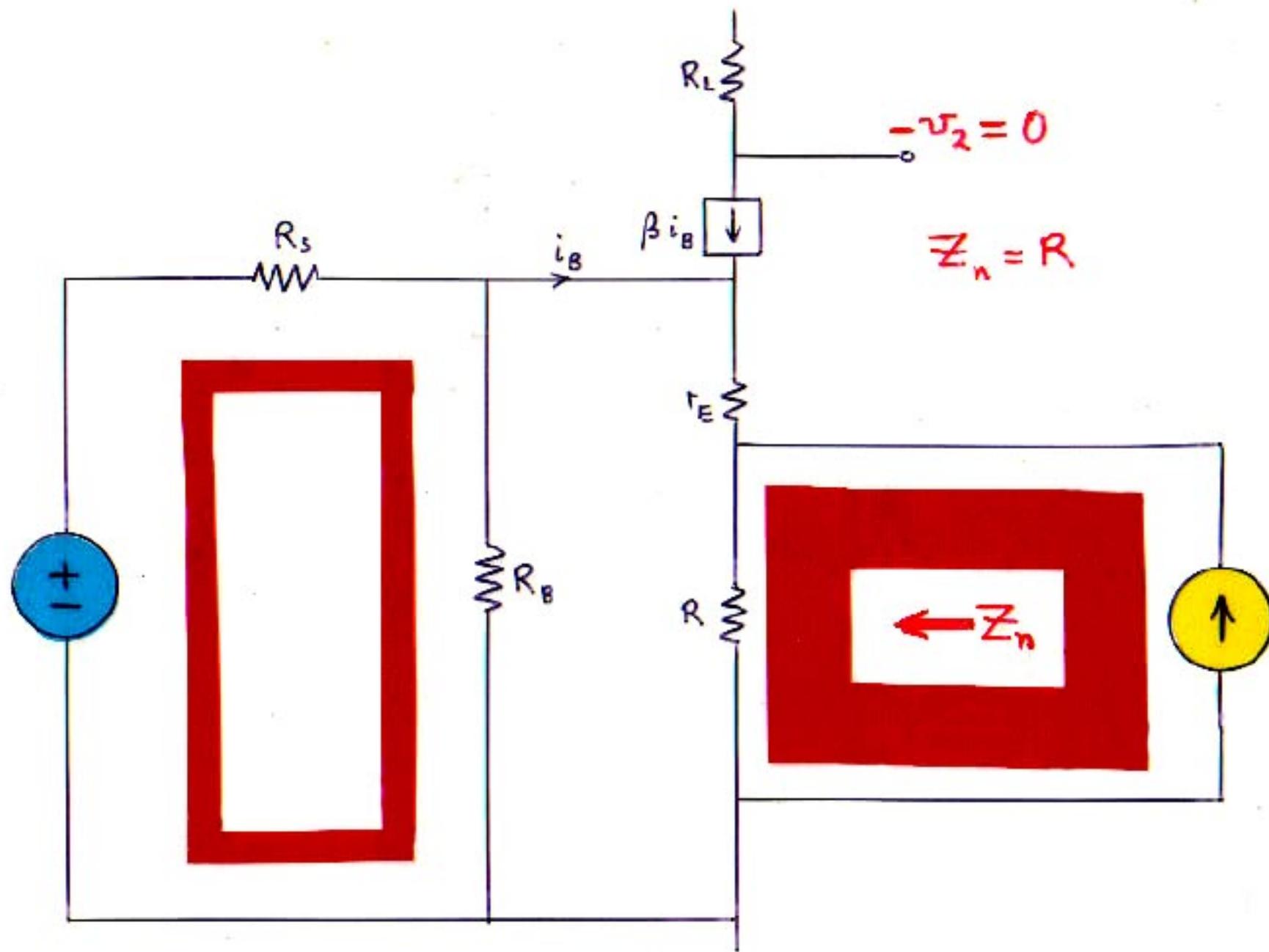

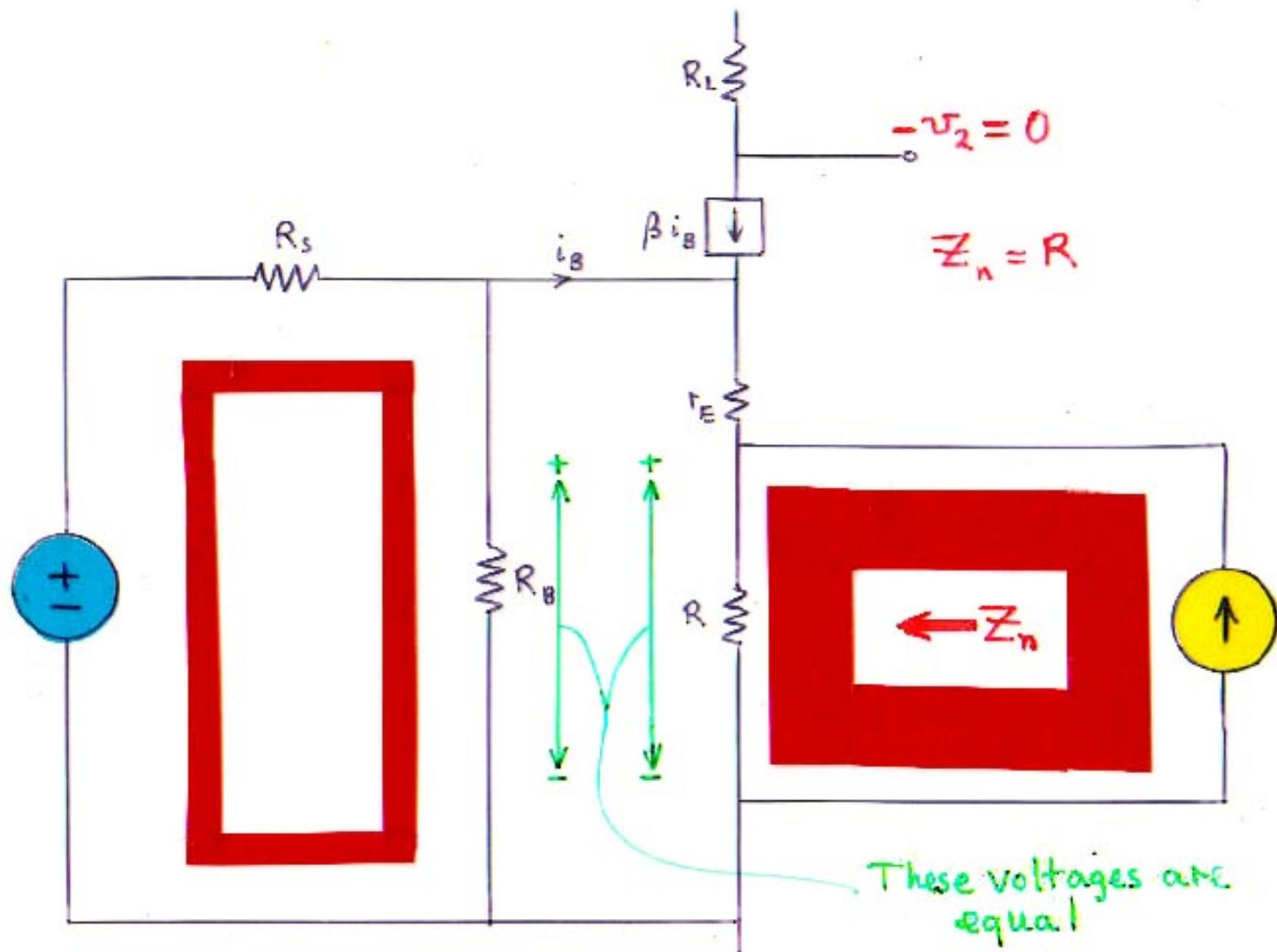

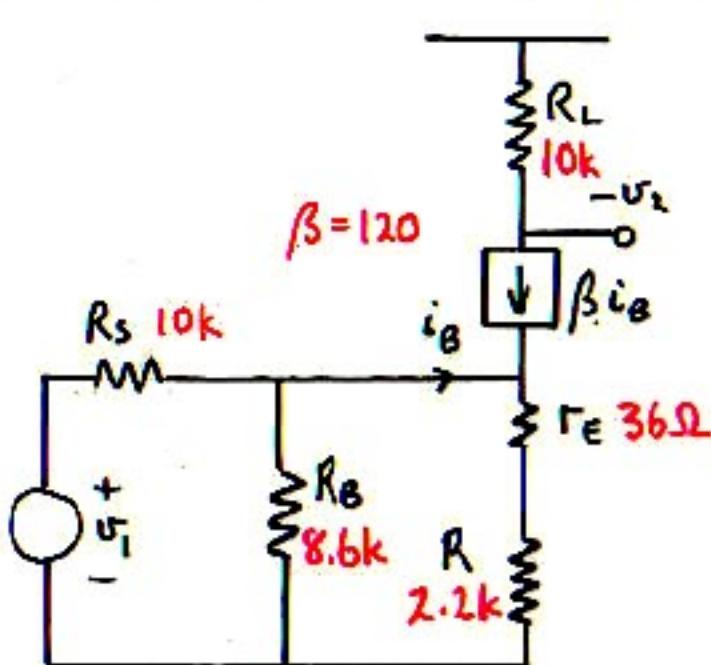
Example: The previously designed CE amplifier

Suppose the gain has been calculated without the emitter bypass capacitance, and the correction factor resulting from addition of the extra element $Z \rightarrow 1/sC_2$ is desired.



Original gain :

$$A_o = \frac{R_L}{R_s + R_B} \frac{\alpha R_L}{R + r_e + (R_s || R_B)/(1+\beta)}$$
$$= 0.46 \frac{10}{2.2 + 0.036 + 0.039}$$
$$= 2.0 \Rightarrow 6\text{dB}$$

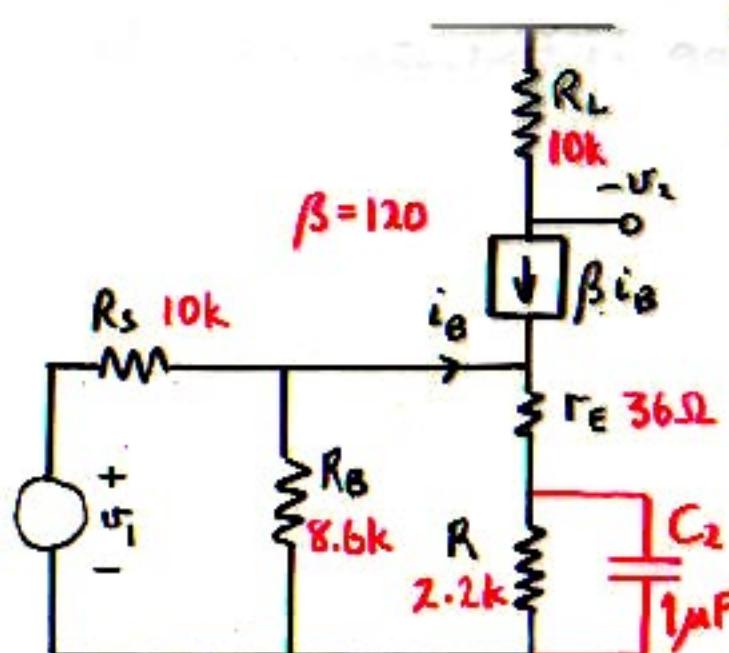

Original gain :

$$A_0 = \frac{R_L}{R_s + R_B} \frac{\alpha R_L}{R + r_E + (R_s || R_B)/(1+\beta)}$$

$$= 0.46 \frac{10}{2.2 + 0.036 + 0.039}$$

$$= 2.0 \Rightarrow 6\text{dB}$$

Hence, corrected gain in presence of $C_2 = 1\mu\text{F}$ bypass capacitance is :

$$A = A_0 \frac{1 + \frac{R_n}{Z}}{1 + \frac{R_d}{Z}} = A_0 \frac{1 + sC_2 R_n}{1 + sC_2 R_d} = A_0 \frac{1 + \frac{s}{\omega_1}}{1 + \frac{s}{\omega_2}} = A_m \frac{1 + \frac{\omega_1}{s}}{1 + \frac{\omega_2}{s}}$$

where

$$\omega_1 \equiv \frac{1}{C_2 R_n} \quad f_1 = \frac{159}{1 \times 2.2} = 72\text{Hz} \quad \omega_2 \equiv \frac{1}{C_2 R_d} = \frac{159}{1 \times 0.075} = 2.1\text{kHz}$$


$$A_m = A_0 \frac{\omega_2}{\omega_1} = A_0 \frac{R_n}{R_d}$$


$$= \frac{R_B}{R_s + R_B} \frac{\alpha R_L}{R + r_E + (R_s || R_B)/(1+\beta)} \frac{R[R + r_E + (R_s || R_B)/(1+\beta)]}{R[r_E + (R_s || R_B)/(1+\beta)]}$$

$$= \frac{R_B}{R_s + R_B} \frac{\alpha R_L}{r_E + (R_s || R_B)/(1+\beta)} = 62 \Rightarrow 36\text{dB}$$

NOTE: Nulling a voltage is not the same as
shorting it!

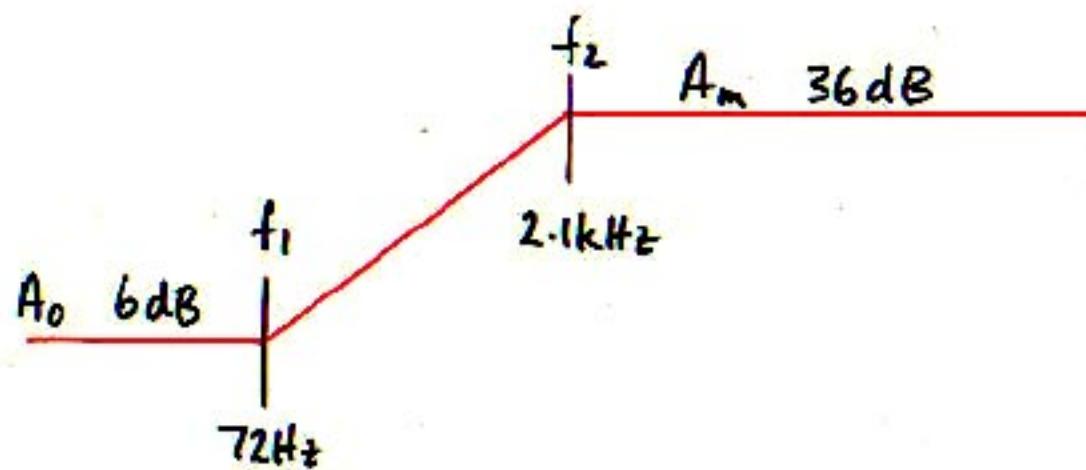NOTE: the null double injection calculation is
easier than the single injection calculation!



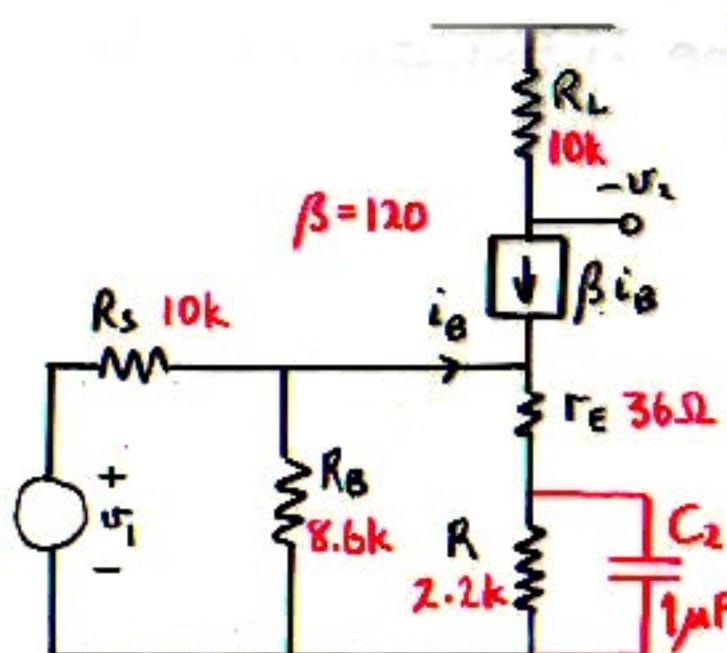

Original gain :

$$A_0 = \frac{R_L}{R_s + R_B} \frac{\alpha R_L}{R + r_E + (R_s || R_B)/(1+\beta)}$$

$$= 0.46 \frac{10}{2.2 + 0.036 + 0.039}$$

$$= 2.0 \Rightarrow 6\text{dB}$$

Hence, corrected gain in presence of $C_2 = 1\mu\text{F}$ bypass capacitance is :

$$A = A_0 \frac{1 + \frac{R_n}{Z}}{1 + \frac{R_d}{Z}} = A_0 \frac{1 + sC_2 R_n}{1 + sC_2 R_d} = A_0 \frac{1 + \frac{s}{\omega_1}}{1 + \frac{s}{\omega_2}} = A_m \frac{1 + \frac{\omega_1}{s}}{1 + \frac{\omega_2}{s}}$$


where


$$\omega_1 \equiv \frac{1}{C_2 R_n} \quad f_1 = \frac{159}{1 \times 2.2} = 72\text{Hz} \quad \omega_2 \equiv \frac{1}{C_2 R_d} = \frac{159}{1 \times 0.075} = 2.1\text{kHz}$$

$$A_m = A_0 \frac{\omega_2}{\omega_1} = A_0 \frac{R_n}{R_d}$$

$$= \frac{R_B}{R_s + R_B} \frac{\alpha R_L}{R + r_E + (R_s || R_B)/(1+\beta)} \frac{R[R + r_E + (R_s || R_B)/(1+\beta)]}{R[r_E + (R_s || R_B)/(1+\beta)]}$$

$$= \frac{R_B}{R_s + R_B} \frac{\alpha R_L}{r_E + (R_s || R_B)/(1+\beta)} = 62 \Rightarrow 36\text{dB}$$

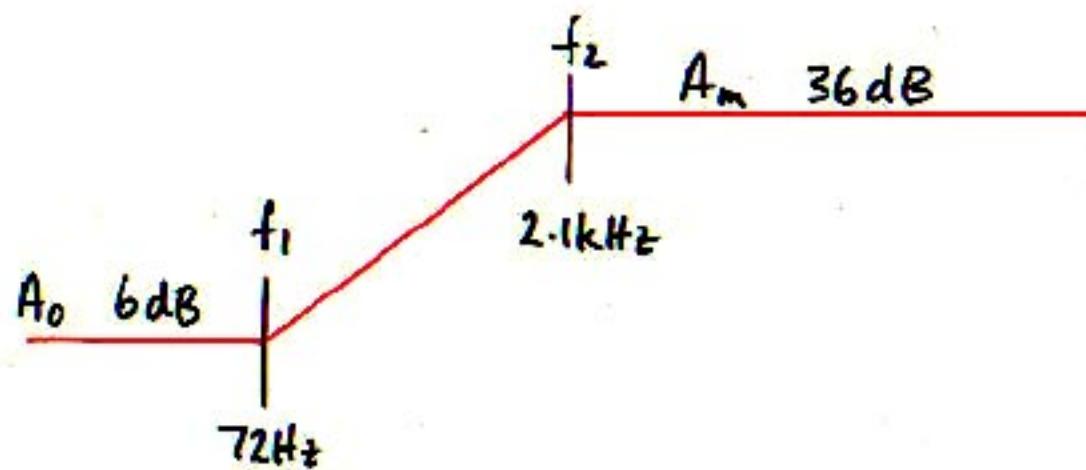

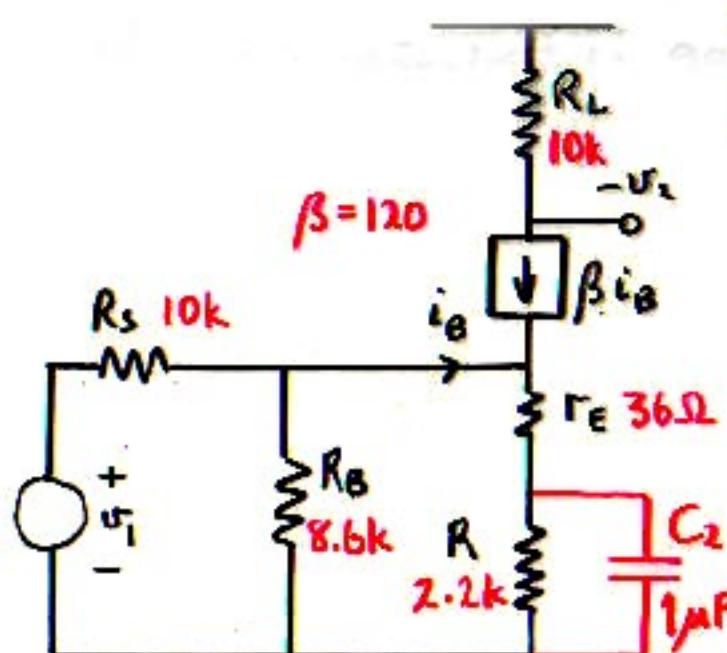

Original gain :

$$A_0 = \frac{R_L}{R_s + R_B} \frac{\alpha R_L}{R + r_E + (R_s || R_B)/(1+\beta)}$$

$$= 0.46 \frac{10}{2.2 + 0.036 + 0.039}$$

$$= 2.0 \Rightarrow 6\text{dB}$$

Hence, corrected gain in presence of $C_2 = 1\mu\text{F}$ bypass capacitance is :

$$A = A_0 \frac{1 + \frac{R_n}{Z}}{1 + \frac{R_d}{Z}} = A_0 \frac{1 + sC_2 R_n}{1 + sC_2 R_d} = A_0 \frac{1 + \frac{s}{\omega_1}}{1 + \frac{s}{\omega_2}} = A_m \frac{1 + \frac{\omega_1}{s}}{1 + \frac{\omega_2}{s}}$$


where

$$\omega_1 \equiv \frac{1}{C_2 R_n} \quad f_1 = \frac{159}{1 \times 2.2} = 72\text{Hz} \quad \omega_2 \equiv \frac{1}{C_2 R_d} = \frac{159}{1 \times 0.075} = 2.1\text{kHz}$$

$$A_m = A_0 \frac{\omega_2}{\omega_1} = A_0 \frac{R_n}{R_d}$$


$$= \frac{R_B}{R_s + R_B} \frac{\alpha R_L}{R + r_E + (R_s || R_B)/(1+\beta)} \frac{R[R + r_E + (R_s || R_B)/(1+\beta)]}{R[r_E + (R_s || R_B)/(1+\beta)]}$$


$$= \frac{R_B}{R_s + R_B} \frac{\alpha R_L}{r_E + (R_s || R_B)/(1+\beta)} = 62 \Rightarrow 36\text{dB}$$

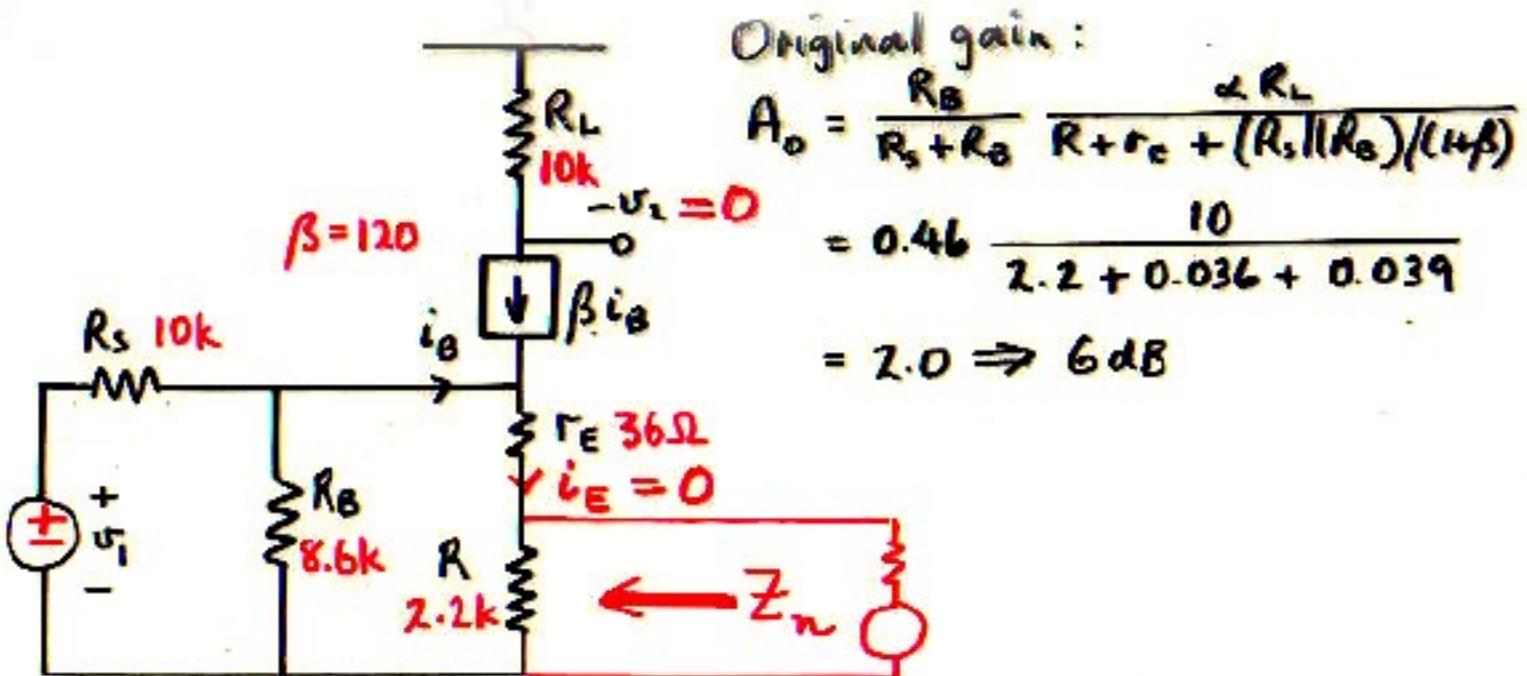


Step 2. Calculate Z_n by applying a second injected signal across R , and adjusting it with respect to v_i to null $v_{o1} = v_2 = 0$. Then, since $v_2 = 0$, $i_E = 0$, hence:

$$Z_n = R_n = R = 2.2\text{k}$$

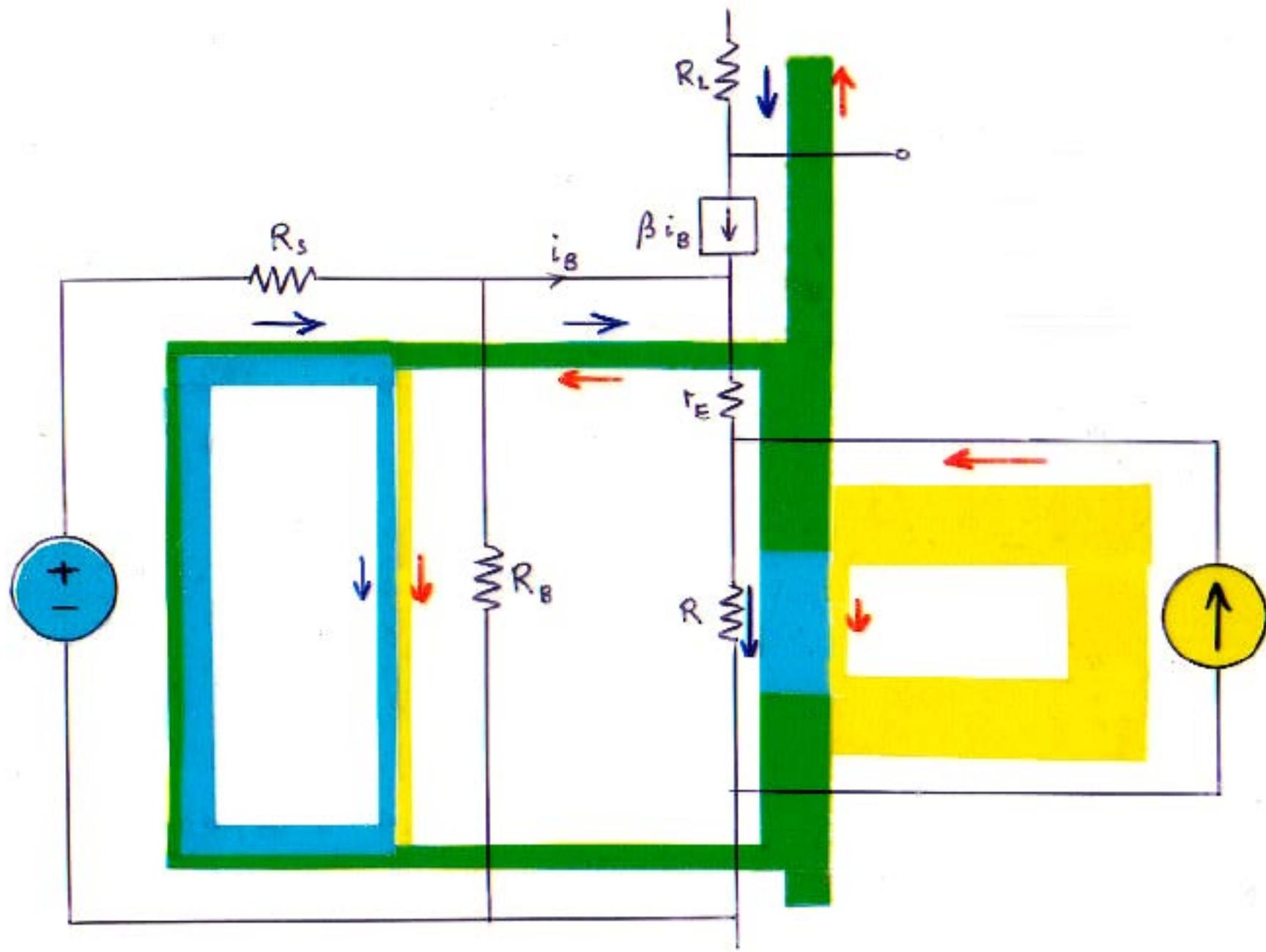

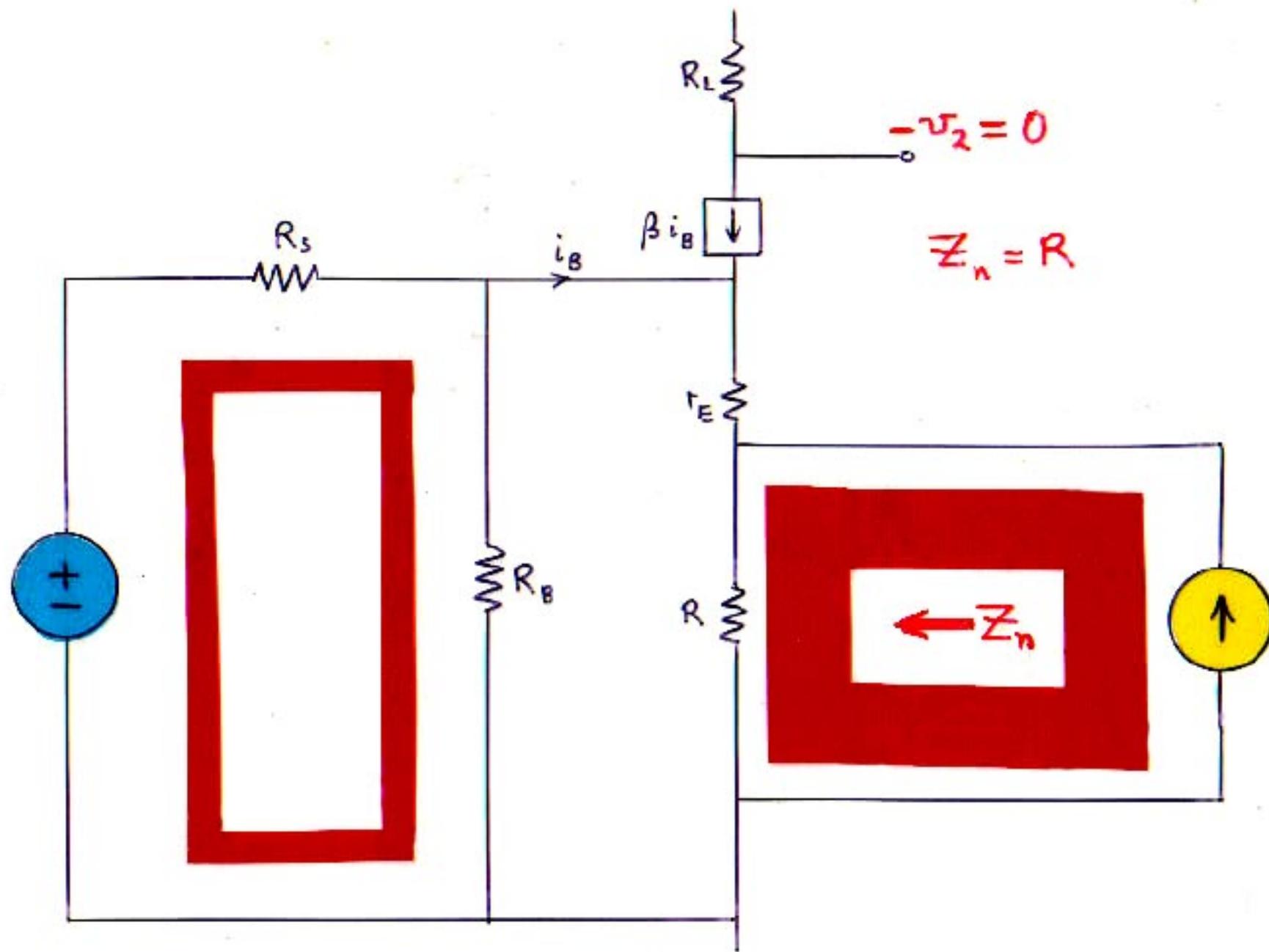

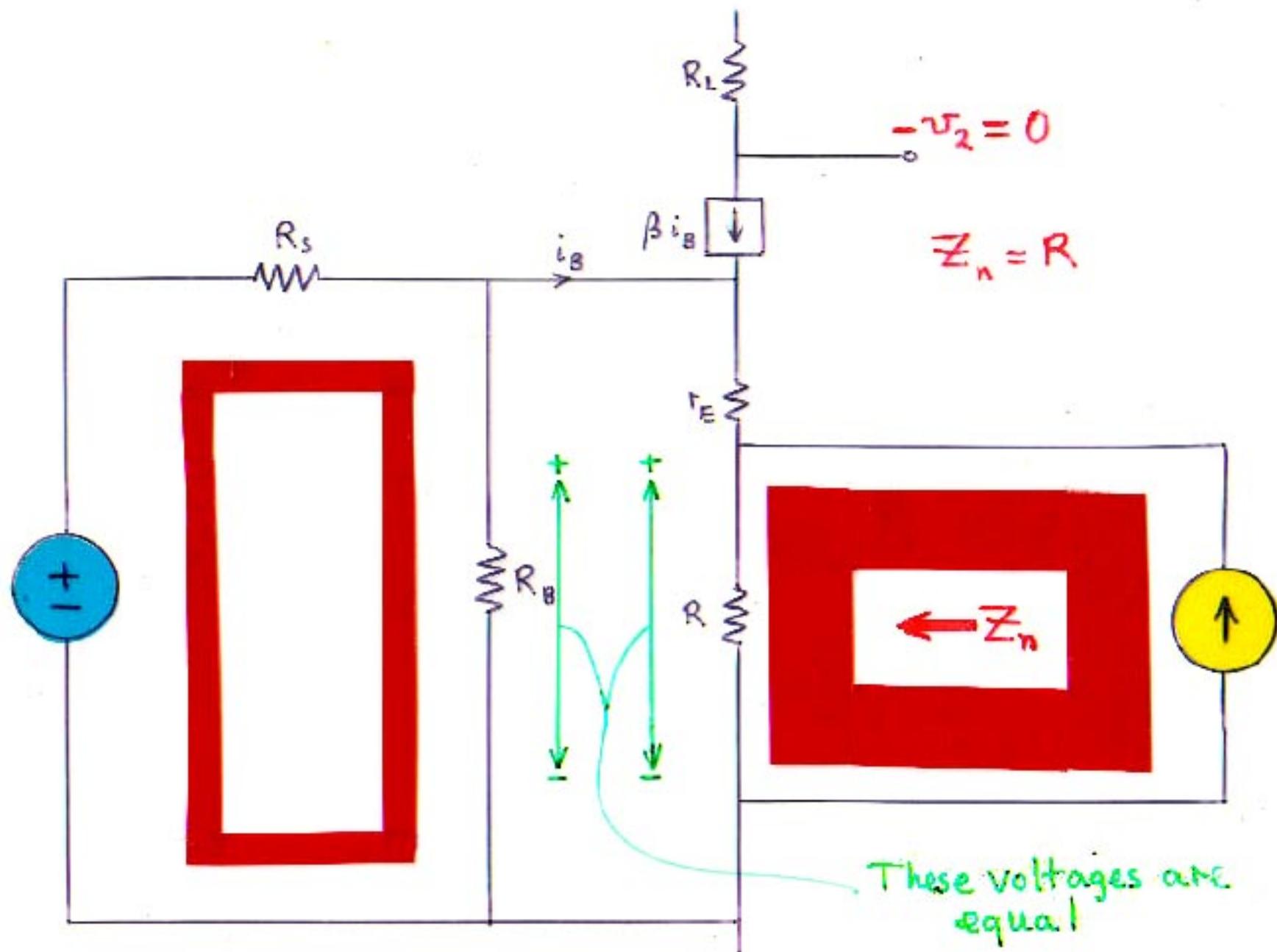

The Extra Element Theorem as derived applies to
the correction factor resulting from an extra shunt element.

There is a corresponding form to find the correction factor
resulting from an extra series element:

$$\text{reference gain} \downarrow$$

$$\text{gain } |z| = \text{gain} |_{z=\infty} \frac{1 + \frac{z_n}{z}}{1 + \frac{z_d}{z}}$$

$$= \text{gain} |_{z=\infty} \frac{\frac{z_n}{z}}{\frac{z_d}{z}} \frac{\frac{z}{z_n} + 1}{\frac{z}{z_d} + 1}$$

$$= \frac{z_n}{z_d} \text{gain} |_{z=\infty} \frac{1 + \frac{z}{z_n}}{1 + \frac{z}{z_d}}$$

The Extra Element Theorem as derived applies to the correction factor resulting from an extra shunt element.

There is a corresponding form to find the correction factor resulting from an extra series element:

$$\text{reference gain} \downarrow$$

$$\text{gain } |_{Z} = \text{gain } |_{Z=\infty} \frac{1 + \frac{z_n}{Z}}{1 + \frac{z_d}{Z}}$$

$$= \text{gain } |_{Z=\infty} \frac{\frac{z_n}{Z}}{\frac{z_d}{Z}} \frac{\frac{Z}{z_n} + 1}{\frac{Z}{z_d} + 1}$$


$$\text{reference gain} \downarrow$$

$$= \text{gain } |_{Z=0} \frac{1 + \frac{Z}{z_n}}{1 + \frac{Z}{z_d}}$$

$$= \left(\frac{z_n}{z_d} \cdot \text{gain } |_{Z=\infty} \right) \frac{1 + \frac{Z}{z_n}}{1 + \frac{Z}{z_d}}$$

This must be
the gain when $Z=0$

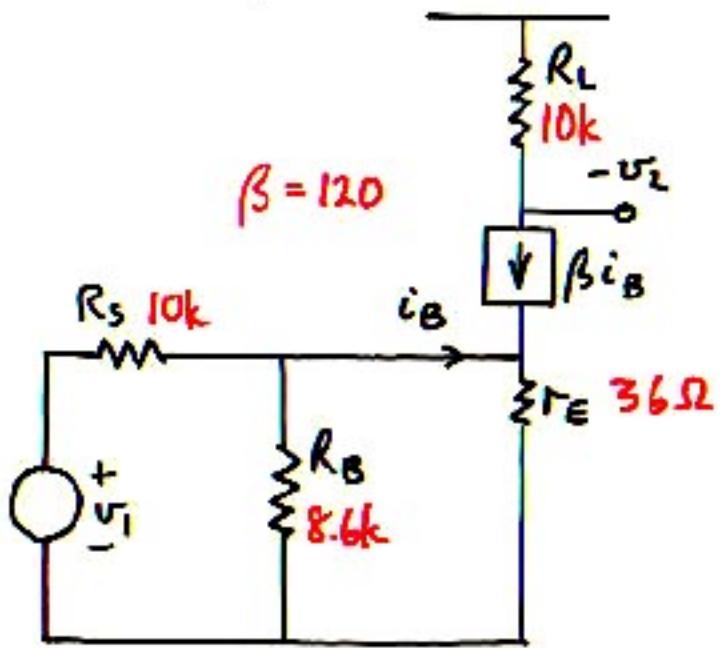
Example: An alternative to the method of the previous example is to find the correction factor to the midband gain A_m resulting from addition of the series "extra element" $Z \rightarrow R \parallel 1/\text{SC}$.



Original gain:


$$A_m = \frac{R_L}{R_s + R_B} \frac{\alpha R_L}{r_E + (R_s || R_B)/(1+\beta)}$$

$$= 62 \Rightarrow 36 \text{ dB}$$

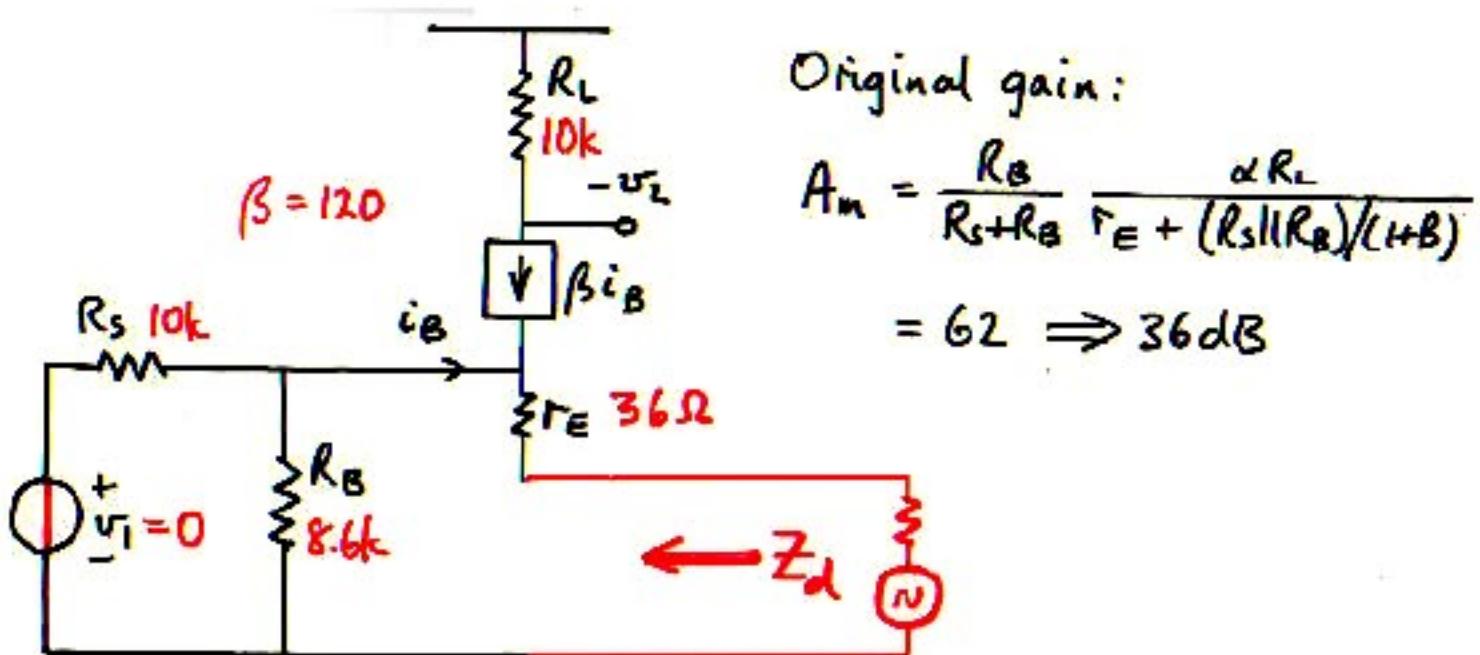

Step 1. Calculate Z_d by shorting $v_{i1} = v_i$ and applying a second injected signal in series with r_E :

$$Z_d = R_d' = r_E + (R_s || R_B)/(1+\beta)$$

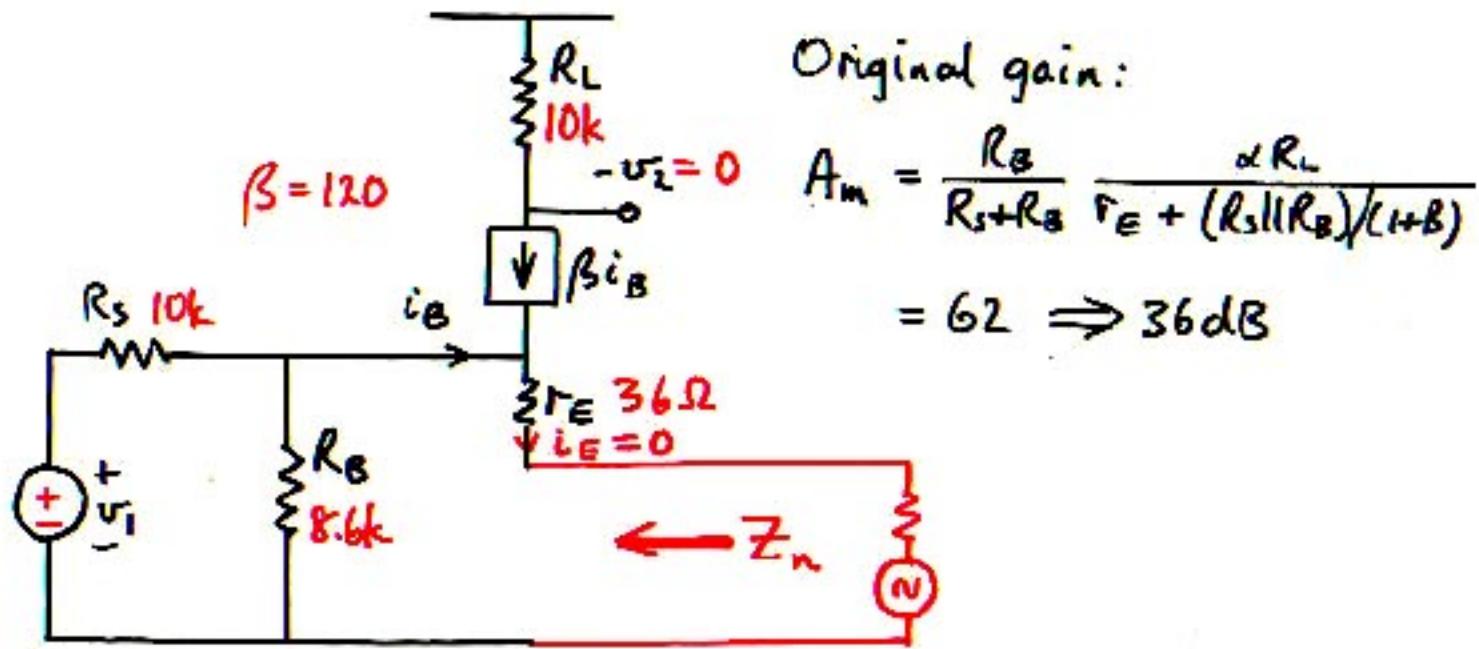

Original gain:


$$A_m = \frac{R_E}{R_s + R_E} \frac{\alpha R_L}{r_E + (R_s || R_E)/(1+\beta)}$$

$$= 62 \Rightarrow 36 \text{ dB}$$

Step 2. Calculate Z_n by applying a second injected signal in series with r_E , and adjusting it with respect to v_i to null $v_{o1} = v_2 = 0$.

Then, since $v_2 = 0$, $i_E = 0$, hence

$$Z_n = R_n' = \infty$$

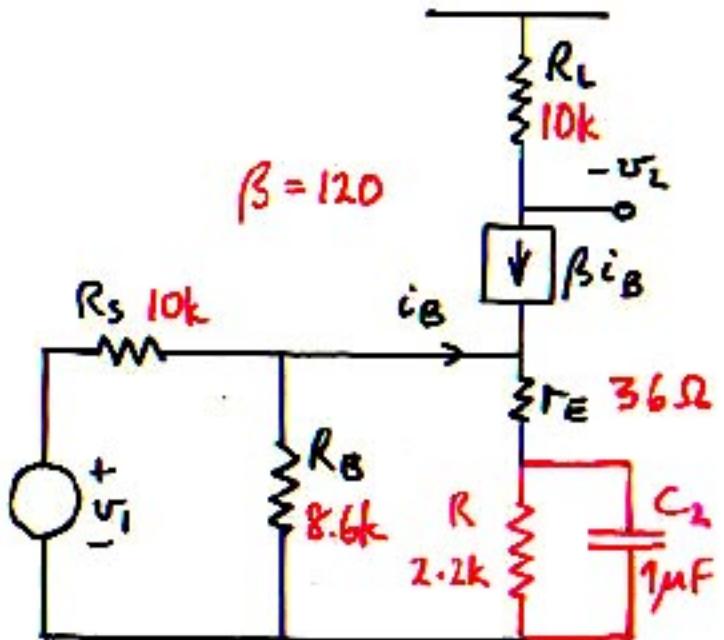

Original gain:

$$A_m = \frac{R_L}{R_s + R_B} \frac{\alpha R_L}{r_E + (R_s || R_B)/(1+\beta)}$$

$$= 62 \Rightarrow 36 \text{ dB}$$

Hence, corrected gain in presence of $R_L || 1/sC_2$ is:

$$A = A_m \frac{1 + \frac{R_L}{R_d'}}{1 + \frac{R}{R_d'}} = A_m \frac{1}{1 + \frac{R}{R_d'} \frac{1}{1 + sC_2 R}} = A_m \frac{1 + 1/sC_2 R}{1 + 1/sC_2 (R || R_d')}$$

However, $R || R_d' = R_d$, so

$$A = A_m \frac{1 + 1/sC_2 R}{1 + 1/sC_2 R_d} \longrightarrow \text{same result as before}$$

Generalization: Extra Element Theorem - #1

There are two forms of Extra Element Theorem:

1.

$$\text{gain}|_z = \text{gain}|_{z=\infty} \frac{1 + \frac{z_n}{z}}{1 + \frac{z_d}{z}}$$

Provides a correction factor for an extra element added in shunt across a node pair.

2.

$$\text{gain}|_z = \text{gain}|_{z=0} \frac{1 + \frac{z}{z_n}}{1 + \frac{z}{z_d}}$$

Provides a correction factor for an extra element added in series with a branch.

The "extra element" z can be any two-terminal combination of impedances.

Note that in all cases the null double injection calculation is easier than the single injection calculation.


This results from use of the null condition
(which makes several other quantities zero);

and


because the relation between u_{i_1} and u_{i_2} to produce the null is never needed — only the null itself is used.

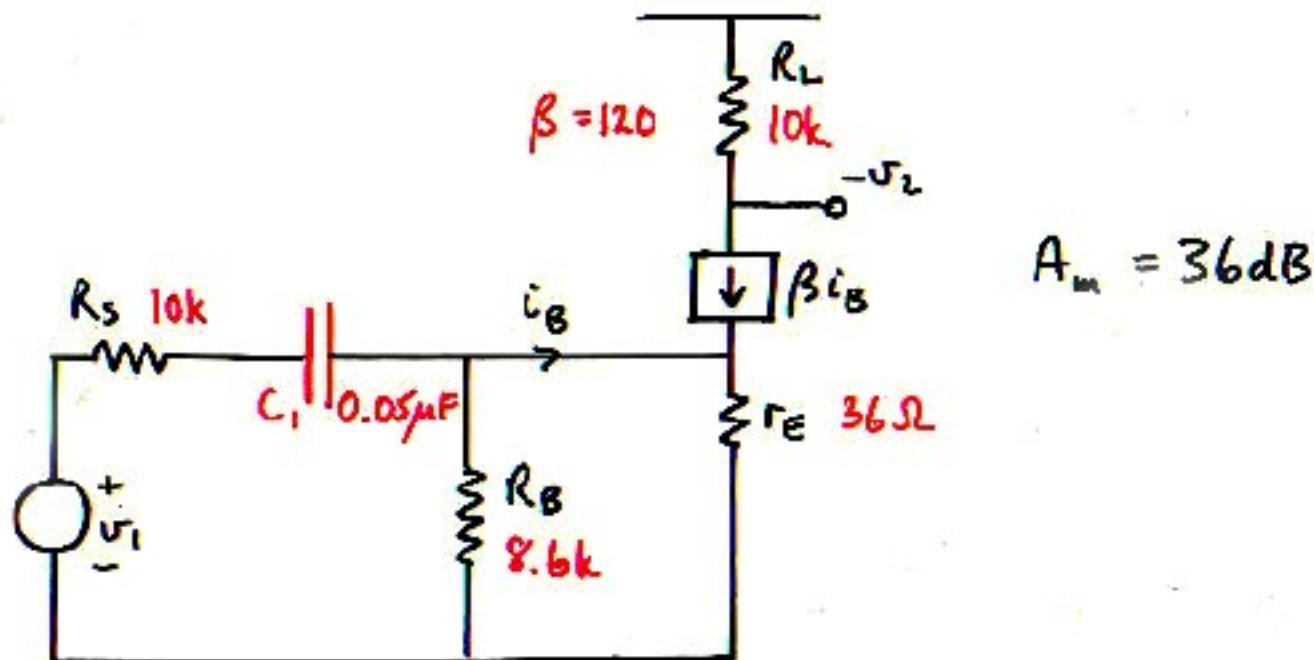Exercise


In the CE amplifier stage, find the correction factor to the midband gain A_m resulting from inclusion of the coupling capacitance $C_1 = 0.05\mu F$:



Exercise Solution

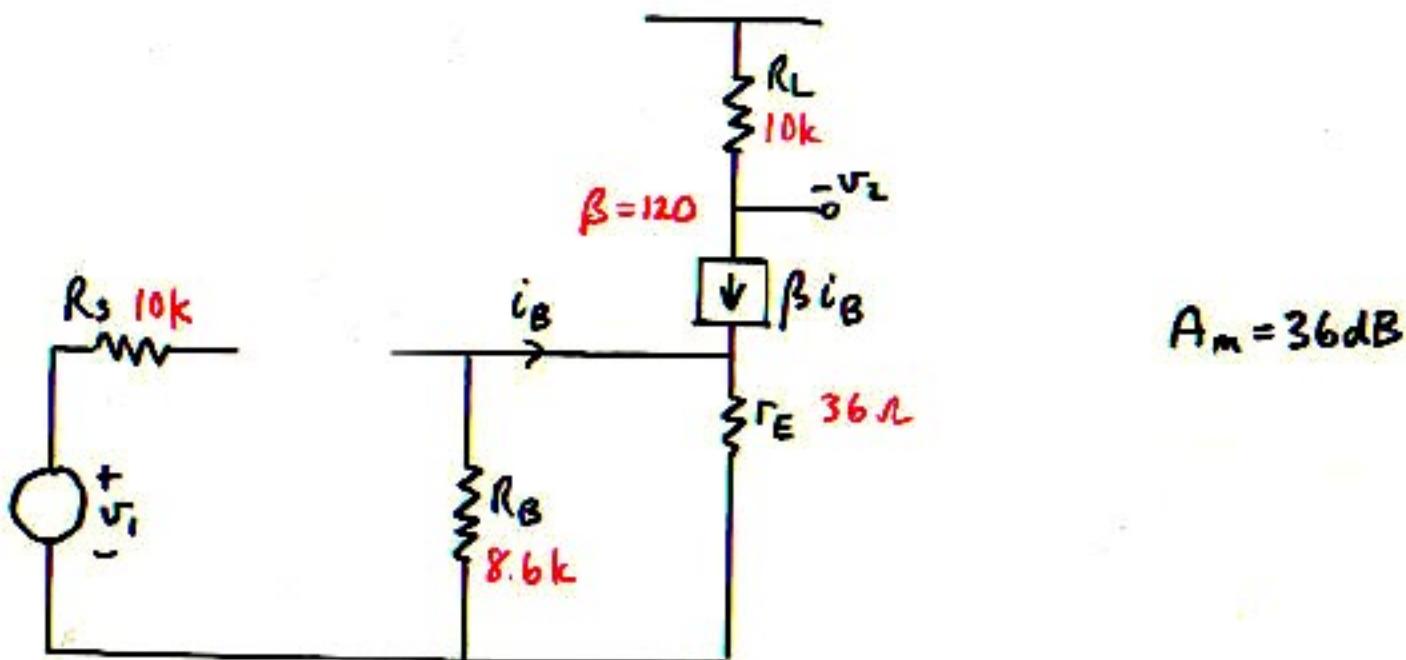


Exercise Solution

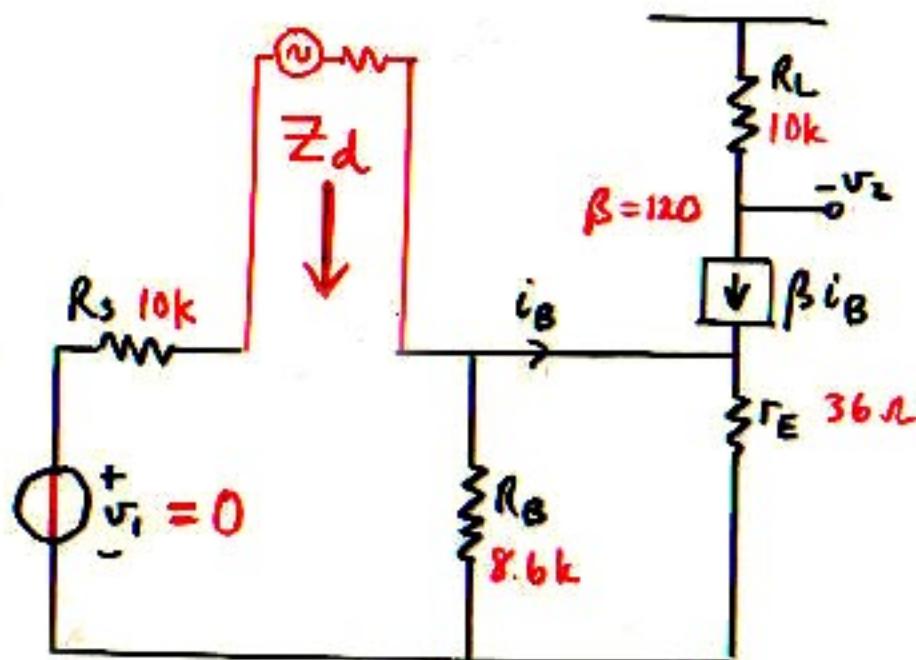

$$A_m = 36 \text{ dB}$$

Exercise Solution

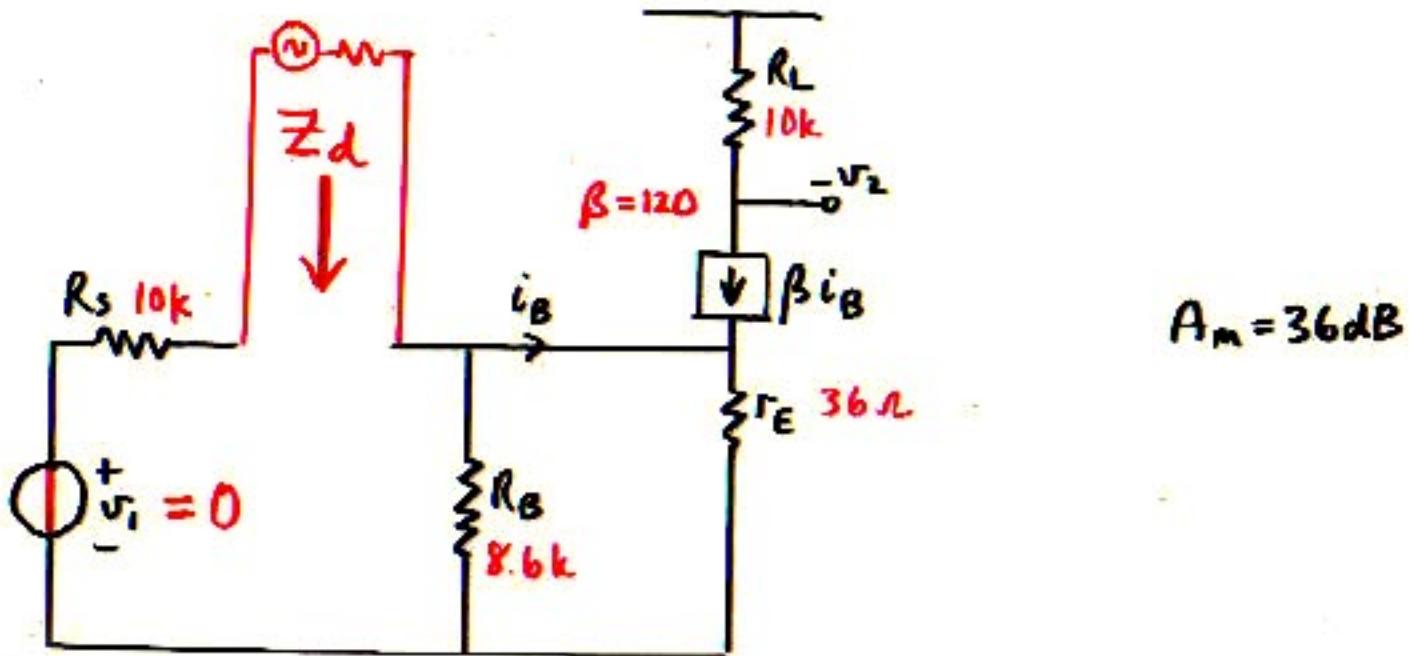


$$A_m = 36 \text{ dB}$$

Step 1.


$$\begin{aligned}
 Z_d &= R_d = R_s + R_B \parallel ((1+\beta)r_E) \\
 &= 10 + 8.6 \parallel (120 \times 0.036) \\
 &= 10 + 8.6 \parallel 4.3 \\
 &= 13k
 \end{aligned}$$

Exercise Solution

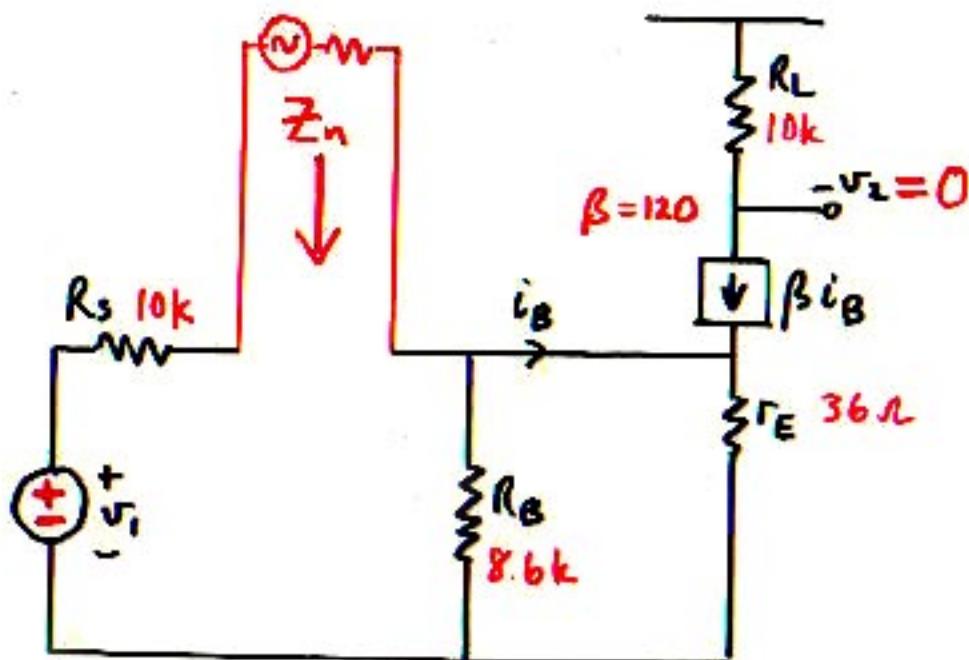

$$A_m = 36 \text{ dB}$$


Exercise Solution

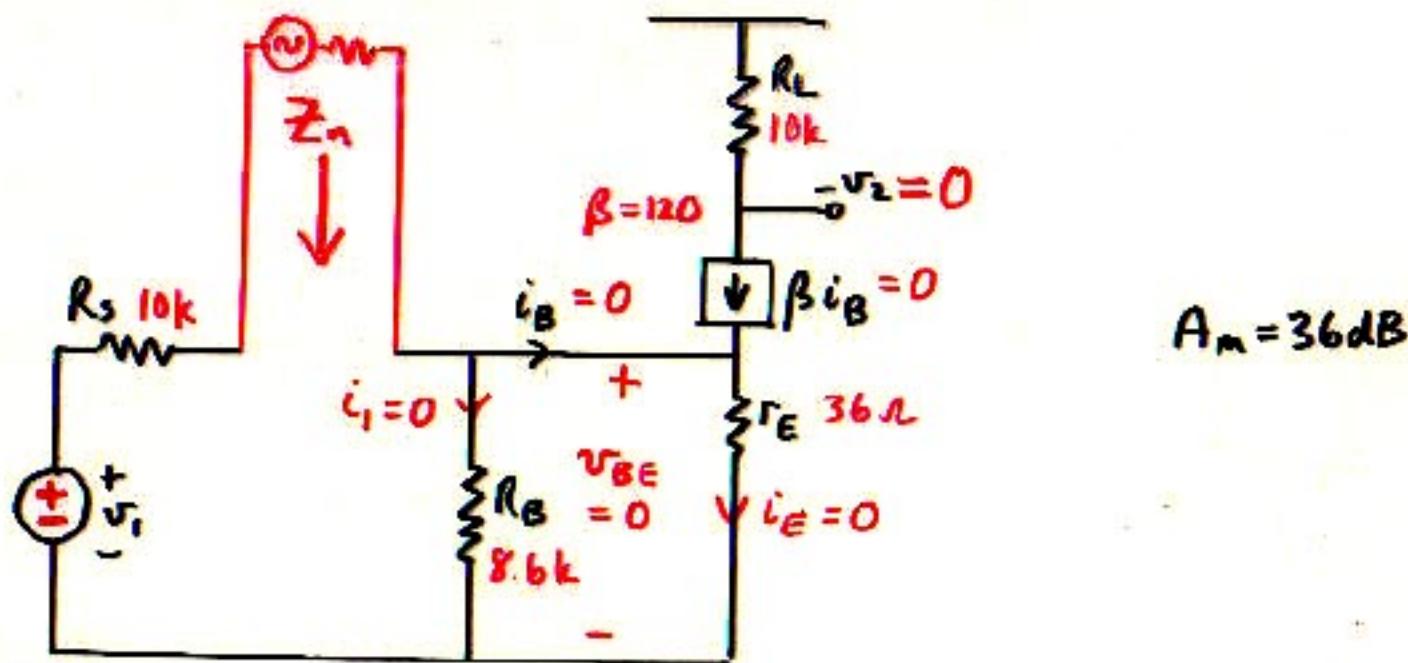

Step 2.

$$Z_n = R_n = \infty$$

Exercise Solution

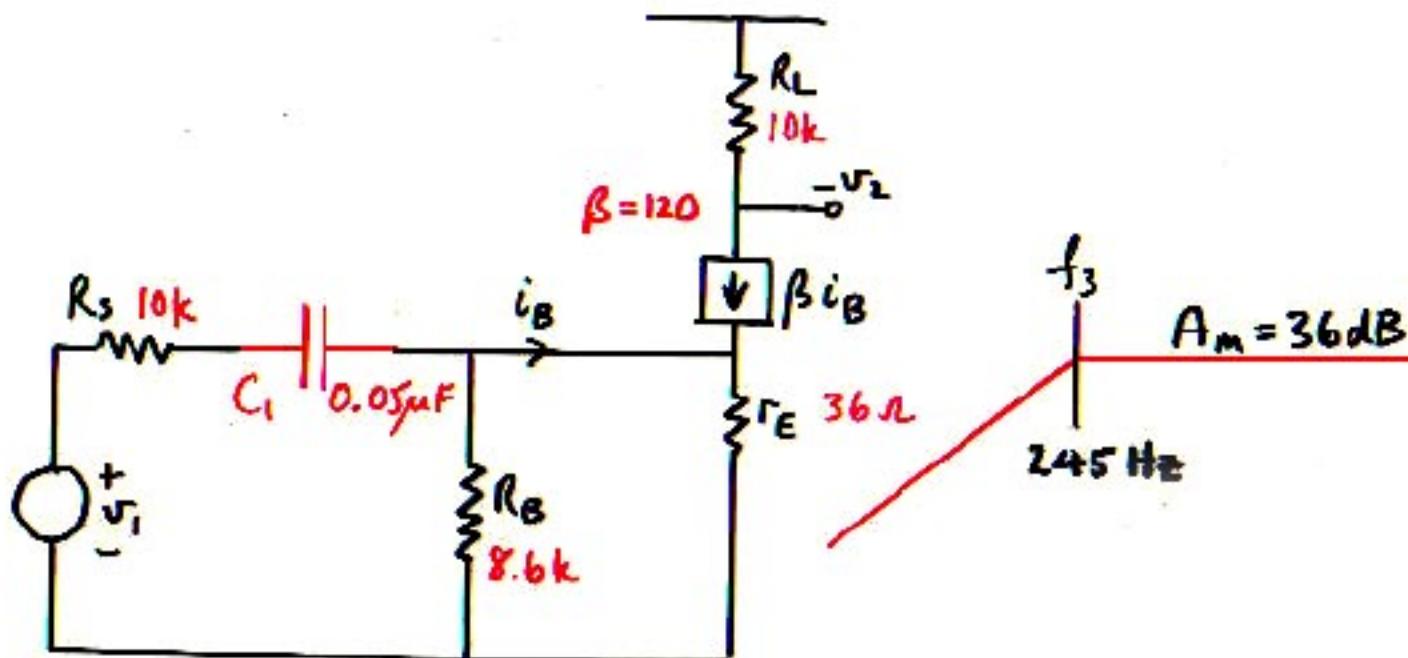

Hence corrected gain in the presence of $Z \rightarrow 1/sC_1$, is

$$A = A_m \frac{1 + \frac{Z}{Z_k}}{1 + \frac{Z}{Z_k}} = A_m \frac{1}{1 + \frac{1}{sC_1R_d}} = A_m \frac{1}{1 + \frac{\omega_3}{s}}$$

where

$$\omega_3 = \frac{1}{C_1R_d} \quad f_3 = \frac{159}{0.05 \times 13} = 245\text{Hz}$$

Generalization: Extra Element Theorem - #2

If the reference circuit is purely resistive,
 $Z_d = R_d$ and $Z_n = R_n$ are pure resistances.

If, also, the extra element is a pure reactance,
the Extra Element Theorem correction
factor gives the corner frequencies
directly.


Generalization: Extra Element Theorem - #3

The Extra Element Theorem can profitably be used to divide the analysis of a complicated circuit into successive simpler steps:


Designate one element as "extra," and the circuit without the element as the "reference circuit."
Calculate the gain of the (simpler) reference circuit, then restore the omitted element by the Extra Element Theorem correction factor.

This is a particularly useful approach when the designated "extra" element is a reactance and the reference circuit is purely resistive.


Exercise : lag-lead network

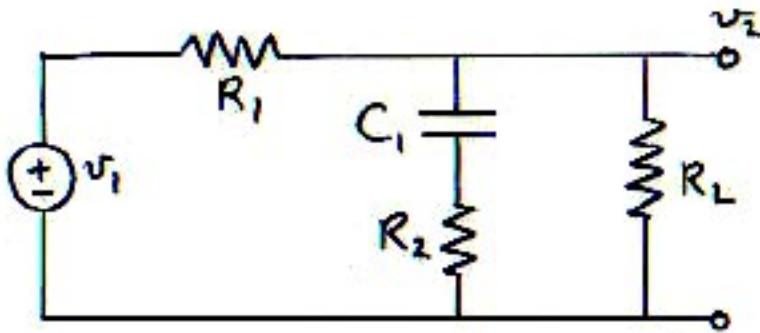

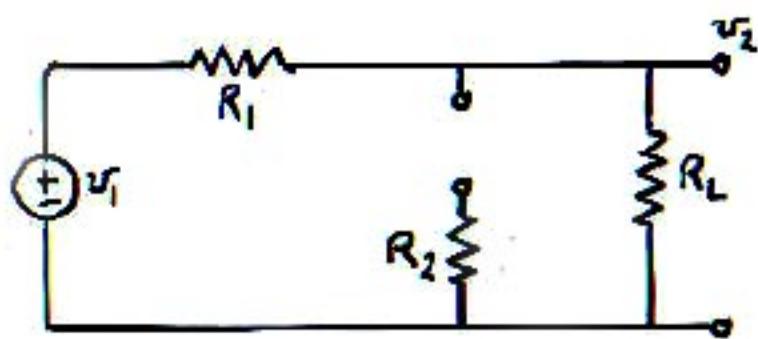Find the transfer function $A = v_2/v_1$ by designating C_1 as an "extra" element.




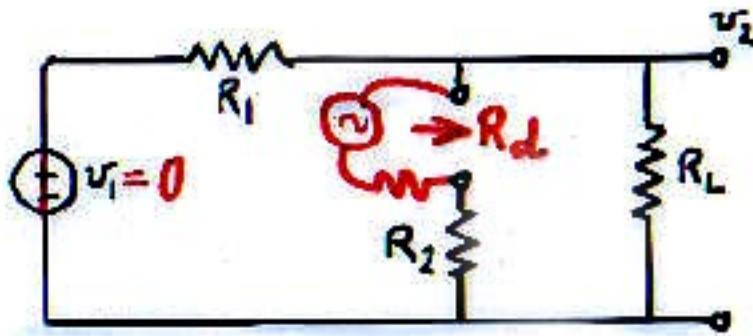
$$\frac{v_2}{v_1} = \frac{R_L}{R_1 + R_L}$$



$$\frac{v_2}{v_1} = \frac{R_L}{R_1 + R_L}$$

$$R_d = R_2 + R_1 \parallel R_L$$

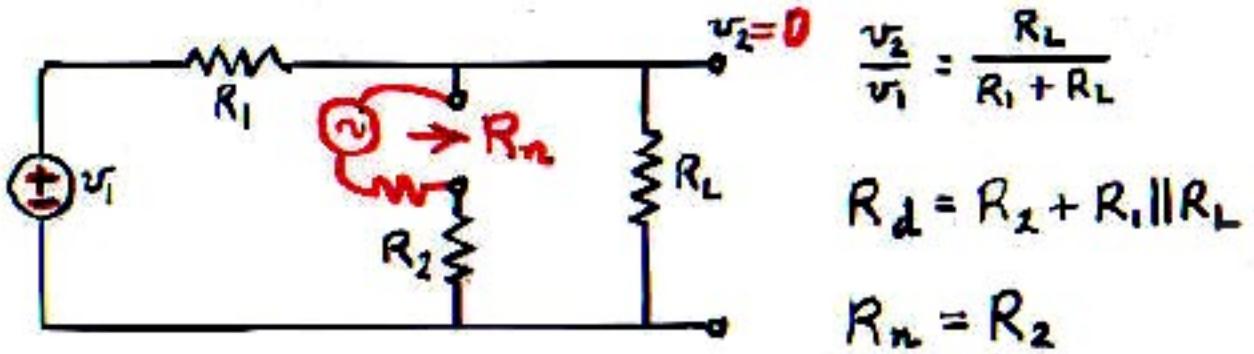

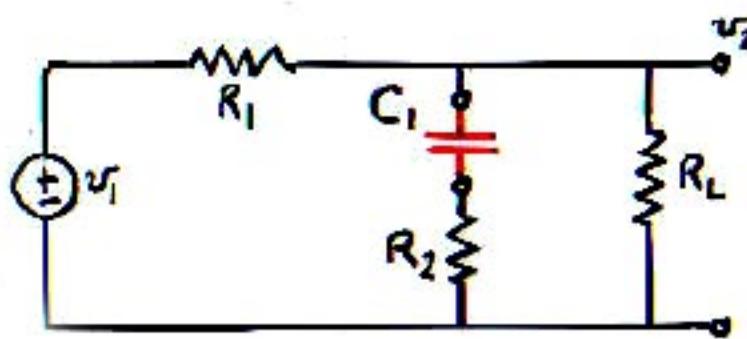

$$\frac{v_2}{v_1} = \frac{R_L}{R_1 + R_L}$$

$$R_d = R_2 + R_1 \parallel R_L$$

$$R_n = R_2$$

$$\frac{v_2}{v_1} = \frac{R_L}{R_1 + R_L} \cdot \frac{1 + sC_1 R_2}{1 + sC_1 (R_2 + R_1 \parallel R_L)}$$


The Extra Element Theorem may be used to find an extra element correction factor for any transfer function of a linear circuit. It is necessary merely to identify the "input" and "output" signals; Z_d and Z_n are then calculated as the driving point impedance seen by the extra element with the "input" zero and with the "output" nulled, respectively.

Examples of transfer functions:

- "output" \rightarrow current drawn from power supply (a transadmittance)
"input" \rightarrow input voltage
- "output" \rightarrow output voltage ripple component (a voltage gain; audio susceptibility of a power supply)
Power Supply Ripple Voltage
- "input" \rightarrow corresponding driving voltage (a self-impedance,
e.g. input or output impedance)
"output" \rightarrow any driving current

Example: Input impedance Z_i of a CE amplifier stage with emitter bypass capacitance as "extra" element.

"Reference circuit":

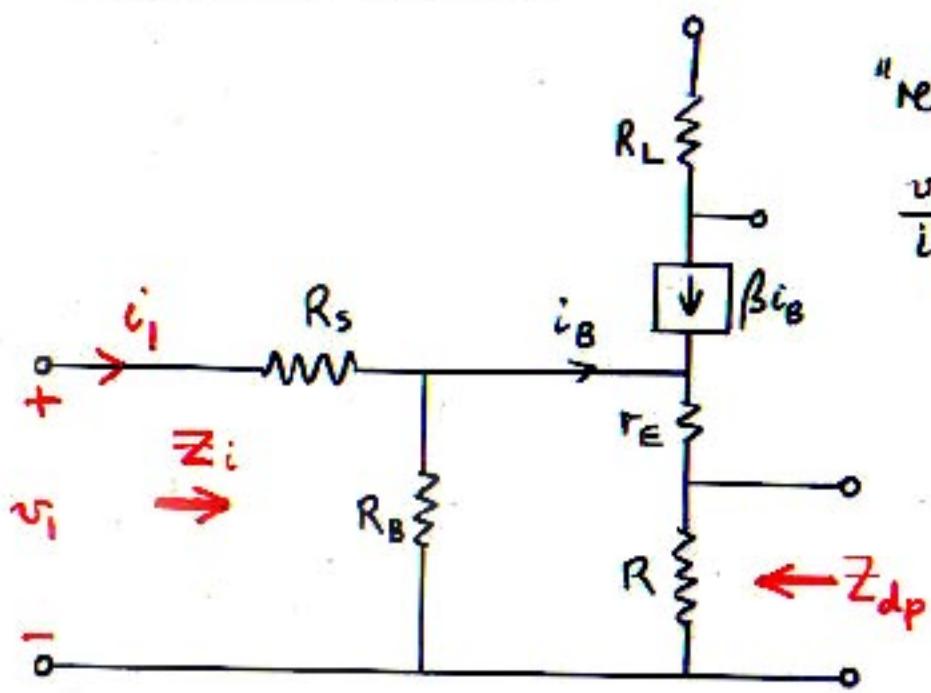


"reference transfer function":

$$\left. \frac{v_i}{i_1} \right|_{Z=\infty} = Z_i \Big|_{Z=\infty} = R_s + R_B \parallel (1+\beta)(r_E + R)$$

$$Z = \frac{1}{sC_E}$$

Example: Input impedance Z_i of a CE amplifier stage with emitter bypass capacitance as "extra" element.

"Reference circuit":

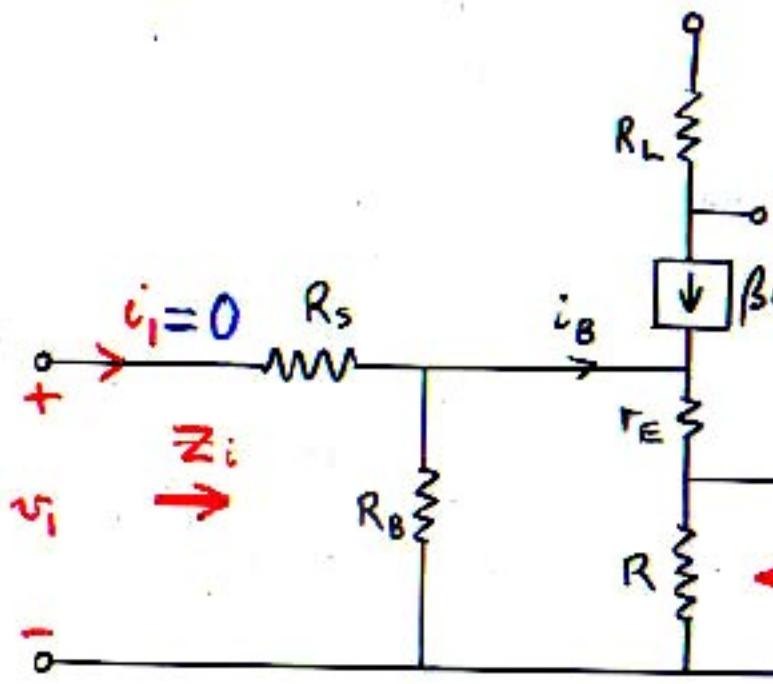

"reference transfer function":


$$\left. \frac{v_o}{i_i} \right|_{Z=\infty} = Z_i \left|_{Z=\infty} \right. = R_s + R_B \parallel (1+\beta)(r_e + R)$$

$$Z_d = Z_{dp} \left. \right|_{\text{"input" zero}} = Z_{dp} \Big|_{i_i=0} = R_d = R \parallel (r_e + \frac{R_B}{1+\beta})$$

$$Z_d = Z_{dp} \left. \right|_{\text{"input" zero}} = Z_{dp} \Big|_{i_i=0} = R_d = R \parallel (r_e + \frac{R_B}{1+\beta})$$

Example: Input impedance Z_i of a CE amplifier stage with emitter bypass capacitance as "extra" element.

"Reference circuit":

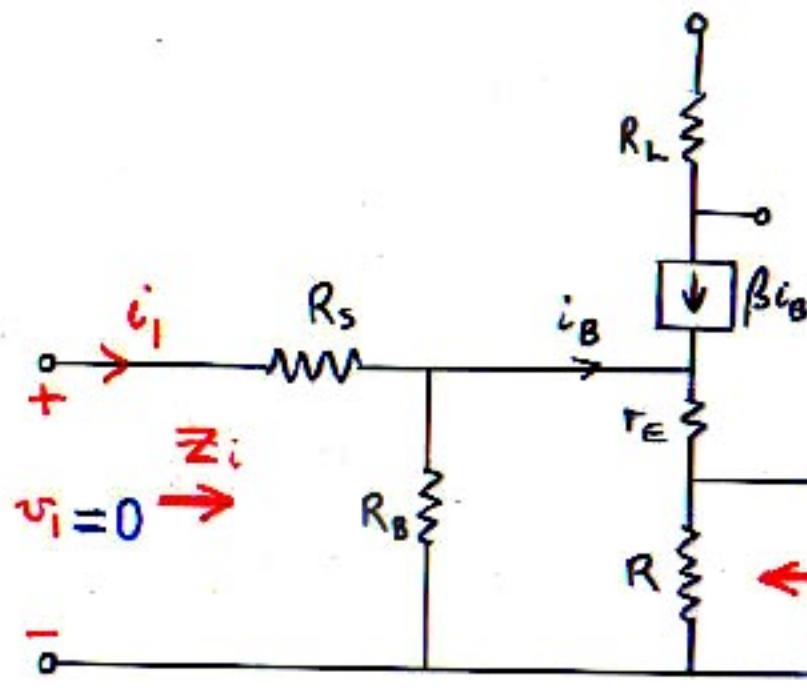

"reference transfer function":


$$\left. \frac{v_i}{i_i} \right|_{Z=\infty} = Z_i \left|_{Z=\infty} \right. = R_s + R_B \parallel (1+\beta)(r_E + R)$$

$$Z_{dp} = Z_n \quad Z = \frac{1}{sC_2}$$

$$Z_n = Z_{dp} \Big| \text{"output nulled"} = Z_{dp} \Big|_{v_o=0} = R_n = R \parallel (r_E + \frac{R_s \parallel R_B}{1+\beta})$$

Example: Input impedance Z_i of a CE amplifier stage with emitter bypass capacitance as "extra" element.

"Reference circuit":

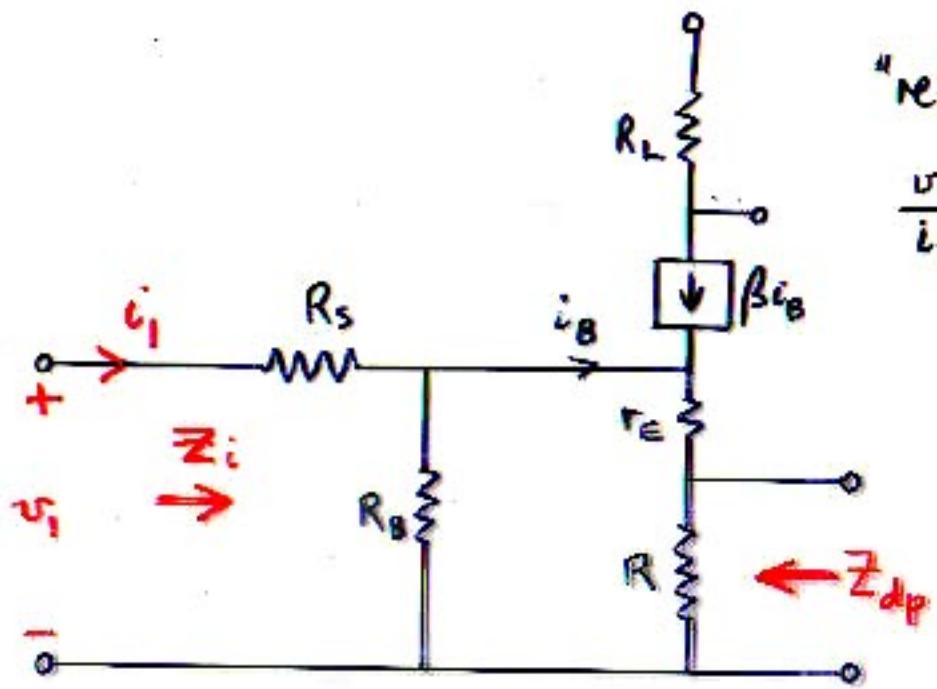

"reference transfer function":


$$\left. \frac{v_i}{i_1} \right|_{Z=\infty} = Z_i \left|_{Z=\infty} \right. = R_s + R_B \parallel (1+\beta)(r_e + R)$$

$$Z = \frac{1}{sC_2}$$

Hence, $Z_i = [R_s + R_B \parallel ((1+\beta)(r_e + R))] \frac{1 + sC_2 R_n}{1 + sC_2 R_d}$

Example: Input impedance Z_i of a CE amplifier stage with emitter bypass capacitance as "extra" element.

"Reference circuit":

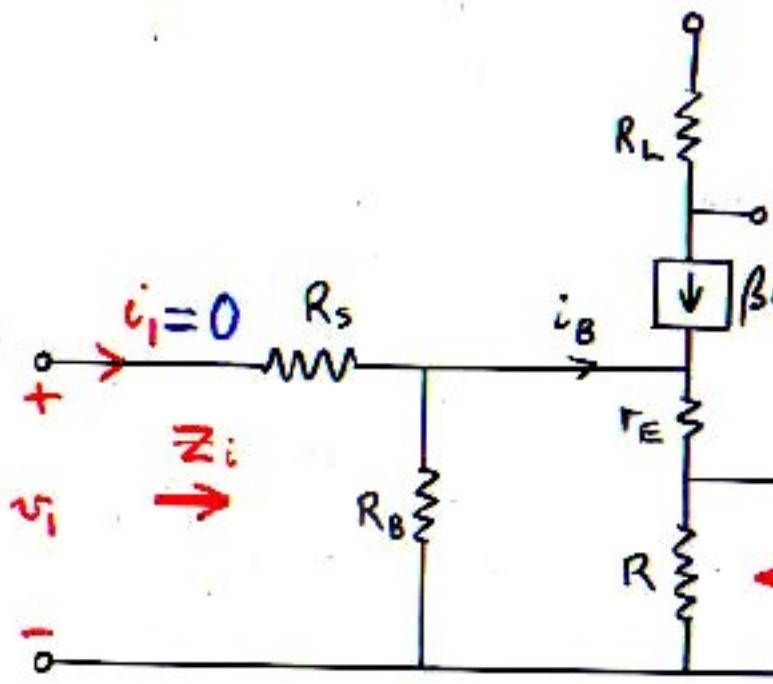


"reference transfer function":

$$\left. \frac{v_o}{i_i} \right|_{Z=0} = Z_i \left|_{Z=0} \right. = R_s + R_B \parallel (1+\beta)(r_e + R)$$

$$Z_d = \frac{1}{sC_2}$$

$$Z_d = Z_{dp} \left. \left(\text{"input" zero} \right) \right. = Z_{dp} \Big|_{i_i=0} = R_d = R \parallel \left(r_e + \frac{R_B}{1+\beta} \right)$$

"Reference circuit":

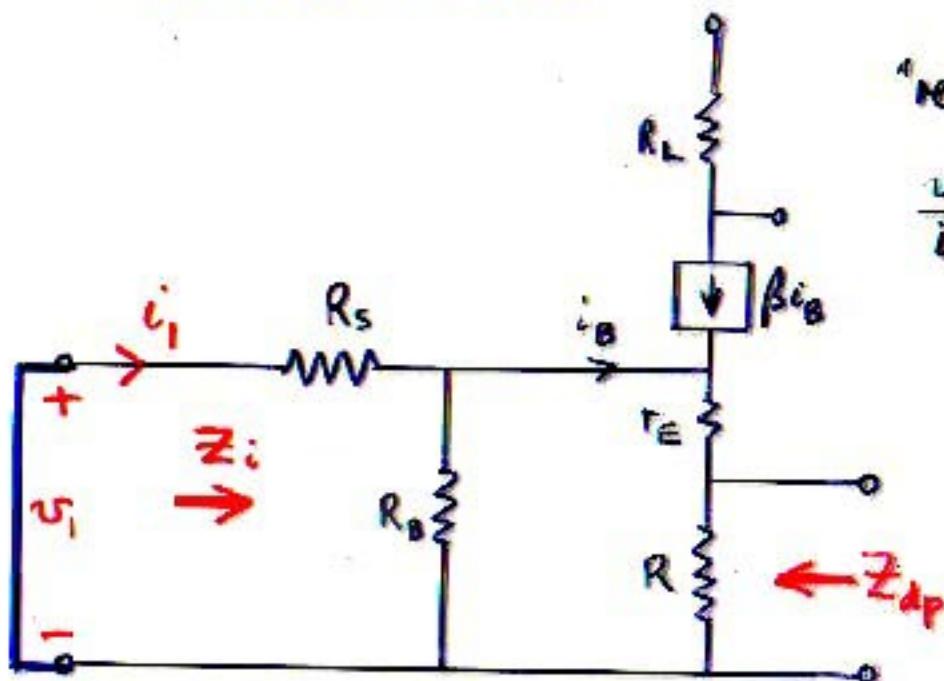


"reference transfer function":

$$\left. \frac{v_o}{i_1} \right|_{z=0} = \left. z_i \right|_{z=0} = R_s + R_B \parallel (1+\beta)(r_E + R)$$

A circuit symbol for a capacitor, consisting of two parallel lines. To its right, the equation $Z = \frac{1}{SC_2}$ is written.


NOTE: In the special case of a self-impedance, nulling the "output" voltage is the same as shorting the "input" current, because the "output" and "input" are at the same node pair.

Example: Lag-lead network

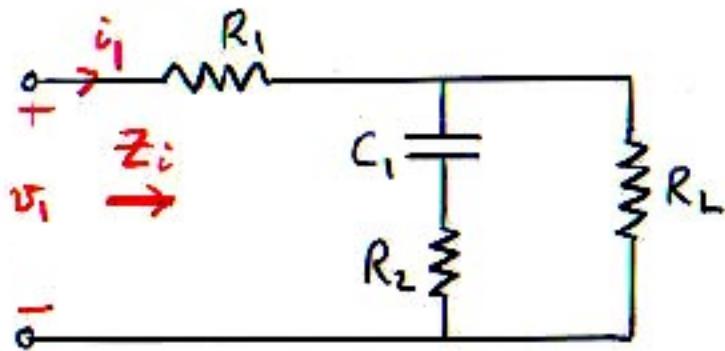

Find the input impedance $Z_i = v_i / i_1$ by designating C_1 as an "extra" element.


"Reference circuit":

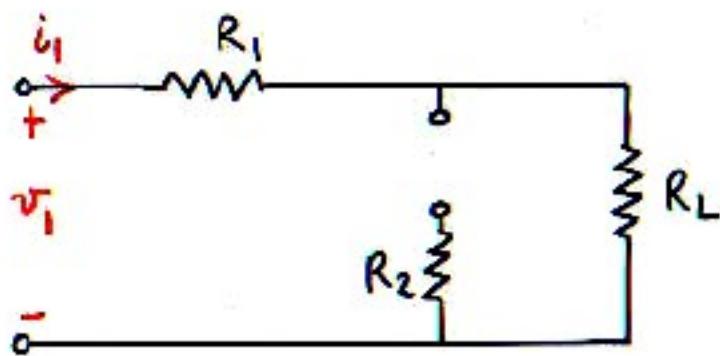

"Reference" input impedance:

$$Z_i|_{z=\infty} = \frac{v_i}{i_1}|_{z=\infty} = R_1 + R_L$$

"Reference circuit:"

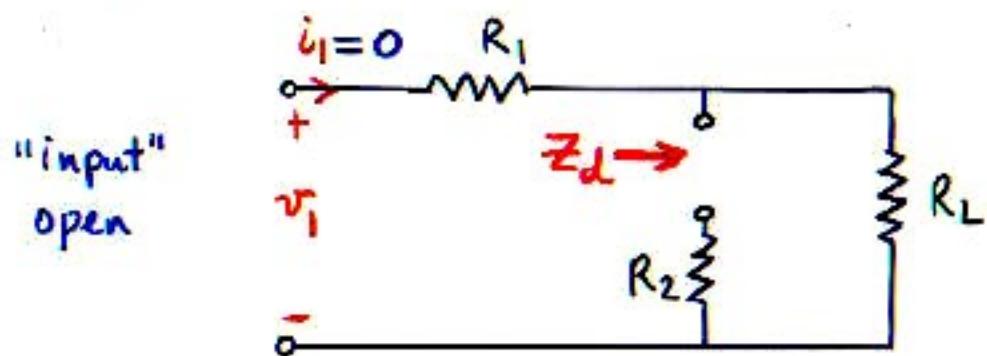


"input"
open

"Reference" input impedance:

$$Z_i|_{z=\infty} = \frac{v_1}{i_1}|_{z=\infty} = R_1 + R_L$$

$$Z_d = R_d = R_2 + R_L$$

"Reference circuit:"

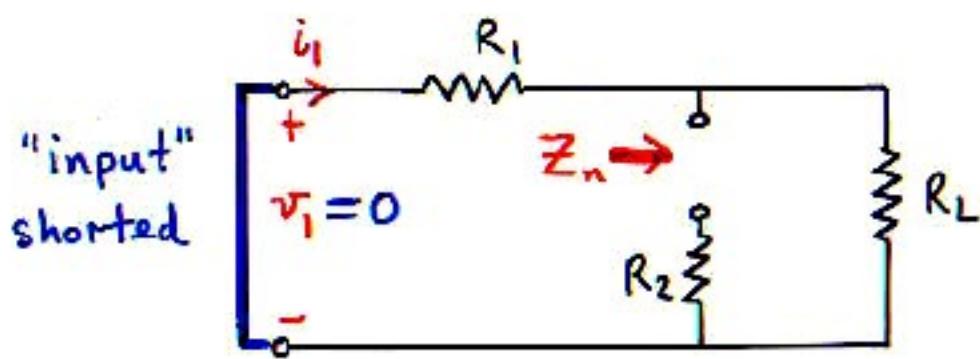

"Reference" input impedance:


$$Z_i|_{z=0} = \frac{v_1}{i_1}|_{z=0} = R_1 + R_L$$

$$Z_n = R_n = R_2 + R_1 \parallel R_L$$


Hence:

$$Z_i = (R_1 + R_L) \frac{1 + sC_1 R_n}{1 + sC_1 R_d}$$


Exercise: Lag-lead network

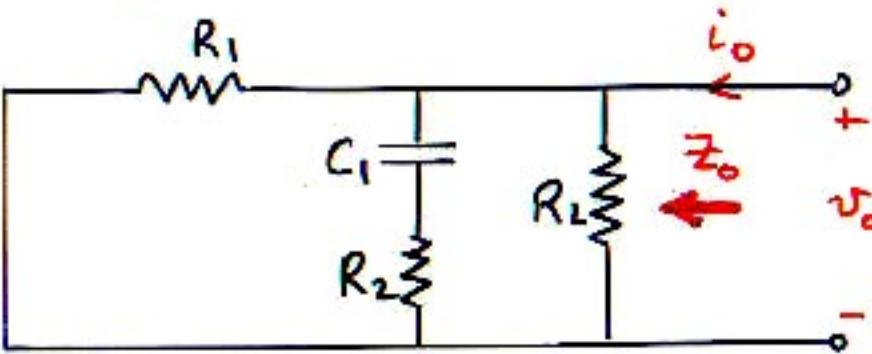

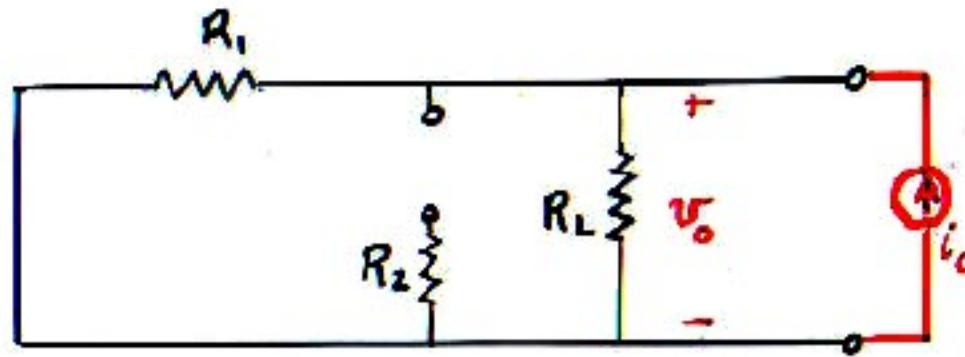
Find the output impedance $Z_o = v_o / i_o$ by designating C_1 as an "extra" element.



$$Z_o \Big|_{Z=\infty} \equiv \frac{v_o}{i_o} \Big|_{Z=\infty} = R_1 \parallel R_L$$

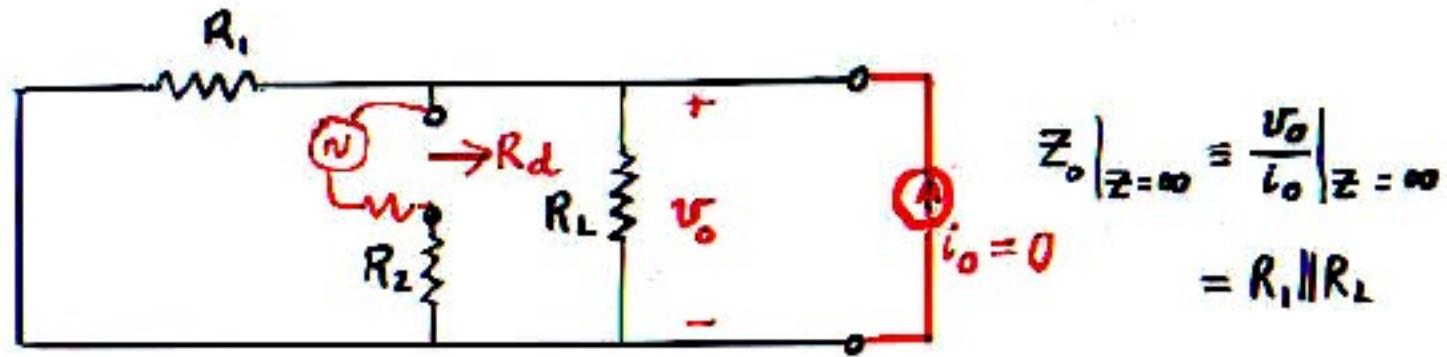

$$R_d = R_2 + R_1 \parallel R_L$$

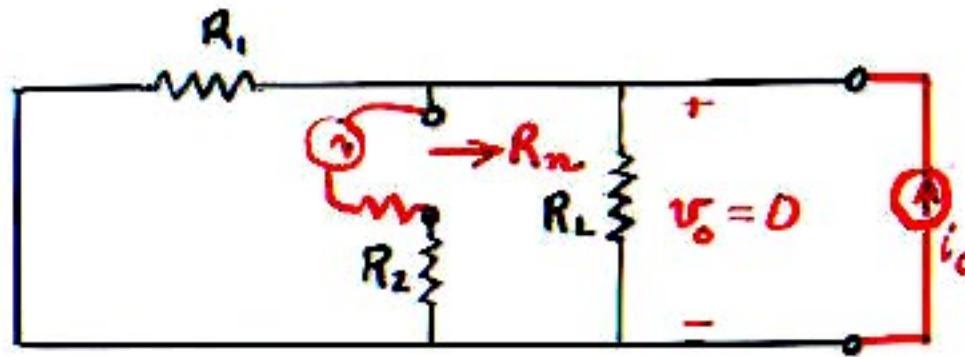

$$Z_0|_{Z=\infty} \equiv \frac{V_0}{I_0}|_{Z=\infty} = R_1 \parallel R_L$$

$$R_d = R_2 + R_1 \parallel R_L$$

$$R_n = R_2$$

With C_1 replaced:

$$Z_0 = R_1 \parallel R_L \frac{1 + s C_1 R_2}{1 + s C_1 (R_2 + R_1 \parallel R_2)}$$

Generalization: Extra Element Theorem - #4


The Extra Element theorem can be used to find an extra element correction factor for any transfer function; Z_d and Z_n are then the driving point impedances seen by the extra element with the "input" zero and with the "output" nulled, respectively.

When the transfer function is a self-impedance, such as the input impedance Z_i or the output impedance Z_o , nulling the "output" is the same as shorting the "input," hence


$$Z_d = Z_{dp} \left| \begin{array}{l} \text{"input" zero} \\ \text{---} \\ \text{"input" open} \end{array} \right. = Z_{dp} \left| \begin{array}{l} \text{"input" open} \end{array} \right.$$

$$Z_n = Z_{dp} \left| \begin{array}{l} \text{"output" nulled} \\ \text{---} \\ \text{"input" shorted} \end{array} \right. = Z_{dp} \left| \begin{array}{l} \text{"input" shorted} \end{array} \right.$$

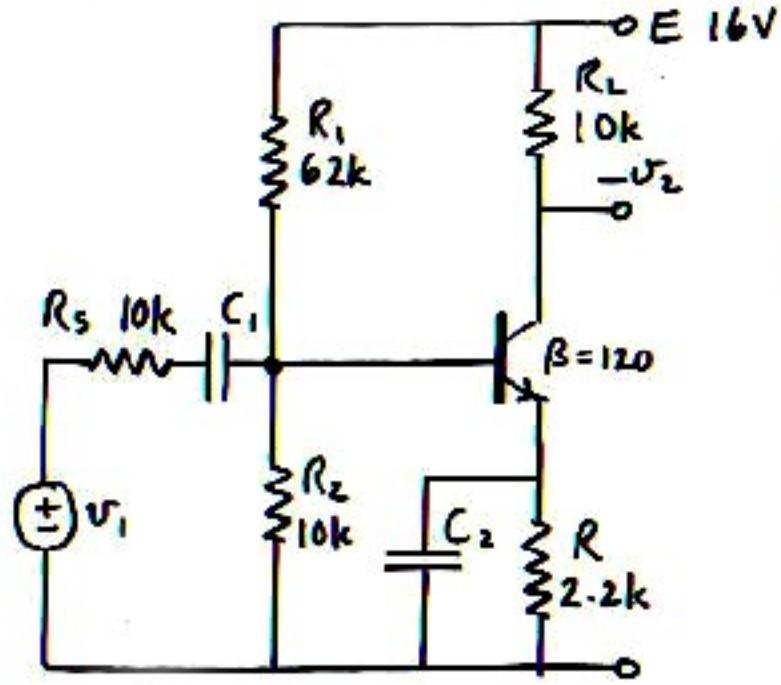
High-frequency properties of CE amplifier



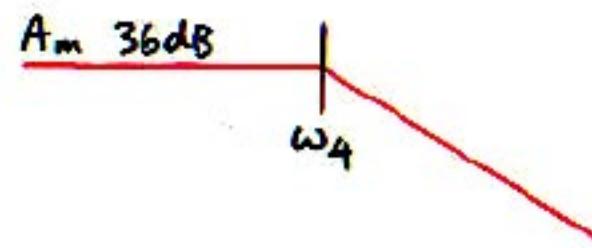Measurement indicates that there is a high-frequency pole ω_4 :




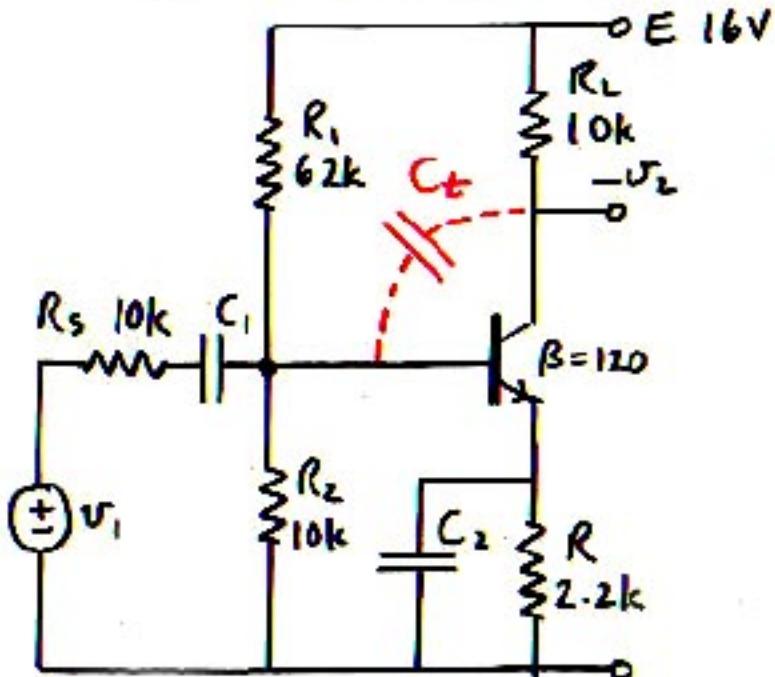High-frequency properties of CE amplifier



Measurement indicates that there is a high-frequency pole ω_4 :


$A_m = 36\text{dB}$

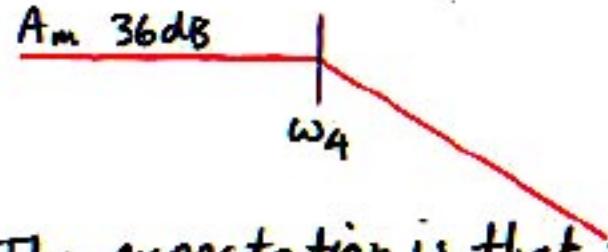


The expectation is that this is caused by the collector-base transition-layer capacitance C_t .

A typical value is $C_t = 5\text{pF}$. The resulting corner frequency with $R_L = 10k$ is $159/5 \times 10^{-6} \times 10 = 3.2\text{MHz}$. Since the actual corner frequency is much lower, there must be a multiplying effect on C_t resulting from its connection to the transistor base instead of to ground.

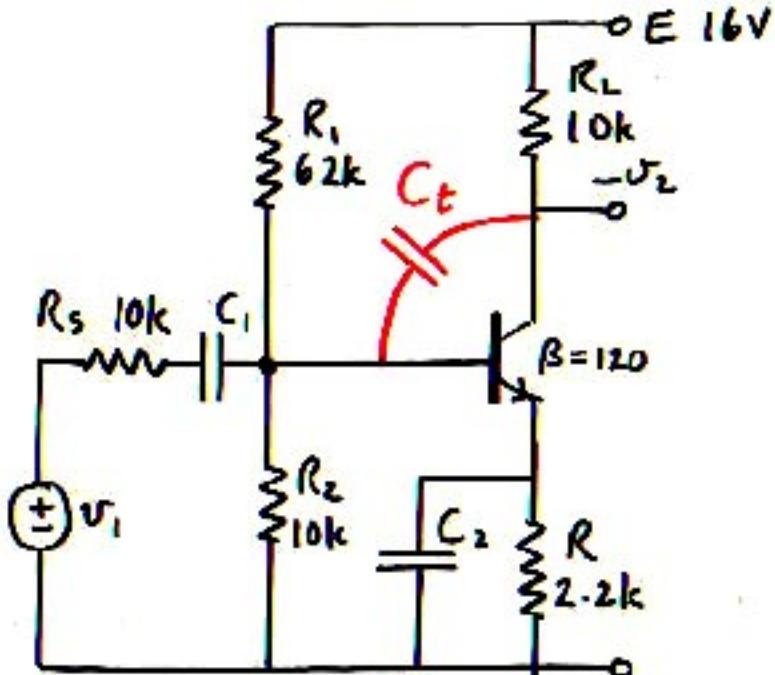High-frequency properties of CE amplifier




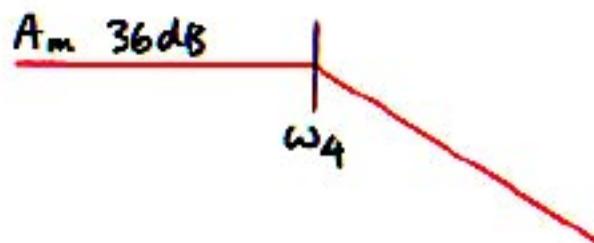Measurement indicates that there is a high-frequency pole ω_4 :




Since the midband gain $A_m = 36\text{dB}$ has already been determined, use the Extra Element Theorem to find the correction factor resulting from inclusion of $Z \rightarrow 1/sC_t$.

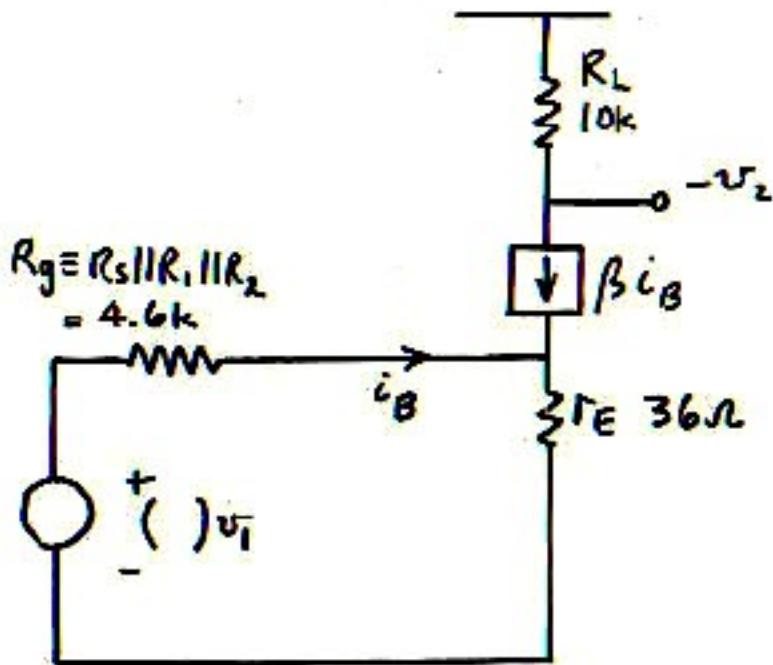Midband model after Thevenin reduction of R_s, R_i, R_2 :




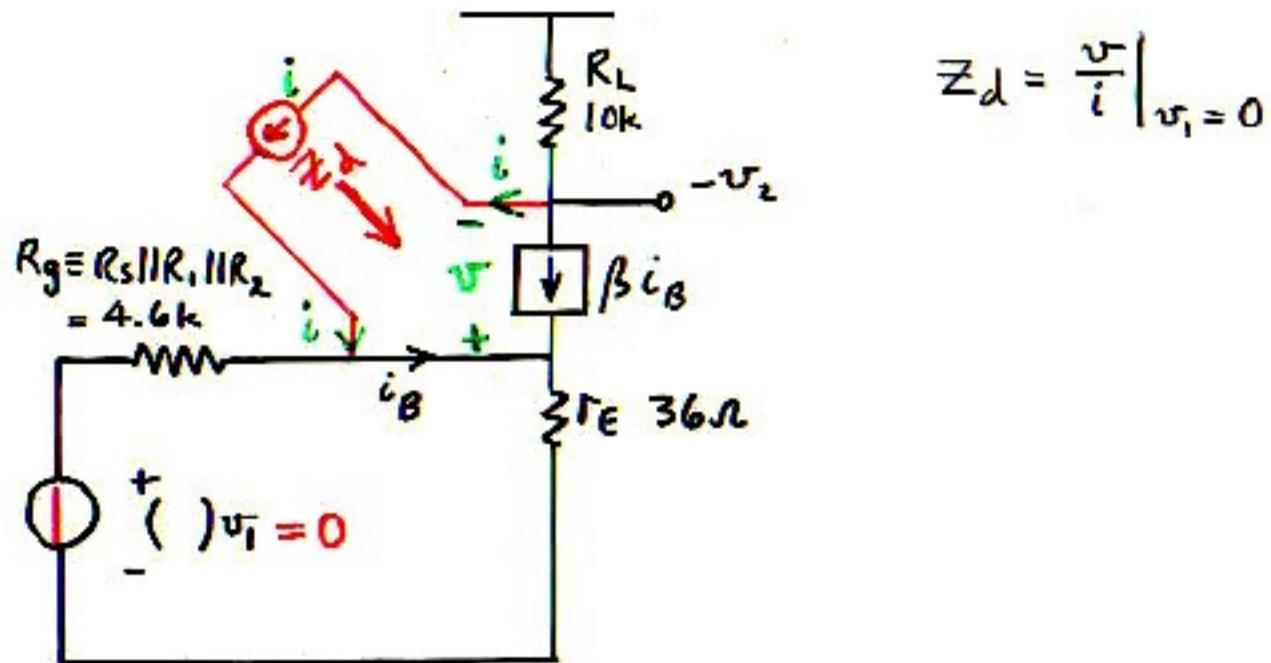Midband model after Thevenin reduction of R_s, R_1, R_2 :




$$Z_d = \frac{v}{i} \Big|_{v_1=0}$$

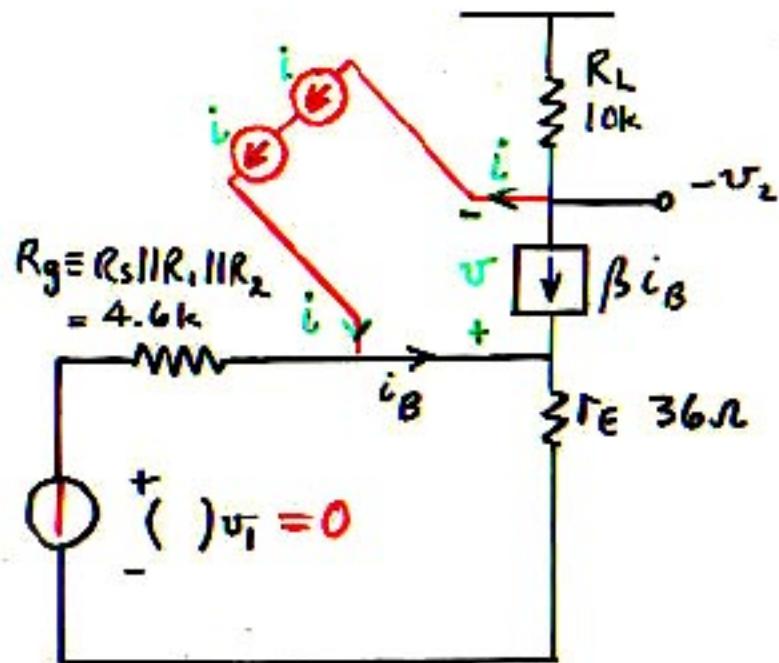Midband model after Thevenin reduction of R_s, R_1, R_2 :



The current generator i can be divided into two equal current generators in series.

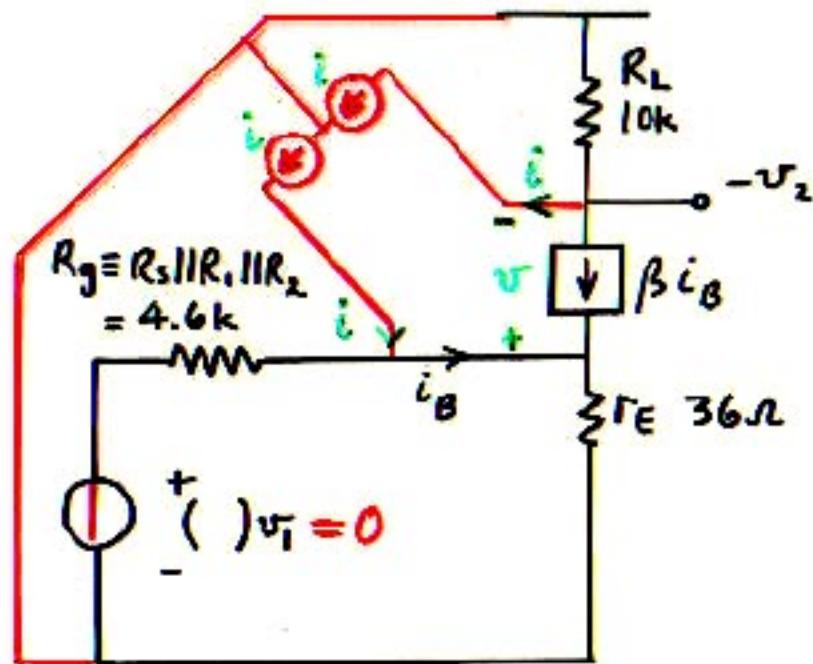
Midband model after Thevenin reduction of R_s, R_1, R_2 :



The current generator i can be divided into two equal current generators in series.


Since the voltage at the junction of the two current generators i is immaterial, the junction can be grounded.

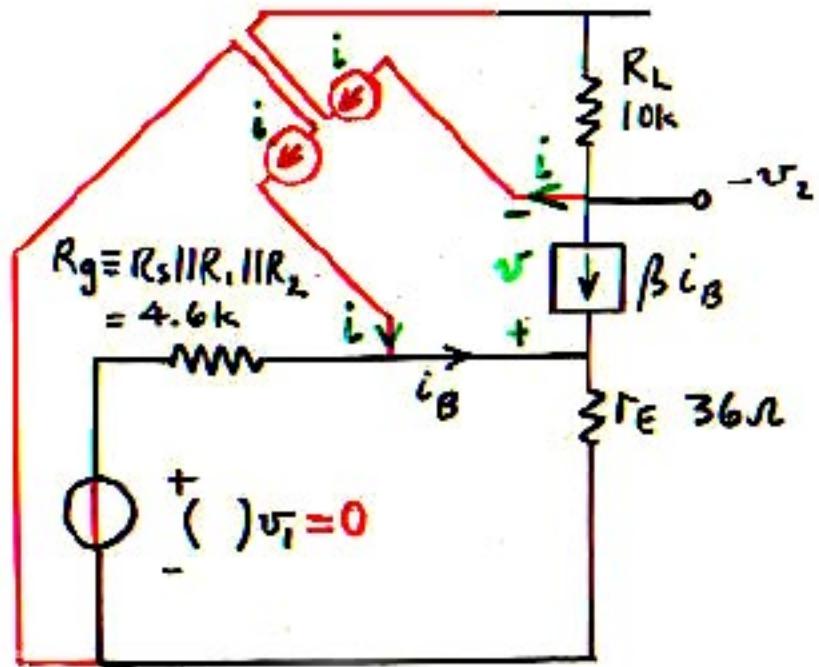Midband model after Thevenin reduction of R_s, R_1, R_2 :



A separate ground can be identified for each current generator i .

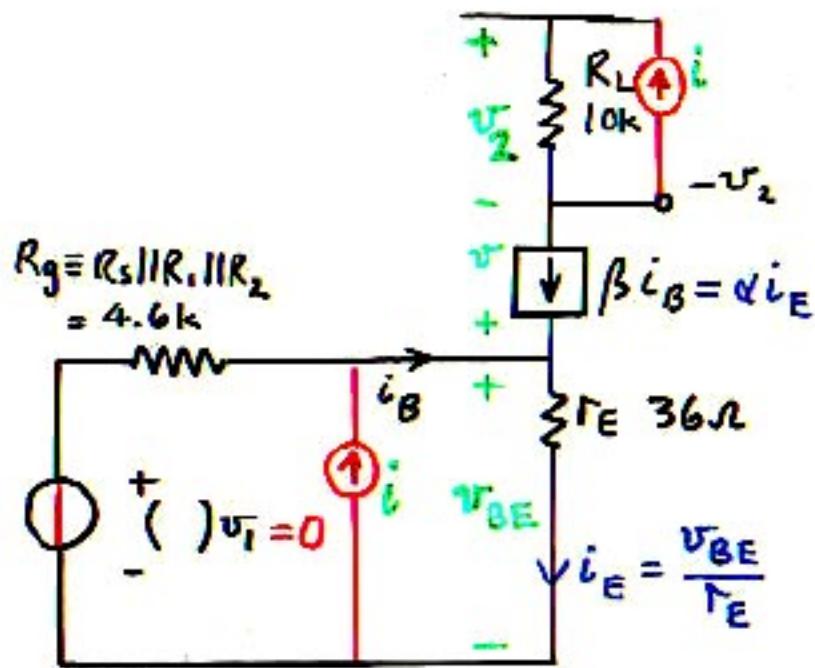Midband model after Thevenin reduction of R_s, R_1, R_2 :



Rearranged diagram.

$$Z_d = R_d = \frac{v}{i} = \frac{v_{BE}}{i} + \frac{v_2}{i}$$

$$v_{BE} = [R_g \parallel (1+\beta)r_E] i$$

$$v_2 = R_L (\alpha i_E + i) = R_L \left(\frac{\alpha}{r_E} v_{BE} + i \right)$$

$$R_d = \frac{v_{BE}}{i} + R_L \left(\frac{\alpha}{r_E} \frac{v_{BE}}{i} + 1 \right)$$

$$R_d = \left(1 + \frac{\alpha R_L}{r_E} \right) [R_g \parallel (1+\beta)r_E] + R_L = R_L \left[R_g \parallel (1+\beta)r_E \right] \left[\frac{1}{R_L} + \frac{\alpha}{r_E} + \frac{1}{R_g \parallel (1+\beta)r_E} \right]$$

$$= R_L \left[R_g \parallel (1+\beta)r_E \right] \left[\frac{1}{R_L} + \frac{\beta}{(1+\beta)r_E} + \frac{1}{R_g} + \frac{1}{(1+\beta)r_E} \right]$$


$$= \frac{R_g \parallel (1+\beta)r_E}{R_g \parallel r_E \parallel R_L} R_L = \frac{4.6 \parallel 4.3}{4.6 \parallel 0.036 \parallel 10} R_L = 62 R_L = 620k$$

Generalization: Floating Current Generator

A floating current generator can be replaced by two separate, equal, grounded current generators.

This is a useful technique in "doing the algebra on the circuit diagram."

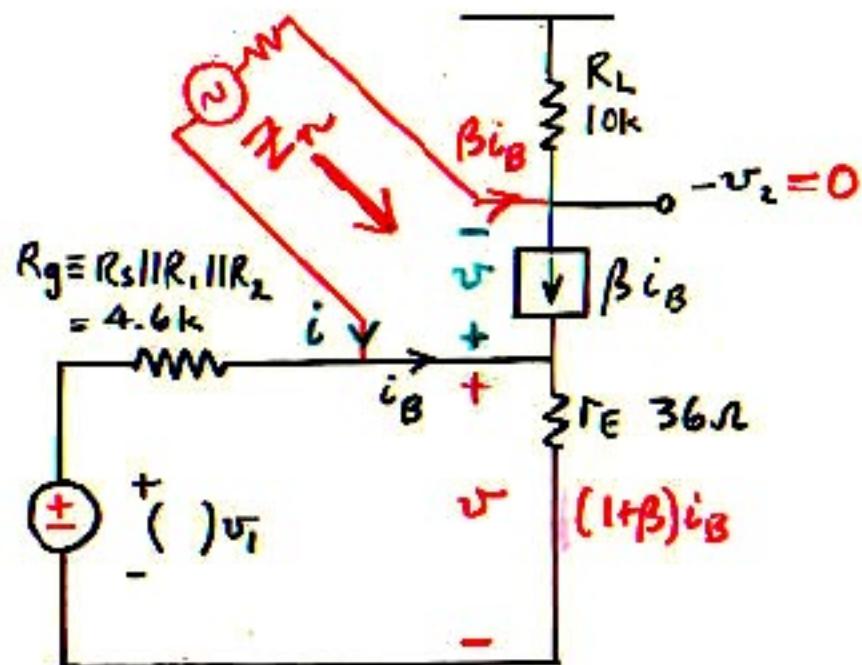
Midband model after Thevenin reduction of R_s, R_1, R_2 :



$$Z_n = R_n = \frac{v}{i} = \frac{(1+\beta)r_E i_B}{-\beta i_B} = -\frac{r_E}{\alpha} = -36\Omega$$

Midband model after Thevenin reduction of R_s, R_1, R_2 :

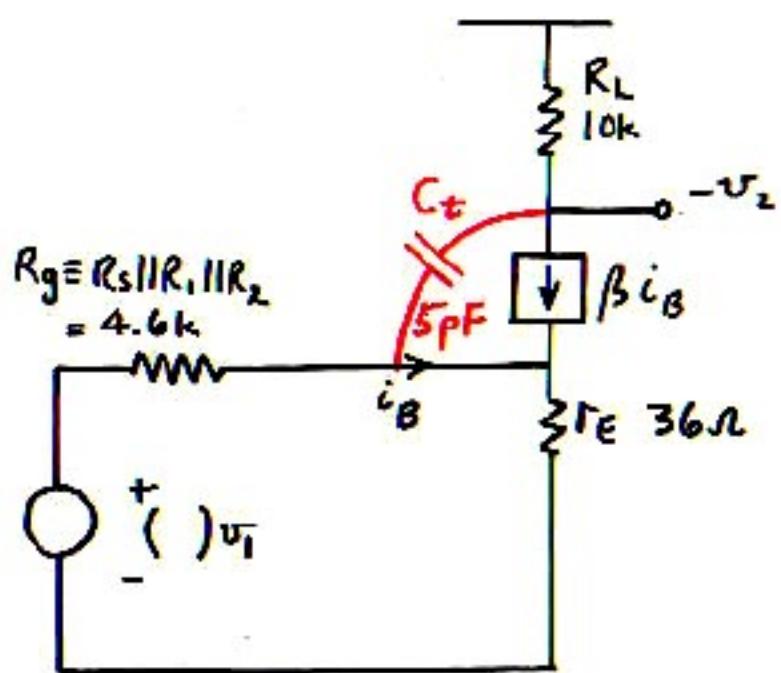Hence corrected gain after inclusion of C_t is



$$A = A_m \frac{1 + \frac{Z_n}{Z}}{1 + \frac{Z_d}{Z}} = A_m \frac{1 + sC_t + R_n}{1 + sC_t R_d}$$


$$= A_m \frac{1 - \frac{s}{\omega_4}}{1 + \frac{s}{\omega_4}} \quad \text{where}$$

$$\omega_4 \equiv \frac{1}{C_t R_d} \quad f_4 = \frac{159}{5 \times 10^{-6} \times 620} = 51\text{kHz}$$

$$\omega_5 \equiv \frac{1}{C_t R_n} \quad f_5 = \frac{159}{5 \times 10^{-6} \times 0.036} = 880\text{MHz}$$

Midband model after Thevenin reduction of R_s, R_1, R_2 :

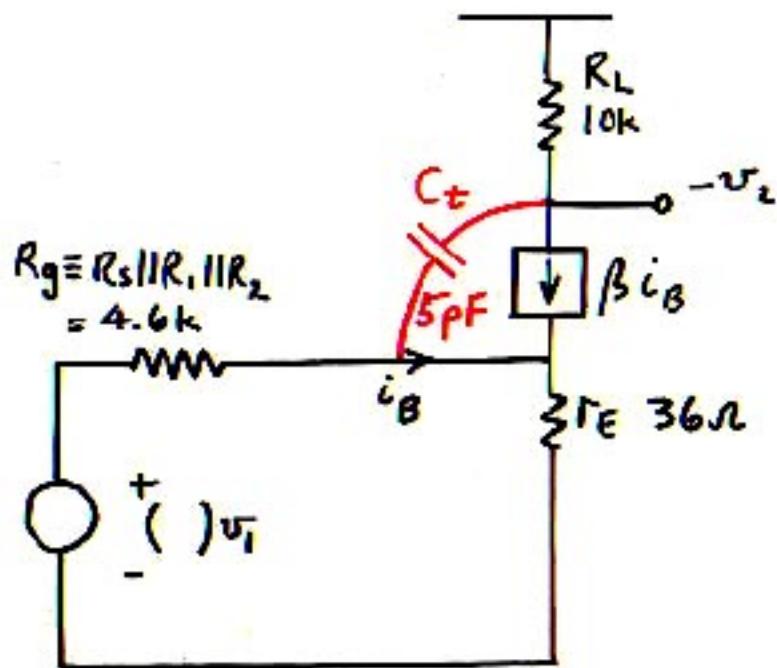Hence corrected gain after inclusion of C_t is



$$A = A_m \frac{1 + \frac{Z_n}{Z}}{1 + \frac{Z_d}{Z}} = A_m \frac{1 + sC_t R_n}{1 + sC_t R_d}$$

$$= A_m \frac{1 - \frac{s}{\omega_5}}{1 + \frac{s}{\omega_4}} \quad \text{where}$$

$$\omega_4 \equiv \frac{1}{C_t R_d} \quad f_4 = \frac{159}{5 \times 10^{-6} \times 620} = 51\text{kHz}$$

$$\omega_5 \equiv \frac{1}{C_t R_n} \quad f_5 = \frac{159}{5 \times 10^{-6} \times 0.036} = 880\text{MHz}$$


Note that the zero $\omega_5 = \frac{1}{C_t R_n} = \frac{\alpha}{C_t R_E}$ is negative (right half-plane), and is at a very high frequency unless there is substantial external emitter resistance and/or there is substantial external collector-base capacitance (as often exists).

Note that the pole $\omega_4 = \frac{1}{C_t R_d} = \frac{1}{C_t R_L} \frac{R_g R_{re} || R_L}{R_g || (1+\beta) r_E}$ is at a much lower frequency than $\omega_5 = \frac{1}{C_t R_L}$, and can be ascribed to an effective multiplication of C_t by a factor


$$m \equiv \frac{R_g || (1+\beta) r_E}{R_g || r_E || R_L} = \frac{R_g || (1+\beta) r_E}{R_g || r_E} \left(1 + \frac{R_g || r_E}{R_L} \right)$$

$R_g \gg (1+\beta) r_E \rightarrow 1 + \beta$
 $R_g \ll r_E \rightarrow 1$

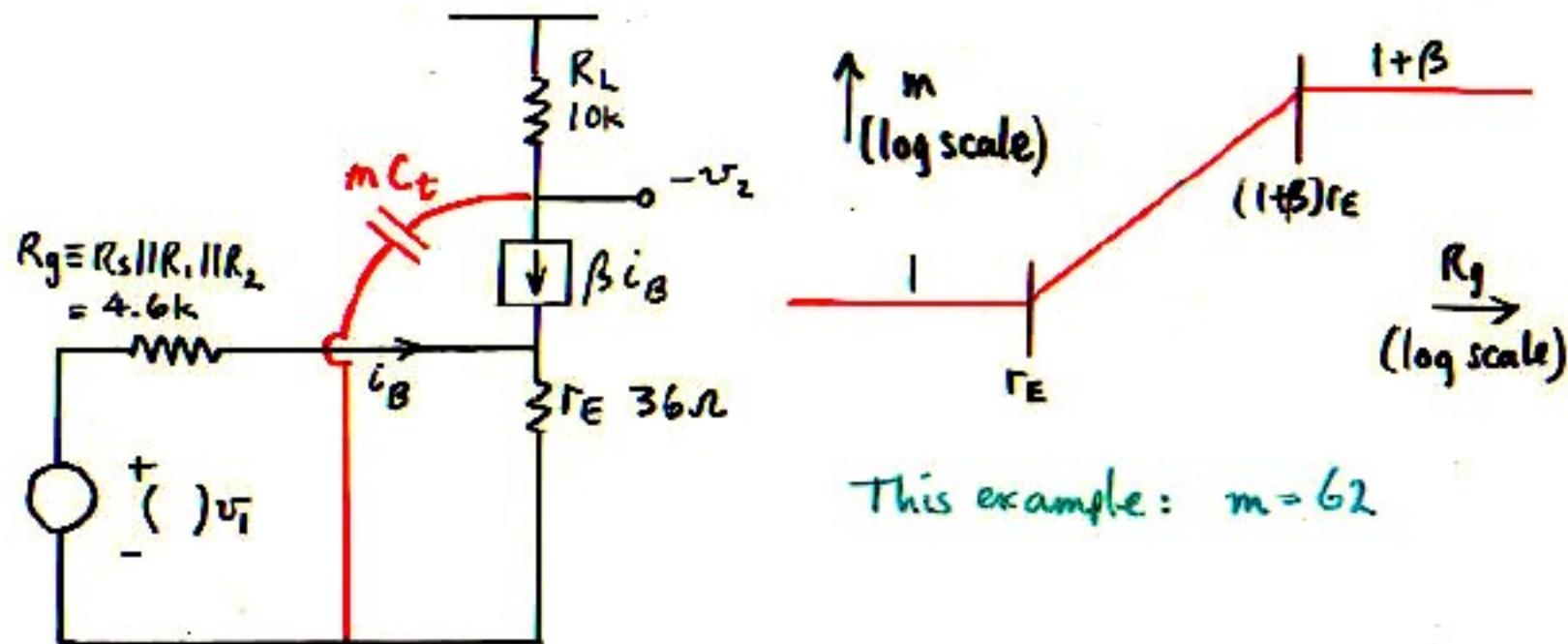Midband model after Thevenin reduction of R_s, R_1, R_2 :



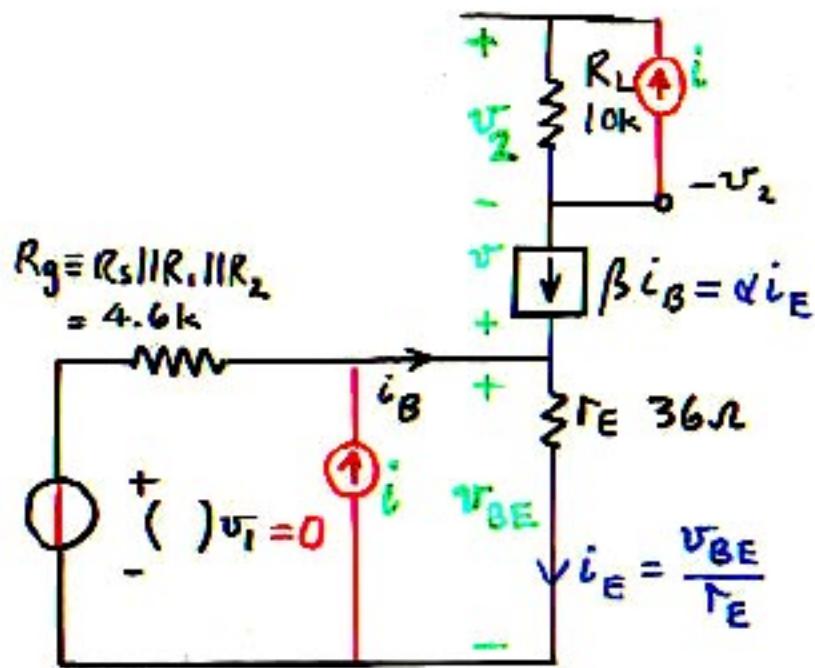Midband model after Thevenin reduction of R_s, R_1, R_2 :



Rearranged diagram.

$$Z_d = R_d = \frac{v}{i} = \frac{v_{BE}}{i} + \frac{v_2}{i}$$

$$v_{BE} = [R_g \parallel (1+\beta)r_E] i$$



$$v_2 = R_L (\alpha i_E + i) = R_L \left(\frac{\alpha}{r_E} v_{BE} + i \right)$$

$$R_d = \frac{v_{BE}}{i} + R_L \left(\frac{\alpha}{r_E} \frac{v_{BE}}{i} + 1 \right)$$

$$R_d = \left(1 + \frac{\alpha R_L}{r_E} \right) [R_g \parallel (1+\beta)r_E] + R_L = R_L \left[R_g \parallel (1+\beta)r_E \right] \left[\frac{1}{R_L} + \frac{\alpha}{r_E} + \frac{1}{R_g \parallel (1+\beta)r_E} \right]$$

$$= R_L \left[R_g \parallel (1+\beta)r_E \right] \left[\frac{1}{R_L} + \frac{\beta}{(1+\beta)r_E} + \frac{1}{R_g} + \frac{1}{(1+\beta)r_E} \right]$$
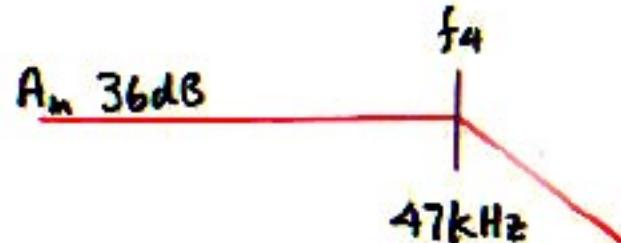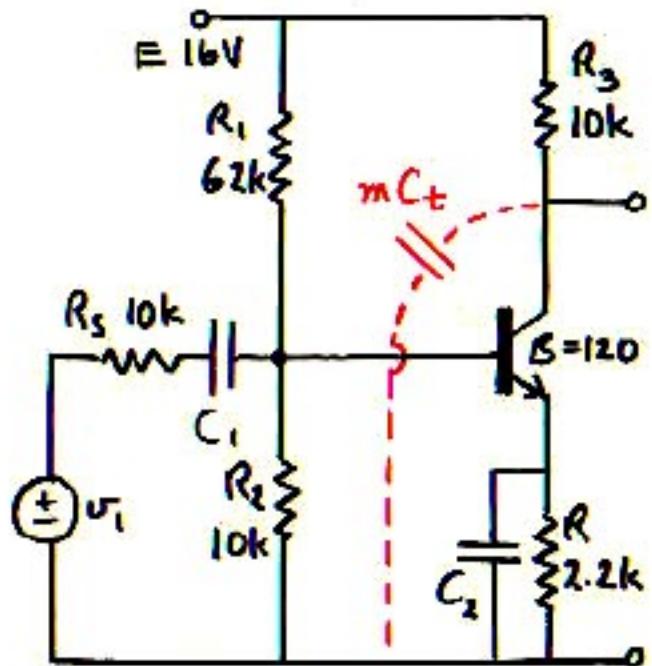
$$= \frac{R_g \parallel (1+\beta)r_E}{R_g \parallel r_E \parallel R_L} R_L = \frac{4.6 \parallel 4.3}{4.6 \parallel 0.036 \parallel 10} R_L = 62 R_L = 620\text{k}$$



By measurement, $f_4 = 47\text{kHz}$; hence


$$mC_t = \frac{159}{0.047 \times 10} = 340\text{pF}$$

So:

$$C_t = 340/62 = 5.5\text{pF}$$

(Note: 13 pF of 10:1 scope probe is negligible)

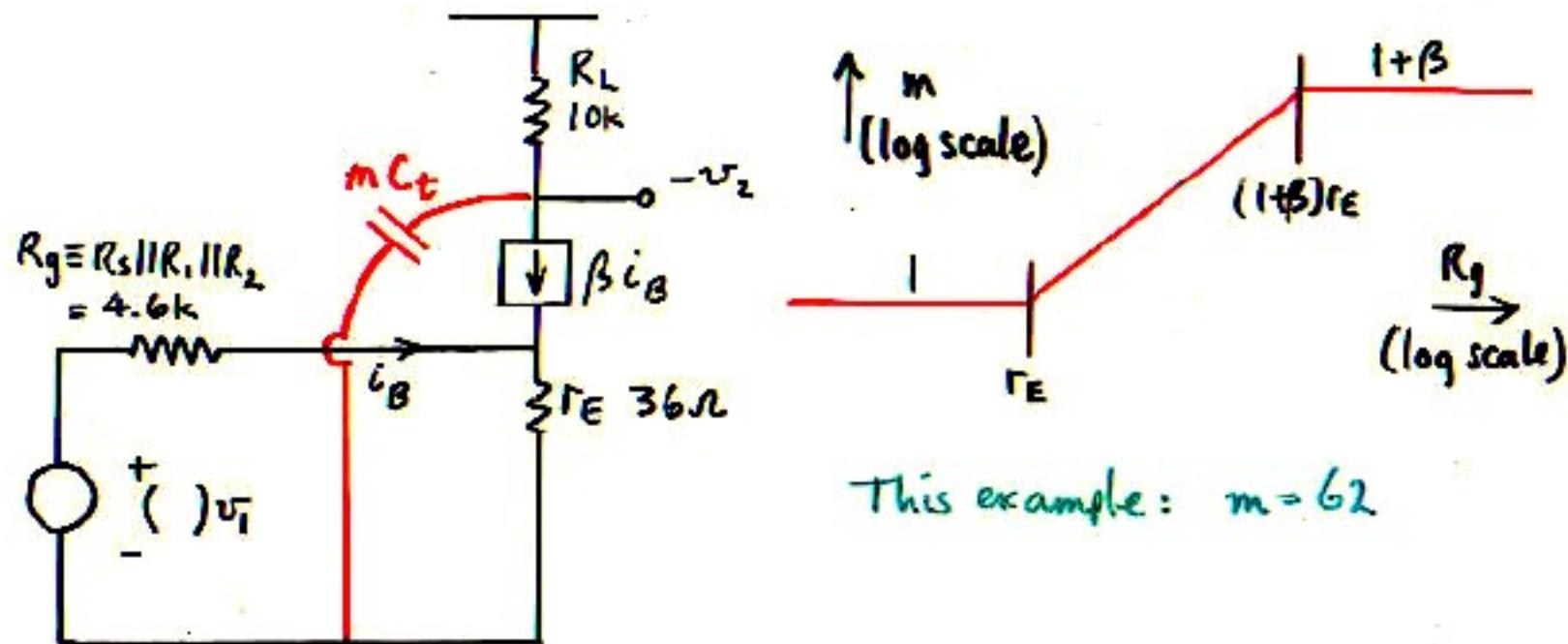Midband model after Thevenin reduction of R_s, R_1, R_2 :



Alternative method for calculation of Z_d

There are two forms of the Extra Element theorem:

$$A = A|_{z=\infty} \frac{1 + \frac{z_n}{z}}{1 + \frac{z_d}{z}} = A|_{z=0} \frac{1 + \frac{z}{z_n}}{1 + \frac{z}{z_d}}$$

where $A|_{z=0} = \frac{z_n}{z_d} A|_{z=\infty}$

Hence in general

$$\frac{A|_{z=0}}{A|_{z=\infty}} = \frac{z_n}{z_d}$$

It may be easier to find $A|_{z=0}$, $A|_{z=\infty}$, and z_n than to find Z_d directly.

Example: Addition of collector-base capacitance C_t to the CE amplifier stage. $A|_{z=\infty}$ and z_n were easily found:

$$A|_{z=\infty} = A_m = \frac{R_B}{R_s + R_B} \cdot \frac{\beta R_L}{R_g + (1+\beta) r_E} \quad z_n = R_n = -\frac{r_E}{\alpha}$$

The Extra Element Theorem as derived applies to the correction factor resulting from an extra shunt element.

There is a corresponding form to find the correction factor resulting from an extra series element:

$$\text{reference gain} \downarrow \\ \text{gain } |_{Z} = \text{gain } |_{Z=\infty} \frac{1 + \frac{z_n}{Z}}{1 + \frac{z_d}{Z}}$$

$$= \text{gain } |_{Z=\infty} \frac{\frac{z_n}{Z}}{\frac{z_d}{Z}} \frac{\frac{Z}{z_n} + 1}{\frac{Z}{z_d} + 1}$$

$$\text{reference gain} \downarrow \\ = \text{gain } |_{Z=0} \frac{1 + \frac{Z}{z_n}}{1 + \frac{Z}{z_d}}$$

$$= \left(\frac{z_n}{z_d} \cdot \text{gain } |_{Z=\infty} \right) \frac{1 + \frac{Z}{z_n}}{1 + \frac{Z}{z_d}}$$

This must be
the gain when $Z=0$

Alternative method for calculation of Z_d

There are two forms of the Extra Element theorem:

$$A = A|_{z=\infty} \frac{1 + \frac{z_n}{z}}{1 + \frac{z_d}{z}} = A|_{z=0} \frac{1 + \frac{z}{z_n}}{1 + \frac{z}{z_d}}$$

where $A|_{z=0} = \frac{z_n}{z_d} A|_{z=\infty}$

Hence in general


$$\frac{A|_{z=0}}{A|_{z=\infty}} = \frac{z_n}{z_d}$$

It may be easier to find $A|_{z=0}$, $A|_{z=\infty}$, and z_n than to find Z_d directly.


Example: Addition of collector-base capacitance C_t to the CE amplifier stage. $A|_{z=\infty}$ and z_n were easily found:

$$A|_{z=\infty} = A_m = \frac{R_B}{R_s + R_B} \cdot \frac{\beta R_L}{R_g + (1+\beta) r_E} \quad z_n = R_n = -\frac{r_E}{\alpha}$$

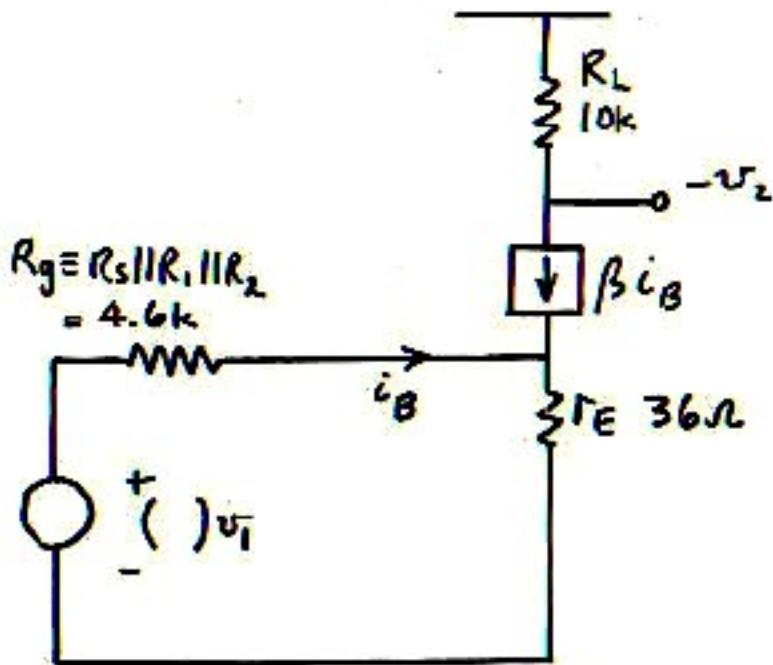Midband model after Thevenin reduction of R_s, R_i, R_2 :



Model for calculation of $A|_{z=0}$

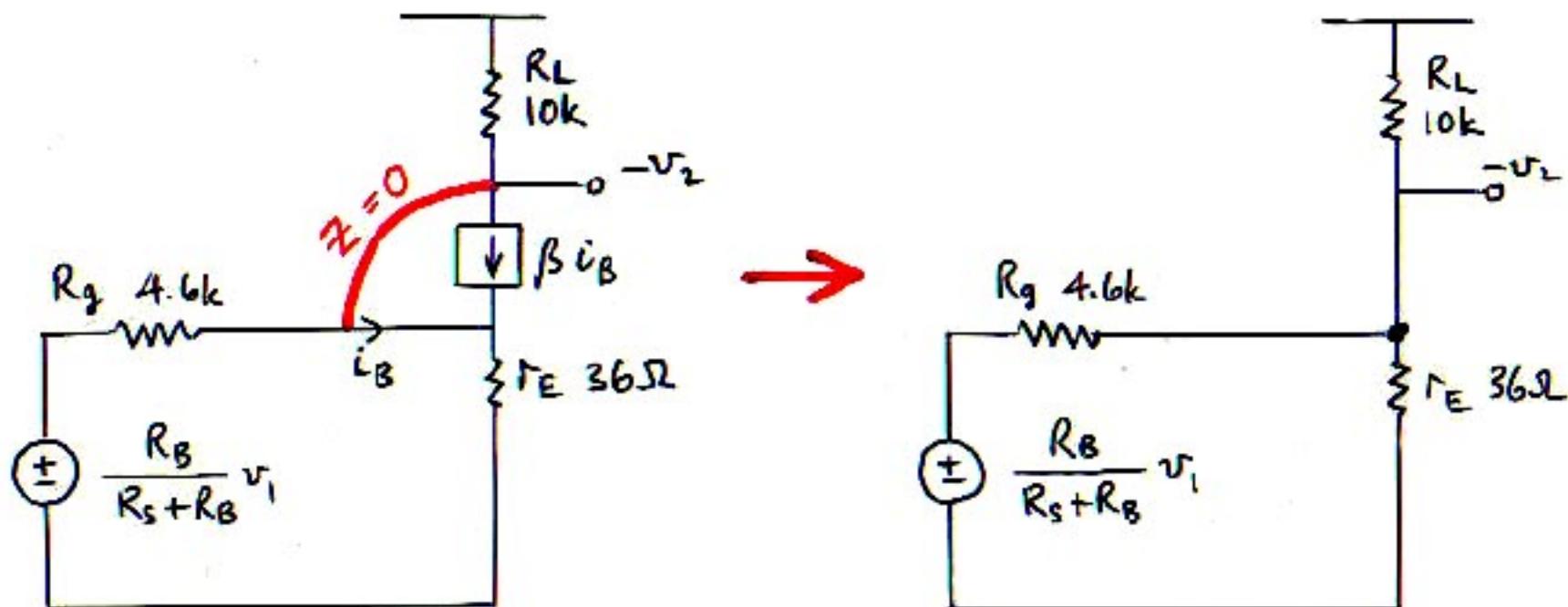

$$A|_{z=0} = -\frac{R_B}{R_s + R_B} \frac{r_E \parallel R_L}{R_g + r_E \parallel R_L} = -\frac{R_B}{R_s + R_B} \frac{R_g \parallel r_E \parallel R_L}{R_g}$$

Hence:

$$Z_d = R_d = R_n \frac{A|_{z=\infty}}{A|_{z=0}} = \frac{r_E}{\alpha} \frac{\beta R_L}{R_g + (1+\beta)r_E} \frac{R_g}{R_g \parallel r_E \parallel R_L} = \frac{R_g \parallel ((1+\beta)r_E)}{R_g \parallel r_E \parallel R_L} R_L$$

This is much easier than was the direct calculation of Z_d !

Generalization: Extra Element theorem - #5

The two reference gains and the two driving point impedances are related by:

$$\frac{A|_{z=0}}{A|_{z=\infty}} = \frac{z_n}{z_d}$$

One reference gain is always known or is easily found.
 z_n is always easier to find than z_d .

Therefore:

It is often easier to find the other reference gain and to use the above ratio relation for z_d , than to find z_d directly.